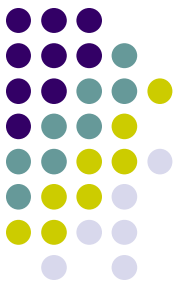


CHAPTER 5


BASIC BJT AMPLIFIERS

(AC ANALYSIS)




The Bipolar Linear Amplifier

- Bipolar transistors have been traditionally used in linear amplifier circuits because of their relatively high gain.
- To use the circuit as an amplifier, the transistor needs to be *biased with a DC voltage* at a quiescent point (Q-point) such that the transistor is *biased in the forward-active region*.
- If a time-varying signal is superimposed on the dc input voltage, the output voltage will change along the transfer curve producing a time-varying output voltage.
- If the time-varying output voltage is directly proportional to and larger than the time-varying input voltage, then the circuit is a *linear amplifier*.

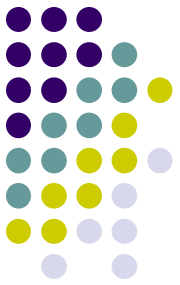


- The linear amplifier applies **superposition principle**
 - Response – sum of responses of the circuit for each input signals alone
 - So, for linear amplifier,
 - DC analysis is performed with AC source turns off or set to zero
 - AC analysis is performed with DC source set to zero


EXAMPLE

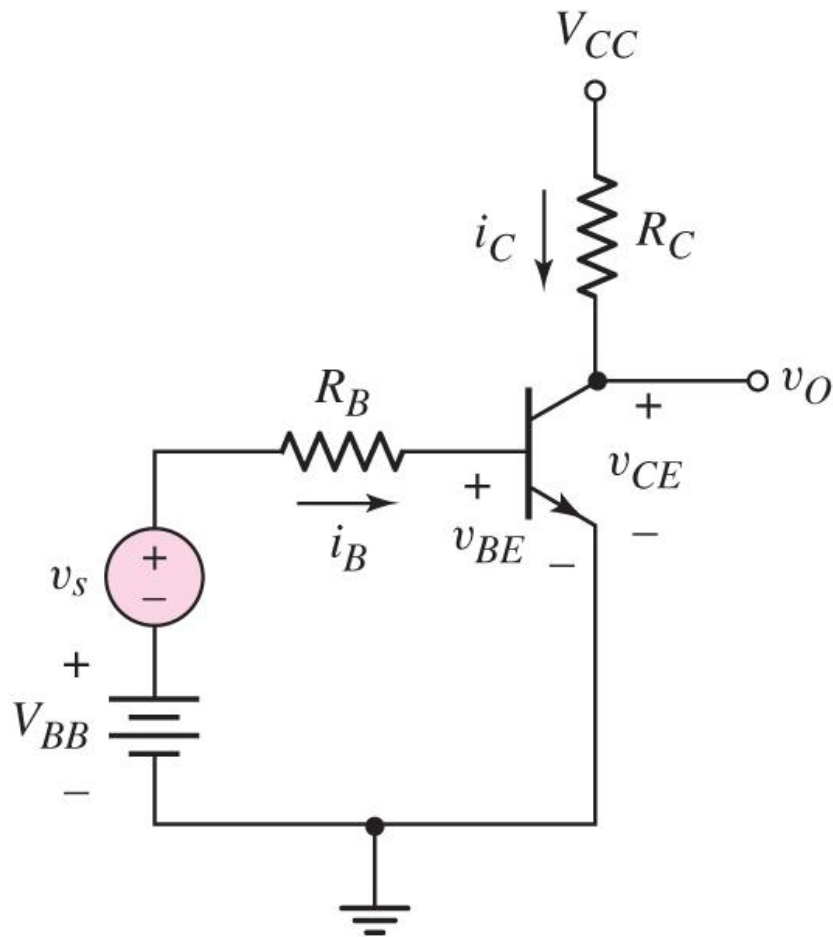

- i_C , i_B and i_E ,
- v_{CE} and v_{BE}

Sum of both
ac and dc
components

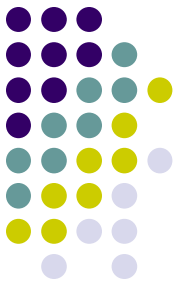

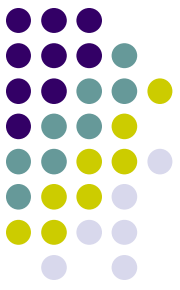

Graphical Analysis and ac Equivalent Circuit


- From the concept of small signal, all the time-varying signals are superimposed on dc values. Then:

$$i_B = I_{BQ} + i_b$$


$$i_C = I_{CQ} + i_c$$

$$v_{CE} = V_{CEQ} + v_{ce}$$

$$v_{BE} = V_{BEQ} + v_{be}$$

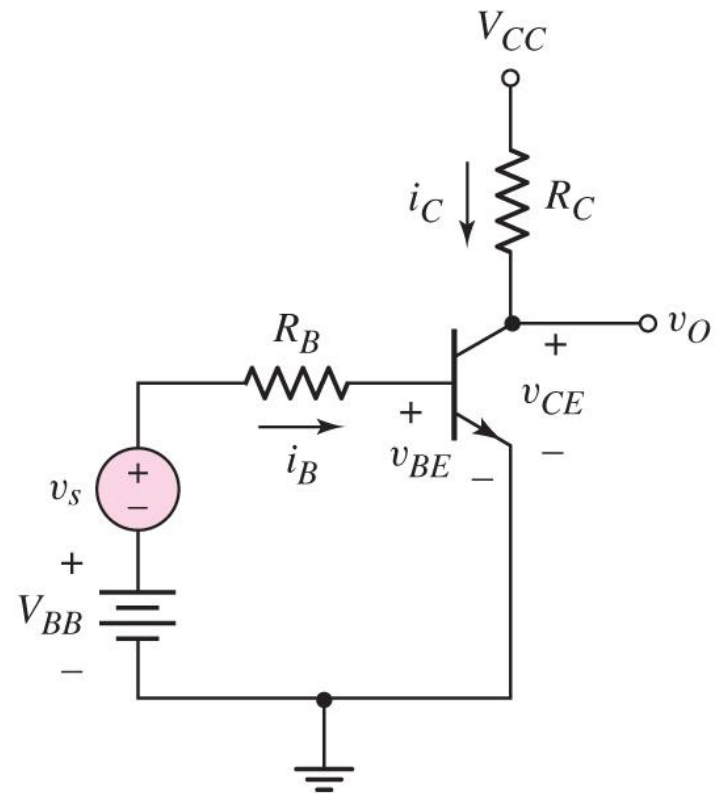


PERFORMING DC and AC analysis

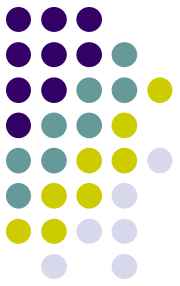


DC ANALYSIS


Turn off AC
SUPPLY = short
circuit

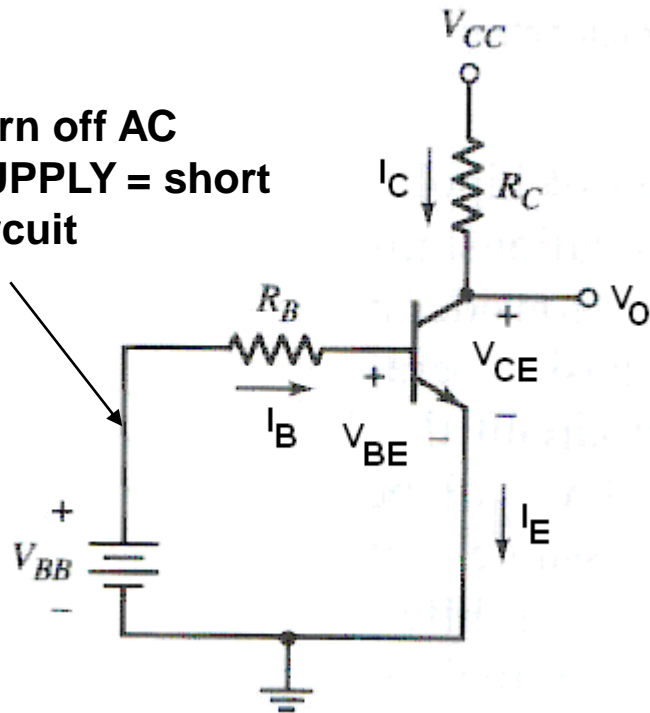



AC ANALYSIS

Turn off DC
SUPPLY = short
circuit

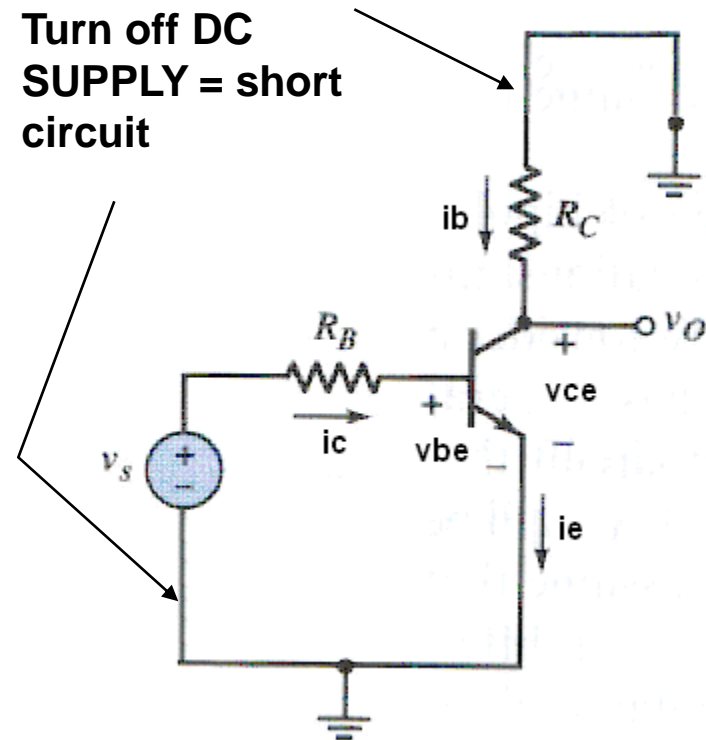


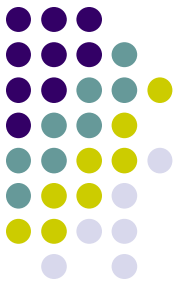


DO YOU STILL REMEMBER?

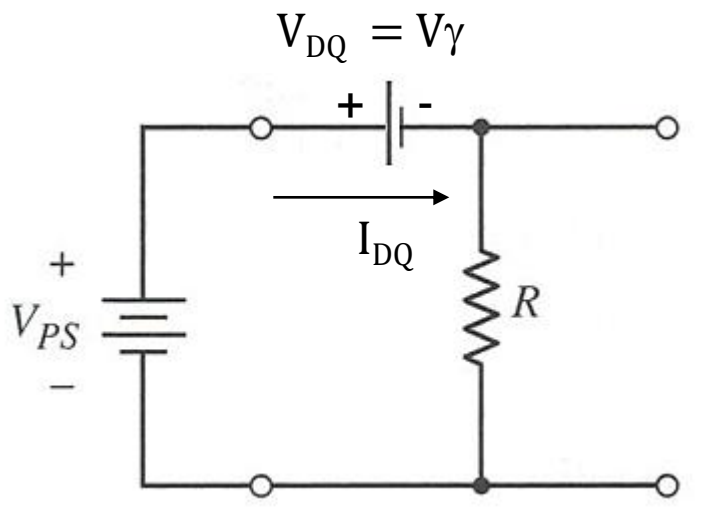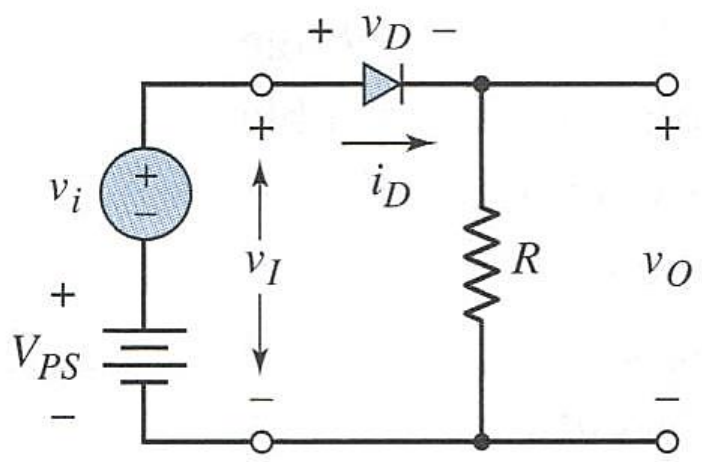


DC equivalent

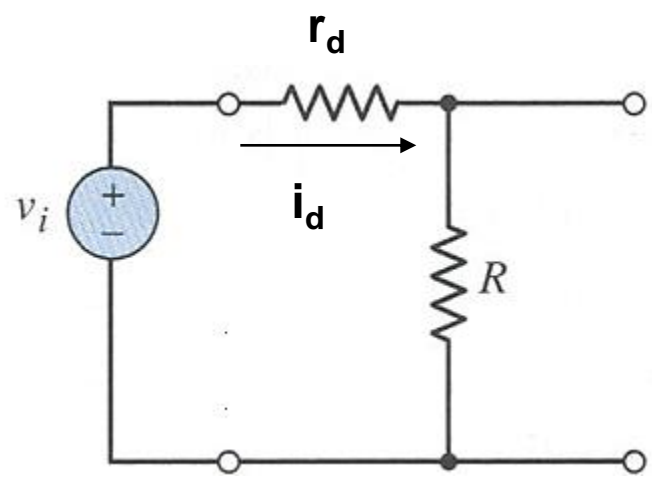




AC equivalent

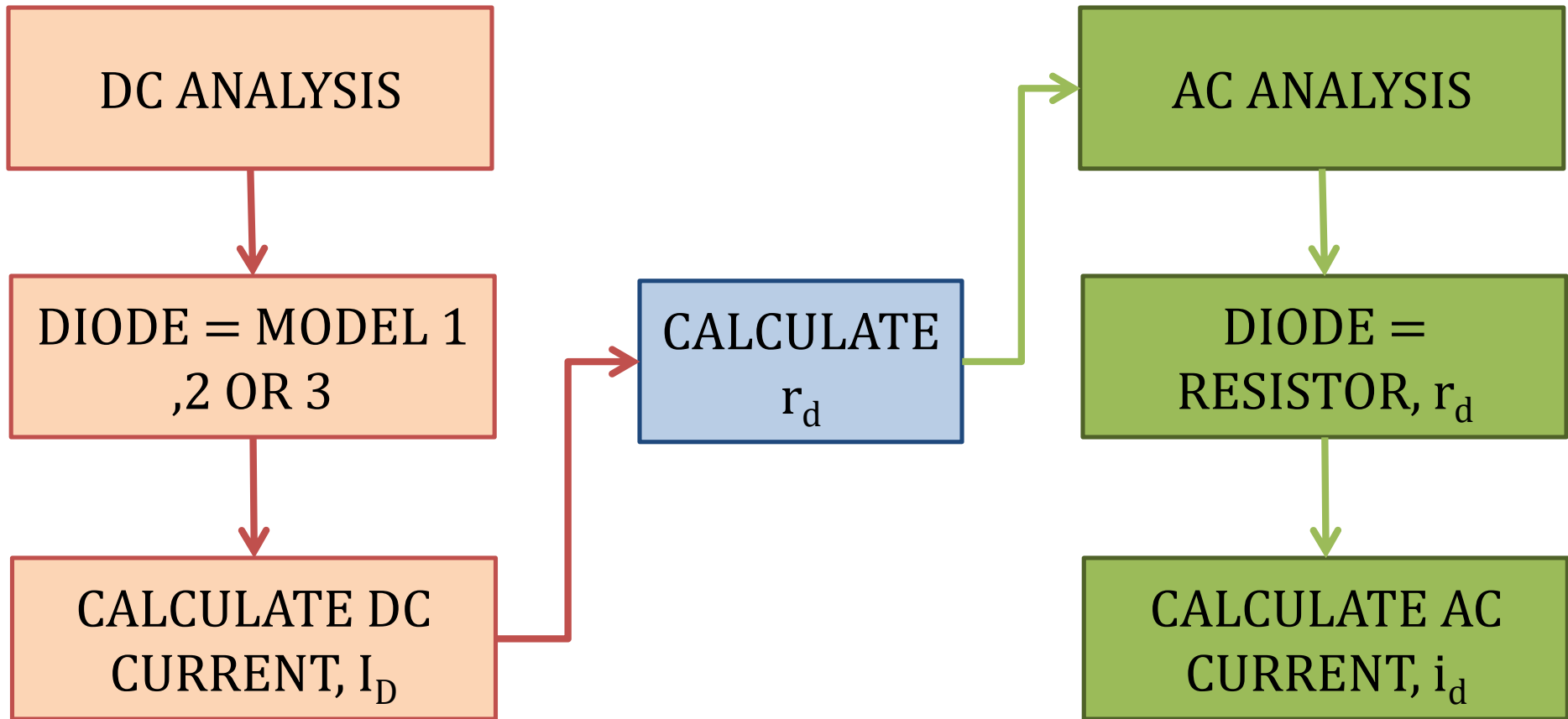

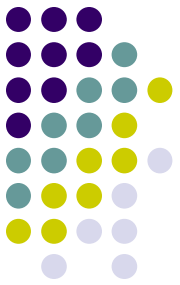


WHAT ABOUT BJT?

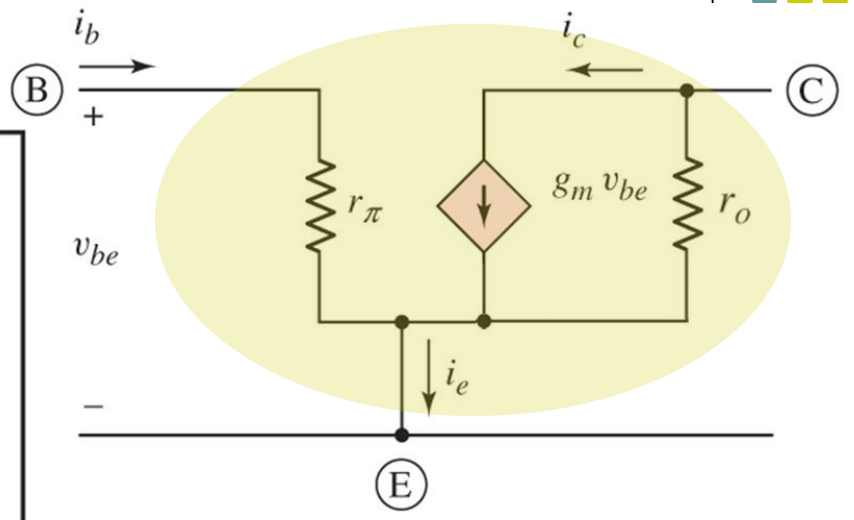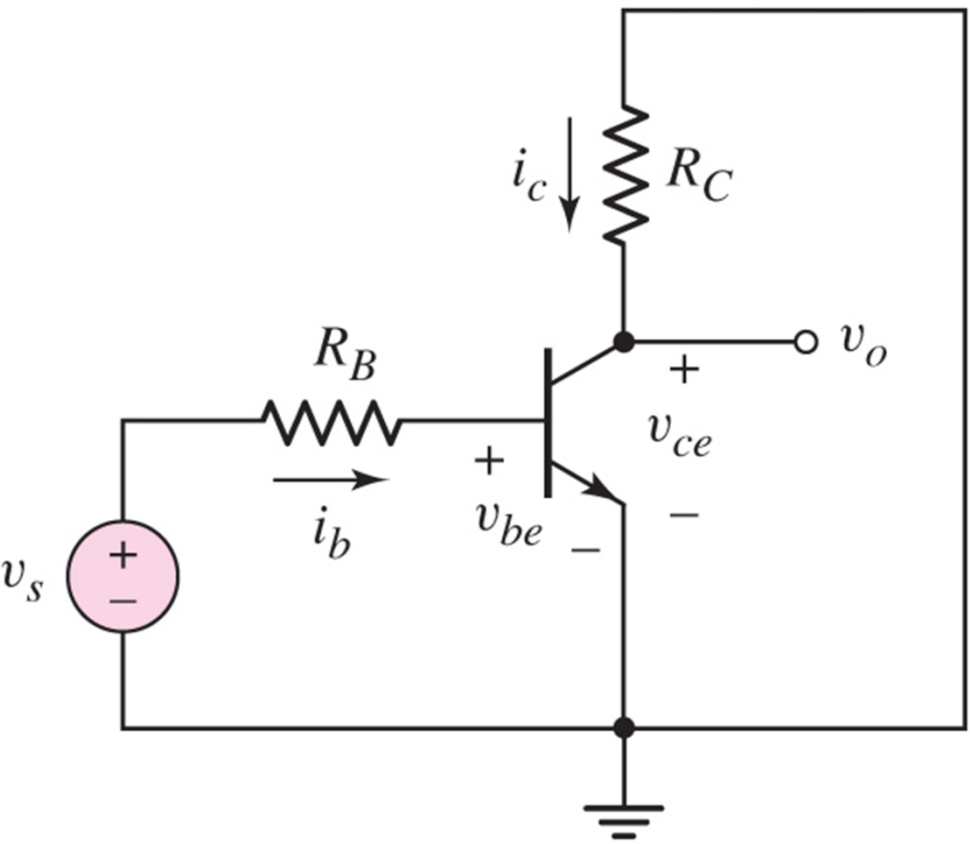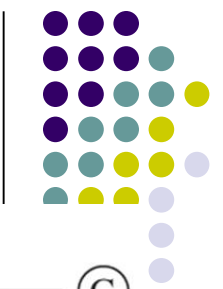
AC equivalent circuit – Small-Signal Hybrid- π Equivalent



OR

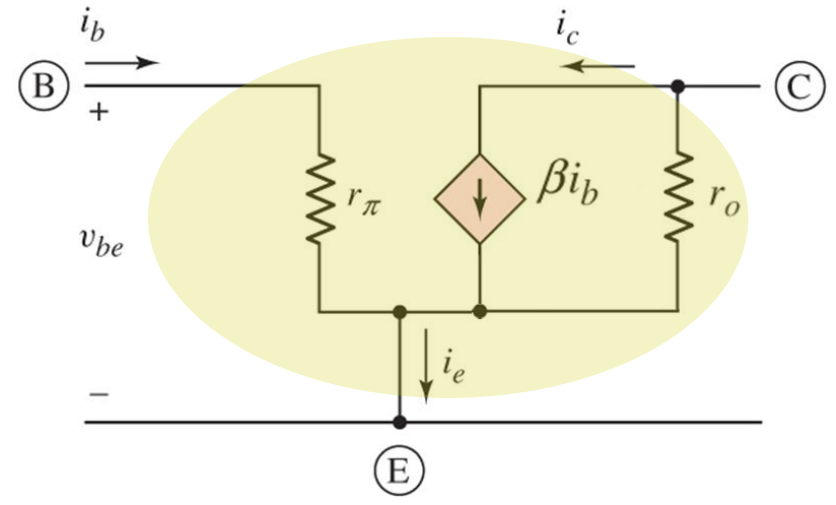

THE SMALL SIGNAL PARAMETERS

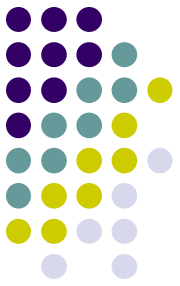

$$r_{\pi} = \frac{V_T}{I_{BQ}} = \frac{\beta V_T}{I_{CQ}}$$

The resistance r_{π} is called **diffusion resistance** or **B-E input resistance**. It is connected between Base and Emitter terminals

$$g_m = \frac{I_{CQ}}{V_T}$$

The term g_m is called a transconductance


$$r_o = V_A / I_{CQ}$$

r_o = small signal transistor output resistance


V_A is normally equals to ∞ , hence, if that is the case, $r_o = \infty \rightarrow$ open circuit

Hence from the equation of the AC parameters, we HAVE to perform DC analysis first in order to calculate them.

Characteristics of Common-Emitter - npn

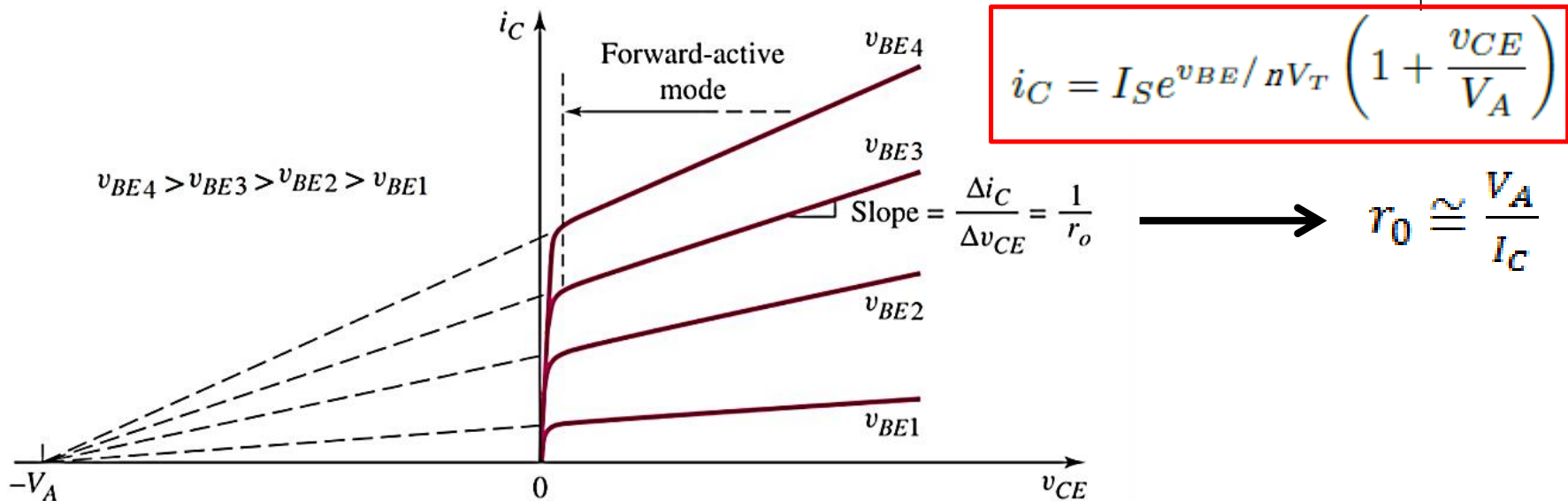

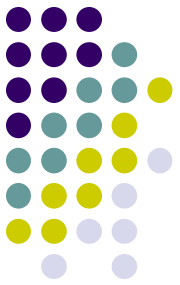I - V characteristic of common-emitter BJT circuit, showing Early voltage and the finite output resistance, of the transistor



EXAMPLE

- The transistor parameters are $\beta = 125$ and $V_A = 200\text{V}$. A value of $g_m = 200\text{ mA/V}$ is desired. Determine the collector current, I_{CQ} and then find r_π and r_o

ANSWERS: $I_{CQ} = 5.2\text{ mA}$, $r_\pi = 0.625\text{ k}\Omega$ and $r_o = 38.5\text{ k}\Omega$