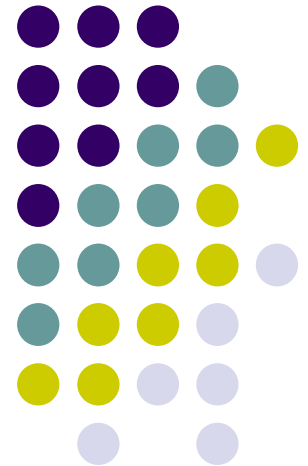




DC Analysis of BJT Circuit and Load Lines





- DC analysis of BJT
 - BE Loop
 - CE Loop
 - When node voltages are known, branch current equations can be used.


KVL

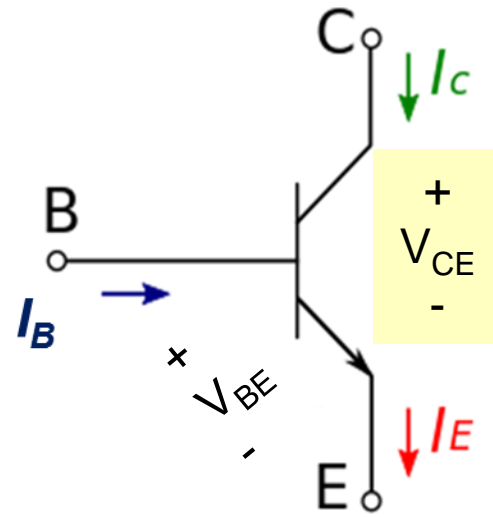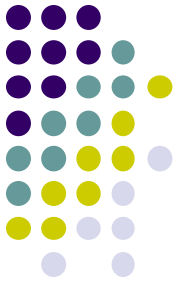



Common-Emitter Circuit

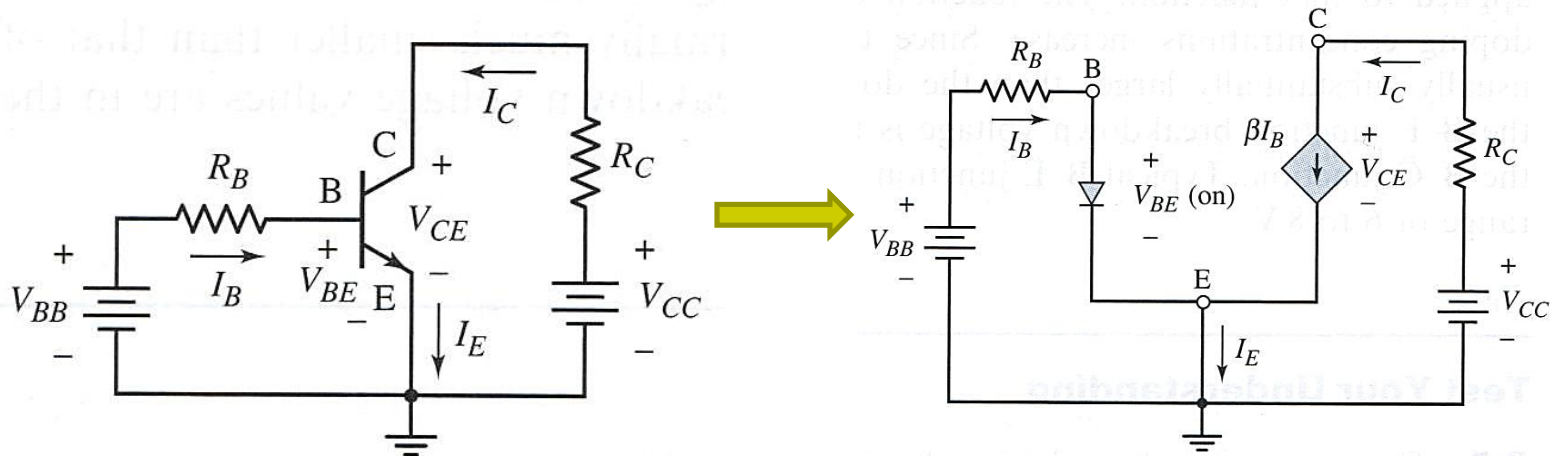- The figures below is showing a common-emitter circuit with an npn transistor and the DC equivalent circuit.




- Assume that the B-E junction is forward biased, so the voltage drop across that junction is the cut-in or turn-on voltage $V_{BE}(\text{on})$.

**Unless given , always
assume $V_{BE} = 0.7V$**



➤ KVL at B-E loop

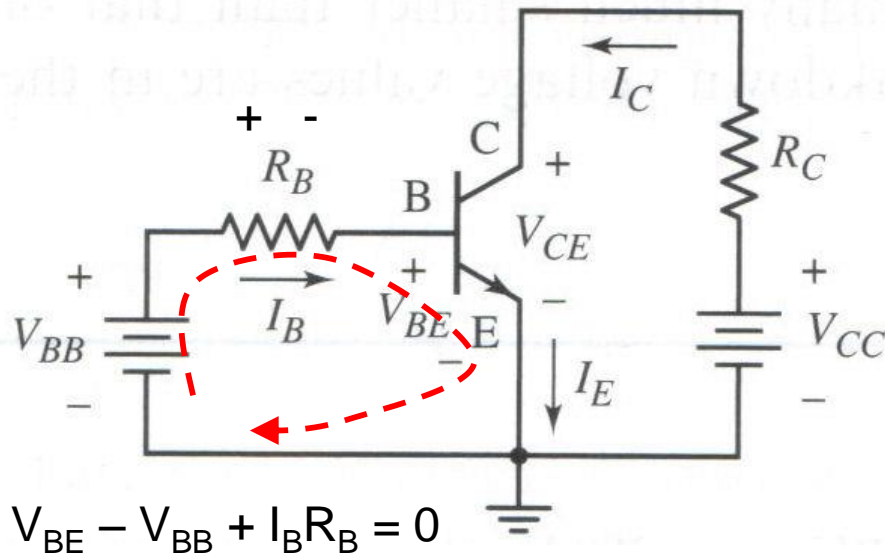


$$I_B = \frac{V_{BB} - V_{BE(on)}}{R_B}$$

You can calculate I_C using $I_C = \beta I_B$


Calculate I_E using $I_E = I_B + I_C$

Input Load Line

I_B versus V_{BE}

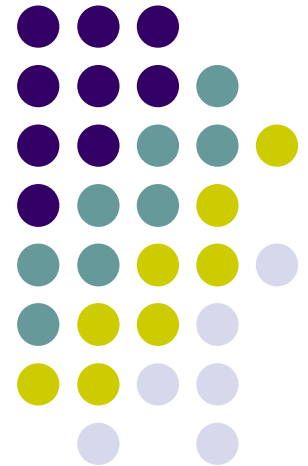

Input Load Line – I_B versus V_{BE}

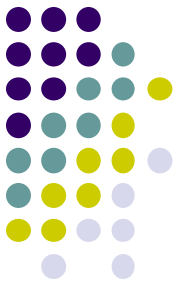

Derived using B-E loop


- The input load line is obtained from Kirchhoff's voltage law equation around the B-E loop, written as follows:

$$V_{BE} - V_{BB} + I_B R_B = 0$$

$$I_B = -\frac{V_{BE}}{R_B} + \frac{V_{BB}}{R_B}$$

$$y = mx + c$$

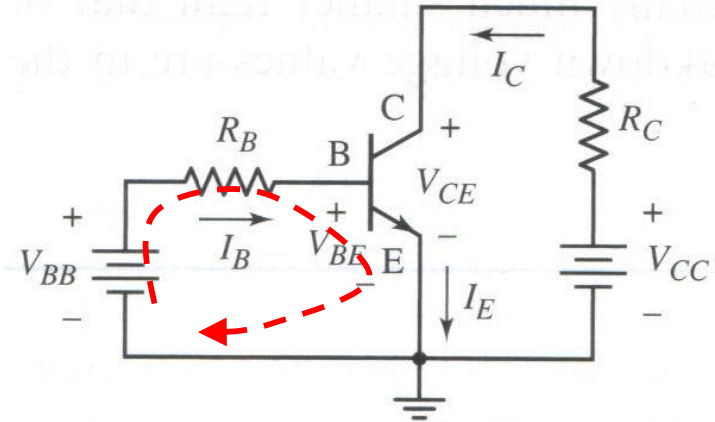- Both the load line and the quiescent base current change as either or both V_{BB} and R_B change.







For example;

- The input load line is essentially the same as the load line characteristics for diode circuits.

$$V_{BE} - 4 + I_B(220k) = 0$$

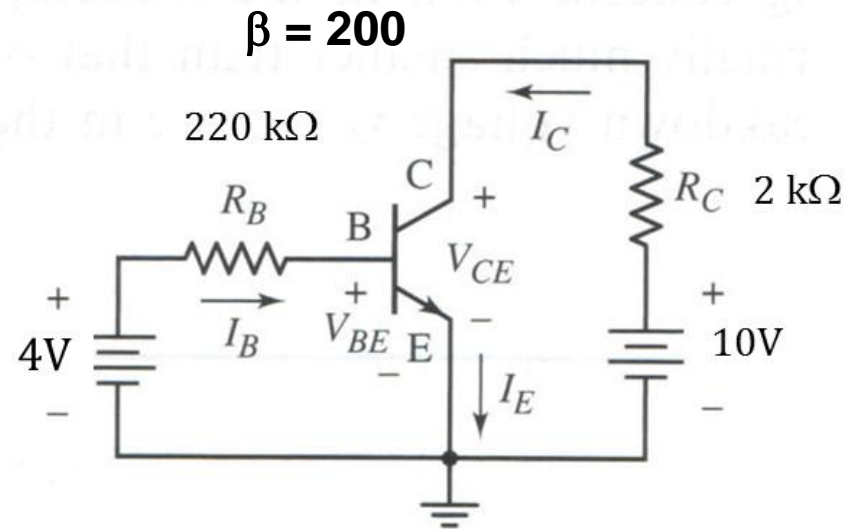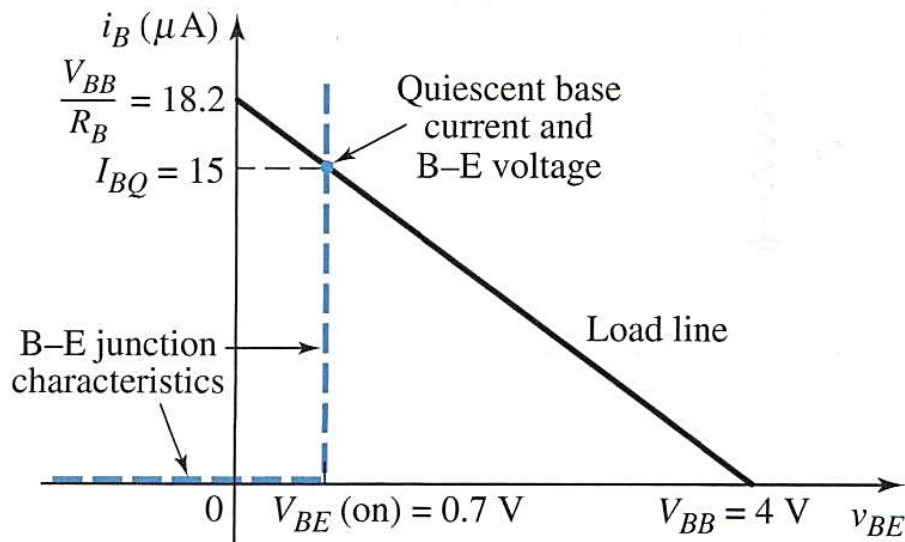


$$I_B = \frac{-V_{BE}}{220k} + \frac{4}{220k}$$

$$y = mx + c$$

➤ $I_{BQ} = 15 \mu A$



➤ KVL at C-E loop of the circuit

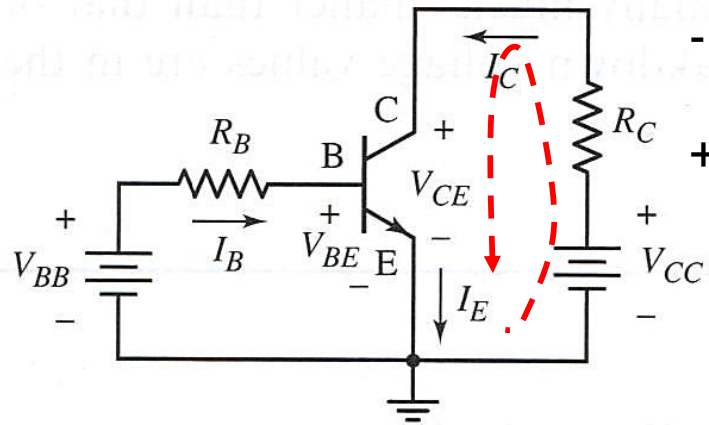


You have calculated the value of I_C from the value of I_B

$$V_{CE} - V_{CC} + I_C R_C = 0$$

$$V_{CE} = V_{CC} - I_C R_C$$


Output Load Line

I_C versus V_{CE}

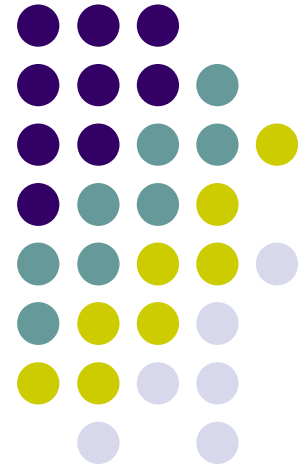

Output Load Line – I_C versus V_{CE}

Derived using C-E loop

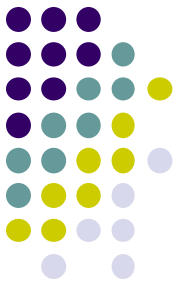



- For the C-E portion of the circuit, the load line is found **by writing Kirchhoff's voltage law around the C-E loop**. We obtain:

$$V_{CE} = V_{CC} - I_C R_C$$

$$I_C = -\frac{V_{CE}}{R_C} + \frac{V_{CC}}{R_C}$$

$$y = mx + c$$

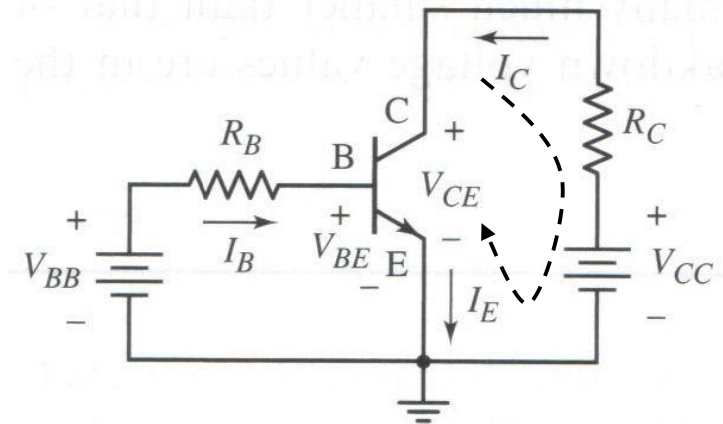

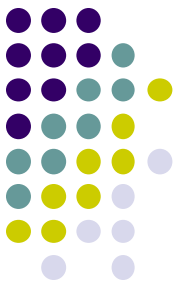


For example;


$$I_C = \frac{-V_{CE}}{2k} + \frac{10}{2k}$$

$$y = mx + c$$

$$\beta = 200$$

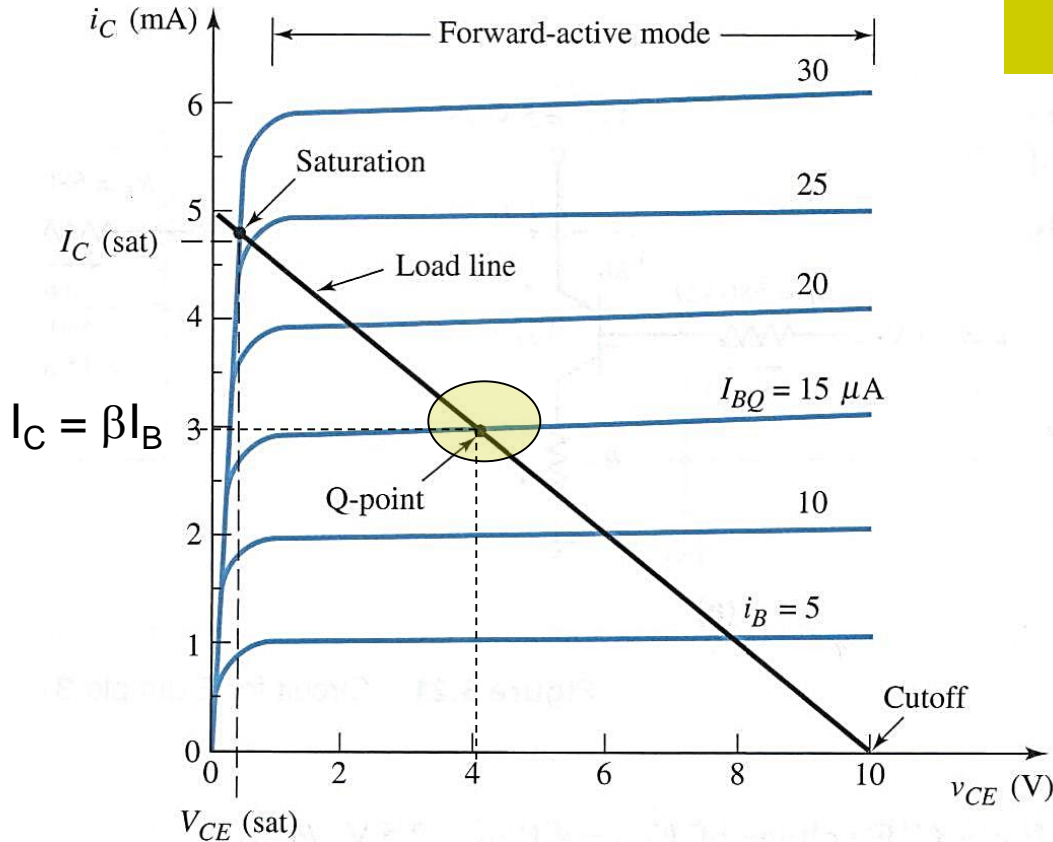

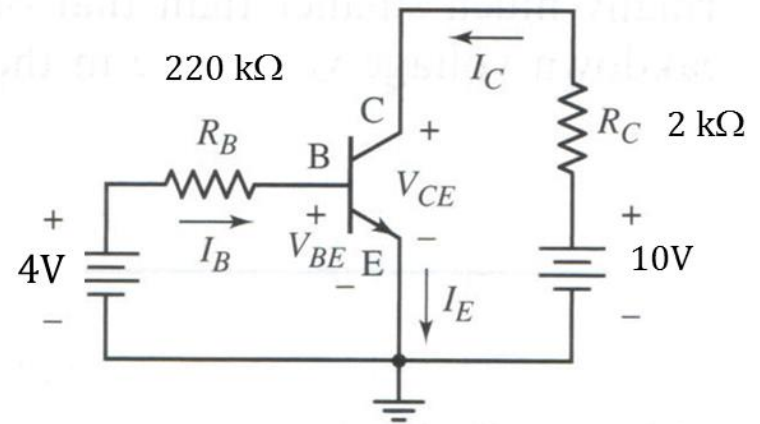
Q-point is the intersection of the **load line** with the i_C vs v_{CE} curve, corresponding to the appropriate base current





- To find the intersection points setting $I_C = 0$, $V_{CE} = V_{CC} = 10 \text{ V}$
- setting $V_{CE} = 0$
 $I_C = V_{CC}/R_C = 5 \text{ mA}$

Examples

BJT DC Analysis

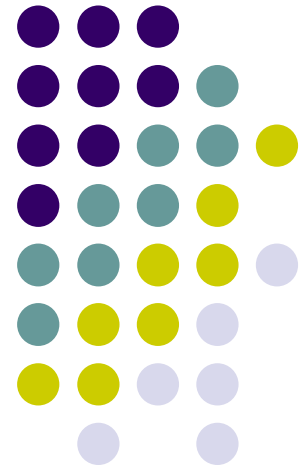

Example 2

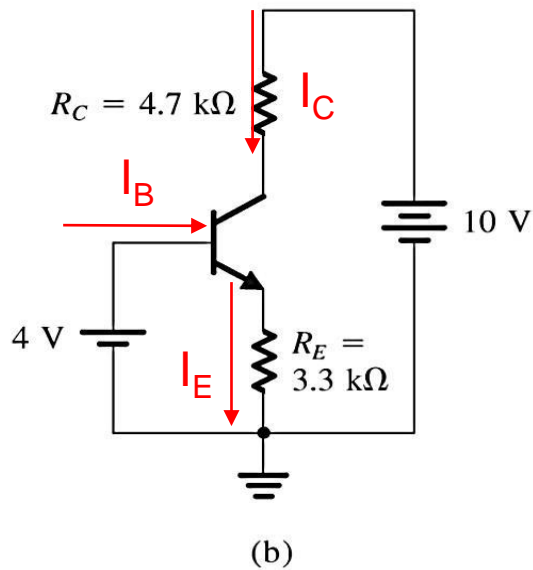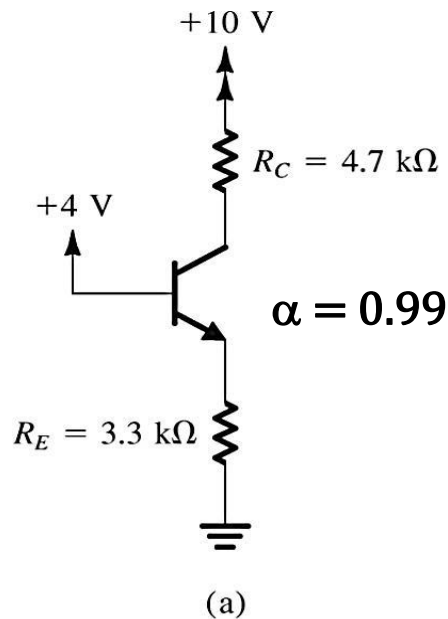



KVL at BE loop: $0.7 + I_E R_E - 4 = 0$
 $I_E = 3.3 / 3.3 = \underline{1 \text{ mA}}$


Hence, $I_C = \alpha I_E = \underline{0.99 \text{ mA}}$

$$I_B = I_E - I_C = \underline{0.01 \text{ mA}}$$

KVL at CE loop: $I_C R_C + V_{CE} + I_E R_E - 10 = 0$
 $V_{CE} = 10 - 3.3 - 4.653 = \underline{2.047 \text{ V}}$



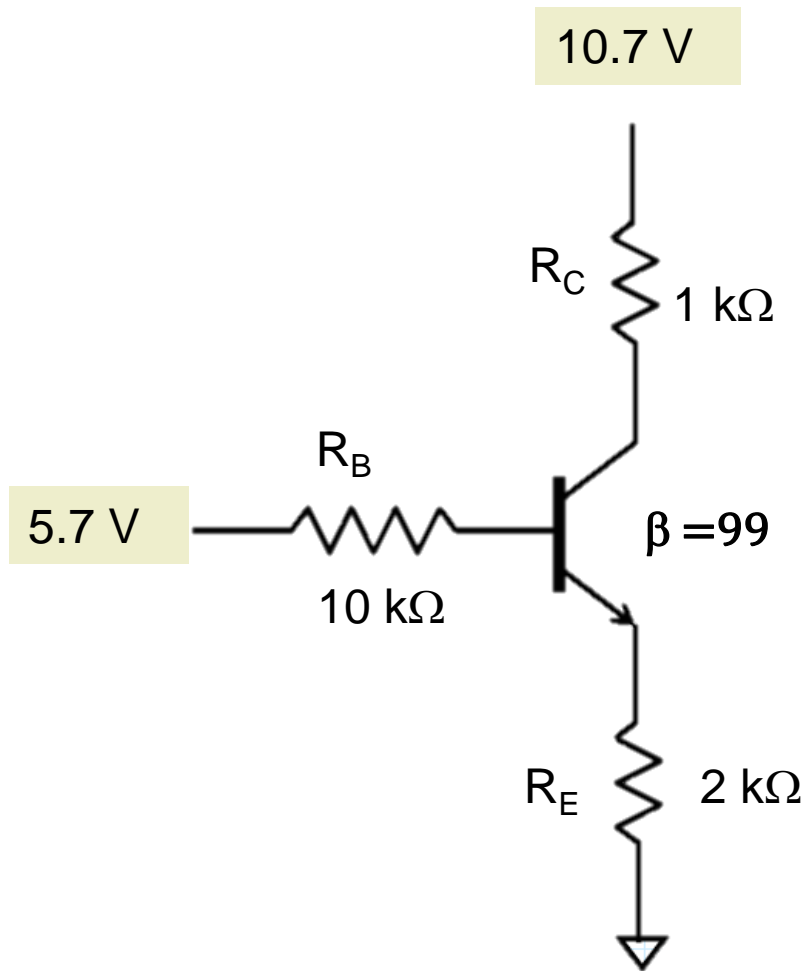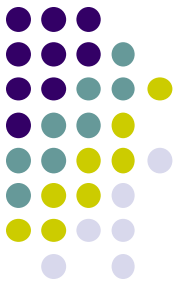


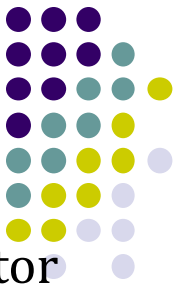


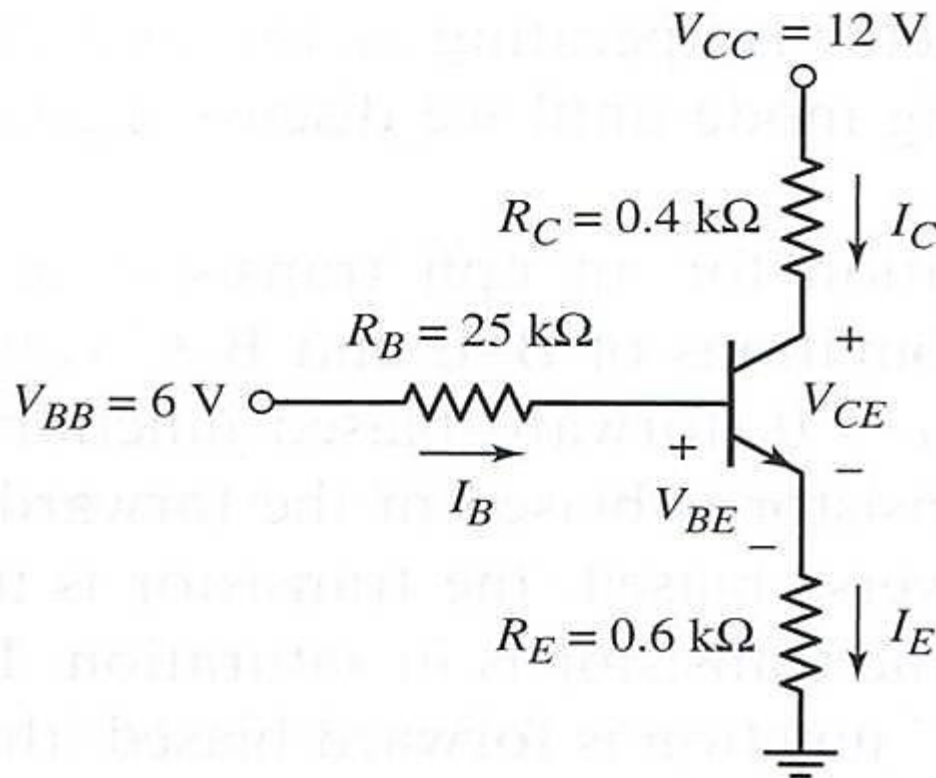Example 3: DC Analysis and Load Line

Calculate the characteristics of a circuit containing an emitter resistor and plot the **output load line**.

For the circuit, let $V_{BE}(\text{on}) = 0.7 \text{ V}$ and $\beta = 75$.



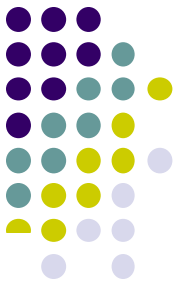

Output Load Line

Use KVL at B-E loop to find the value of I_B

Solution:


Q-Point Values:

Writing the Kirchhoff's voltage law equation around the B-E loop, we have

$$V_{BB} = I_B R_B + V_{BE(\text{on})} + I_E R_E$$

Assuming the transistor is biased in the forward-active mode, we can write $I_E = (1 + \beta)I_B$. We can then solve for the base current:
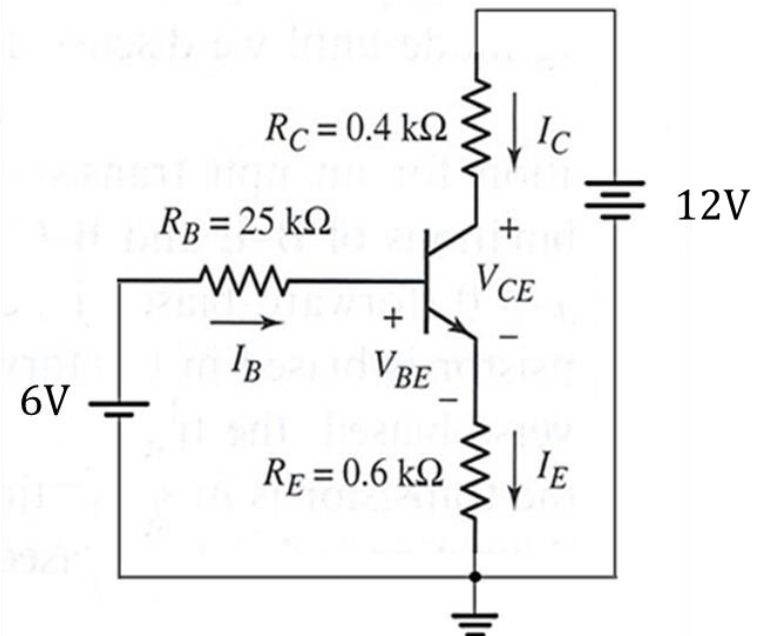
$$I_B = \frac{V_{BB} - V_{BE(\text{on})}}{R_B + (1 + \beta)R_E} = \frac{6 - 0.7}{25 + (76)(0.6)} \Rightarrow 75.1 \mu\text{A}$$





Use KVL at C-E loop – to obtain the linear equation


$$I_C R_C + V_{CE} + I_E R_E - 12 = 0$$

$$I_C R_C + V_{CE} + (I_C/\alpha) R_E - 12 = 0$$

$$V_{CE} = V_{CC} - I_C \left[R_C + \left(\frac{1+\beta}{\beta} \right) R_E \right] = 12 - I_C \left[0.4 + \left(\frac{76}{75} \right) (0.6) \right]$$

or

$$V_{CE} = 12 - I_C(1.01)$$

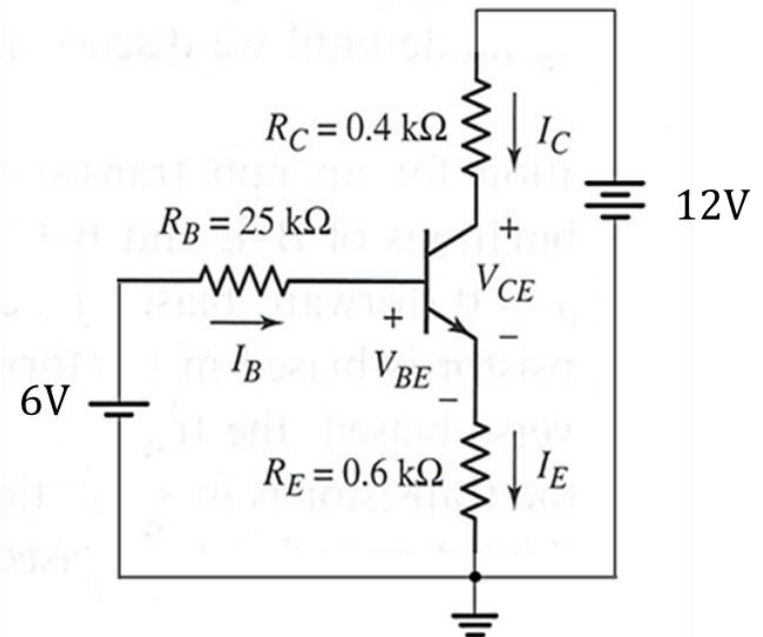



$$V_{CE} = 12 - I_C (1.01)$$
$$I_C = \frac{-V_{CE} + 12}{1.01}$$

