Chapter 4 Bipolar Junction Transistor

# **REMEMBER THIS**

Current flow in the **<u>opposite direction</u>** of the electrons flow; same direction as holes



## **Transistor Structures**

- The bipolar junction transistor (BJT) has three separately doped regions and contains two pn junctions.
- Bipolar transistor is a 3-terminal device.
  - Emitter (E)
  - Base (B)
  - Collector (C)



- The basic transistor principle is that the voltage between two terminals controls the current through the third terminal.
- Current in the transistor is due to the flow of both electrons and holes, hence the name **bipolar**.

# **3 Regions of Operation**

> Active

Operating range of the amplifier. Base-Emitter Junction forward biased. Collector-Base Junction reverse biased

#### Cutoff

The amplifier is basically off. There is voltage but little current. Both junctions reverse biased

#### Saturation

The amplifier is full on. There is little voltage but lots of current. Both junctions forward biased



Е

в

## **OPERATIONS - npn**

#### FORWARD ACTIVE MODE

- The base-emitter (B-E) junction is forward biased and the basecollector (C-B) junction is reverse-biased,.
- Since the B-E junction is forward biased, electrons from the emitter are injected across the B-E junction into the base  $\rightarrow I_E$
- ➢ Once in the base region, the electrons are quickly accelerated through the base due to the reverse-biased C-B region →  $I_C$



Some electrons, in passing through the base region, recombine with majority carrier holes in the base. This produces the current  $\rightarrow I_B$ 



### MATHEMATICAL EXPRESSIONS



### $I_E = I_S [e^{VBE/VT} - 1] = I_S e^{VBE/VT}$

### Based on KCL: $I_E = I_C + I_B$

No. of electrons crossing the base region and then directly into the collector region is a constant factor  $\beta$  of the no. of electrons exiting the base region  $I_{C} = \beta I_{B}$ 

No. of electrons reaching the collector region is directly proportional to the no. of electrons injected or crossing the base region.

$$I_{\rm C} = \alpha I_{\rm E}$$

Ideally  $\alpha = 1$ , but in reality it is between 0.9 and 0.998.

Based on KCL:  $I_E = I_C + I_B$   $I_C = \beta I_B$   $I_C = \alpha I_E$ 

$$I_{E} = \beta I_{B} + I_{B} = I_{B}(\beta + 1) \implies I_{E} = I_{B}(\beta + 1)$$

### Now With $I_C = \beta I_B \rightarrow I_B = I_C / \beta$ Hence, $I_E = [I_C / \beta] (\beta + 1)$ $I_C = I_E [\beta / \beta + 1]$

Comparing with  $I_C = \alpha I_E$   $\longrightarrow$   $\alpha = [\beta / \beta + 1]$ 



#### **EXAMPLE**

Calculate the collector and emitter currents, given the base current and current gain. Assume a common-base current gain,  $\alpha=0.97$  and a base current of  $i_B=25~\mu A$ . Also assume that the transistor is biased forward in the forward active mode.

**Solution:** The common-emitter current gain is  $\beta = \frac{\alpha}{1-\alpha} = \frac{0.97}{1-0.97} = 32.33$ 

The collector current is  $i_C = \beta i_B = 32.33 \times 25 = 808.25 \ \mu A$ 

And the emitter current is  $i_E = i_B + i_C = 25 + 808.25 = 833.25 \ \mu\text{A}$ 

## Examples

- EXAMPLE 1
- Given  $I_B = 6.0 \mu A$  and  $I_C = 510 \mu A$ . Determine  $\beta$ ,  $\alpha$  and  $I_E$

Answers:  $\beta = \underline{85}$   $\alpha = \underline{0.9884}$  $I_E = \underline{516 \ \mu A}$ 

- EXAMPLE 2
- NPN Transistor
- Reverse saturation current Is =  $10^{-13}$ A with current gain,  $\beta = 90$ .
- Based on  $V_{BE} = 0.685V$ , determine  $I_C$ ,  $I_B$  and  $I_E$

Answers:  $I_E = 10^{-13} (e^{0.685/0.026}) = \underline{0.0277 A}$   $I_C = (90/91)(0.0277) = \underline{0.0274 A}$  $I_B = I_E - I_C = \underline{0.3 mA}$  BJT: Current-Voltage Characteristic I<sub>C</sub> versus V<sub>CE</sub>

### **Characteristics of Common-Emitter - npn**



*I-V* characteristic of common-emitter BJT circuit, showing Early voltage and the finite output resistance, of the transistor

