
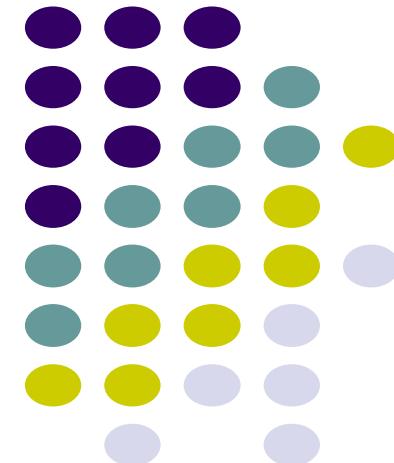


CALCULATION OF GAIN

Voltage Gain = v_o / v_s


Current Gain = i_o / i_s

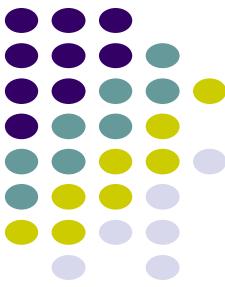





- 3 configurations of BJT Amplifiers
 - Common Emitter
 - Common Collector
 - Common Base

Common-Emitter Amplifier

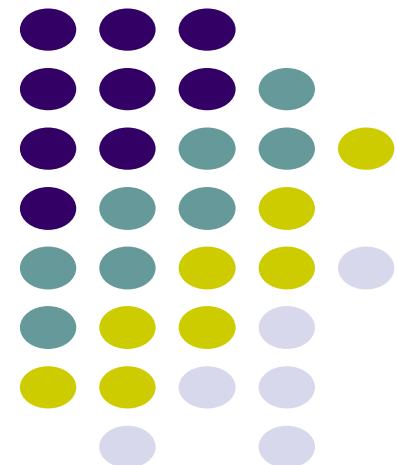


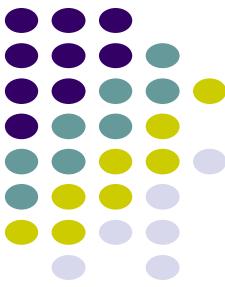

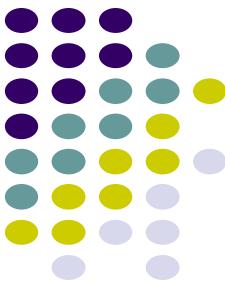- Remember that for **Common Emitter Amplifier**,
 - the **output** is measured at the **collector terminal**.
 - the **gain** is a **negative value**
- Three types of common emitter
 - **Emitter grounded**
 - With R_E
 - With bypass capacitor C_E



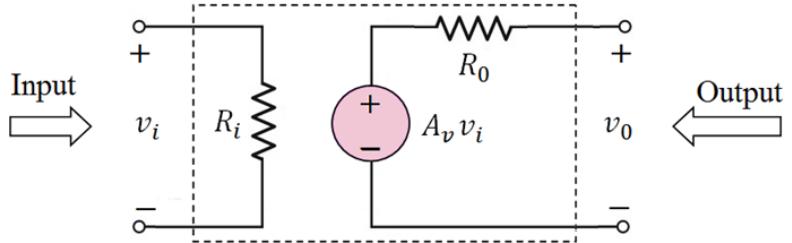STEPS TO OBTAIN VOLTAGE AMPLIFIER COMPONENTS




Equivalent circuit of a voltage amplifier

OUTPUT SIDE


1. Get the equivalent resistance at the output side, R_O
2. Get the v_o equation where $v_o = - g_m v_{be} R_O$

INPUT SIDE

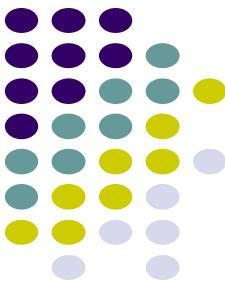3. Calculate R_i
4. Get v_{be} in terms of v_i
5. Get the open circuit voltage gain



Emitter Grounded

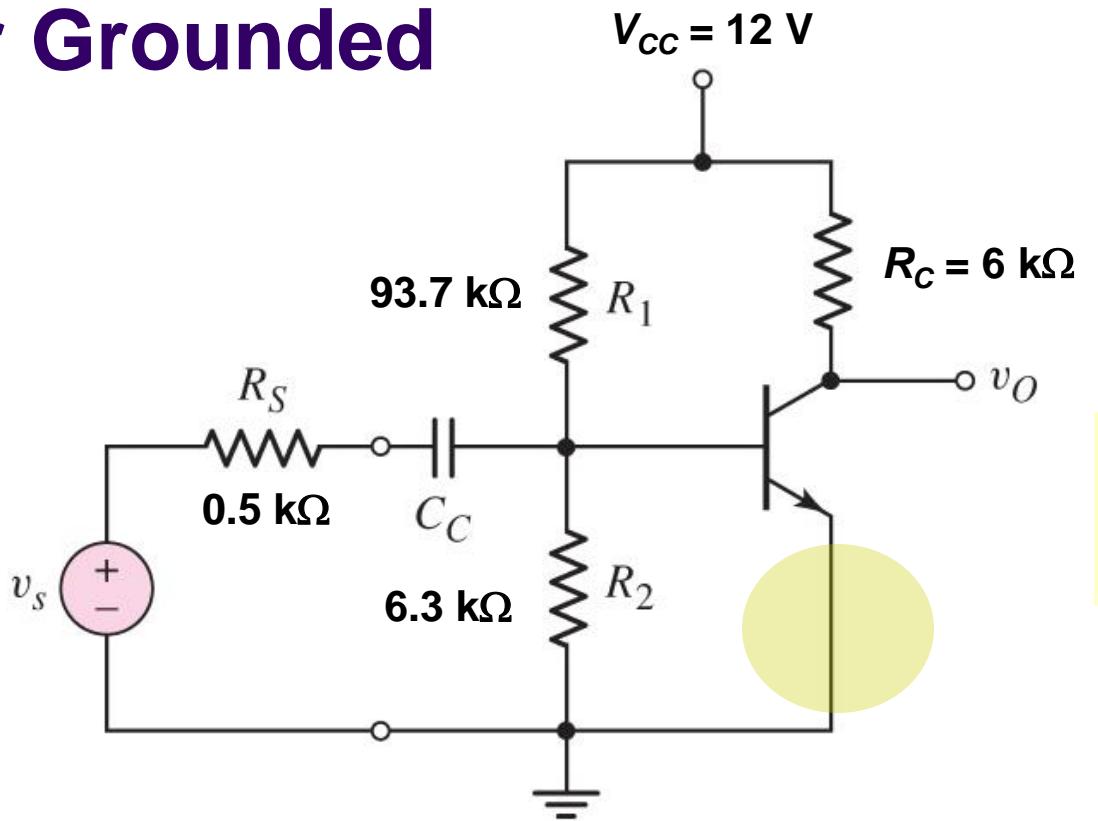


Voltage Divider biasing:

Change to Thevenin Equivalent

$$R_{TH} = 5.9 \text{ k}\Omega$$

$$V_{TH} = 0.756 \text{ V}$$

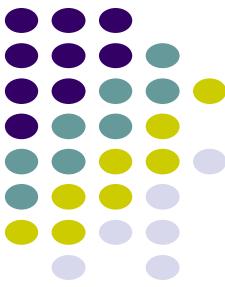

- Perform DC analysis to obtain the value of I_C


$$\text{BE loop: } 5.9I_B + 0.7 - 0.756 = 0$$

$$I_B = 0.00949$$

$$I_C = \beta I_B = 0.949 \text{ mA}$$




- Calculate the small-signal parameters

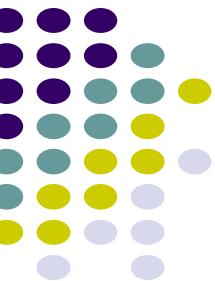
$$r_\pi = 2.74 \text{ k}\Omega, r_o = 105.37 \text{ k}\Omega \text{ and } g_m = 36.5 \text{ mA/V}$$



Emitter Grounded
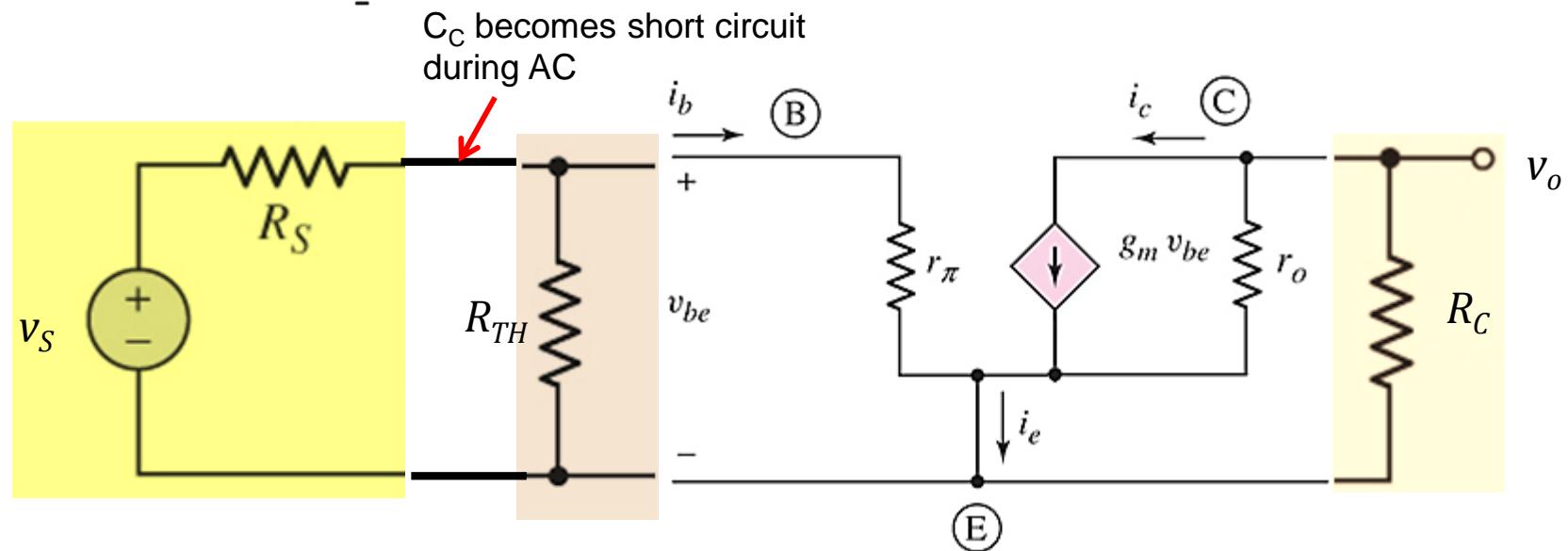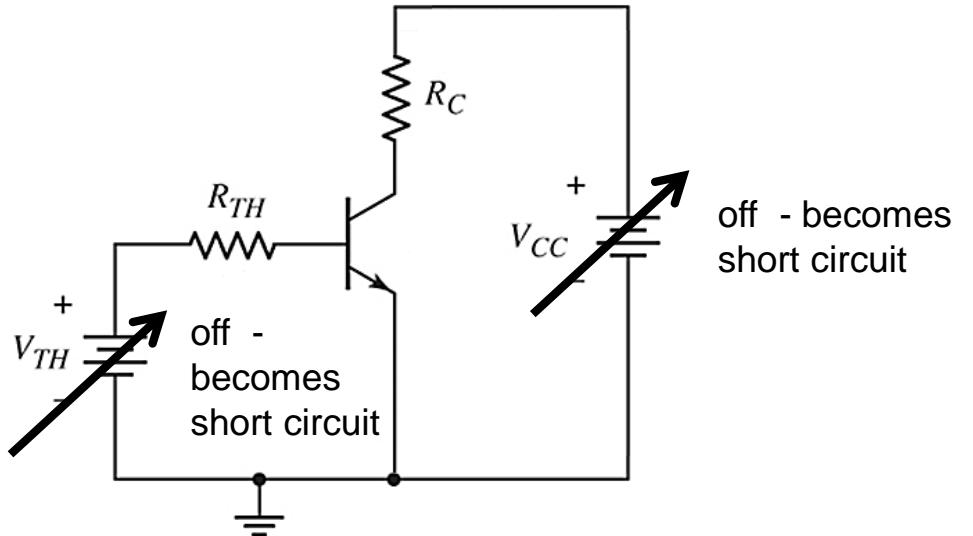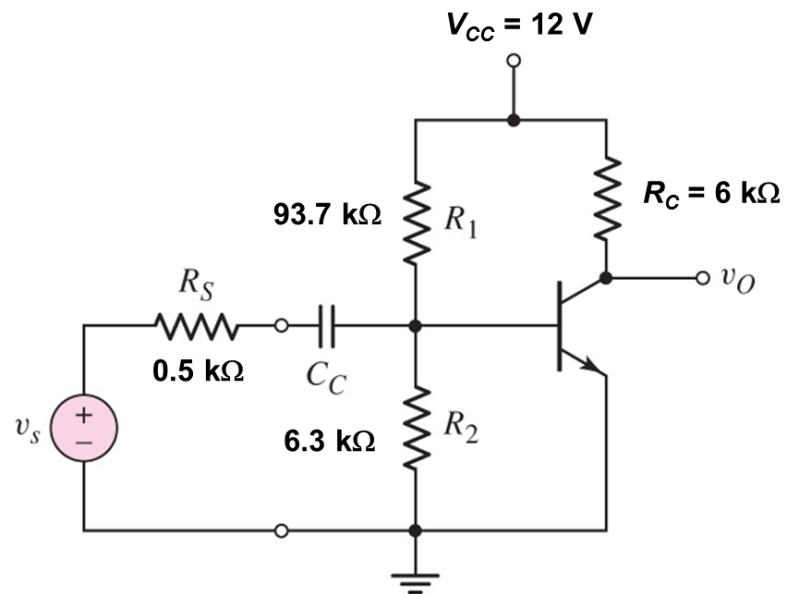
$$\begin{aligned}\beta &= 100 \\ V_{BE} &= 0.7V \\ V_A &= 100 V\end{aligned}$$



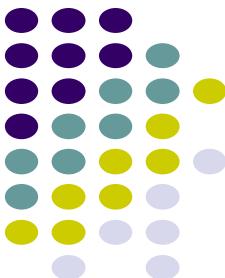


1. $R_o = r_o \parallel R_C$

2. Equation of v_o : $v_o = - (r_o \parallel R_C) g_m v_{be}$

3. Calculate $R_i = R_{TH} \parallel r_\pi$

4. $v_{be} = v_i$


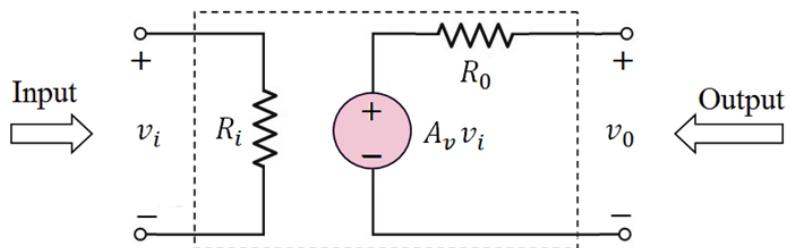


Equivalent circuit of a voltage amplifier

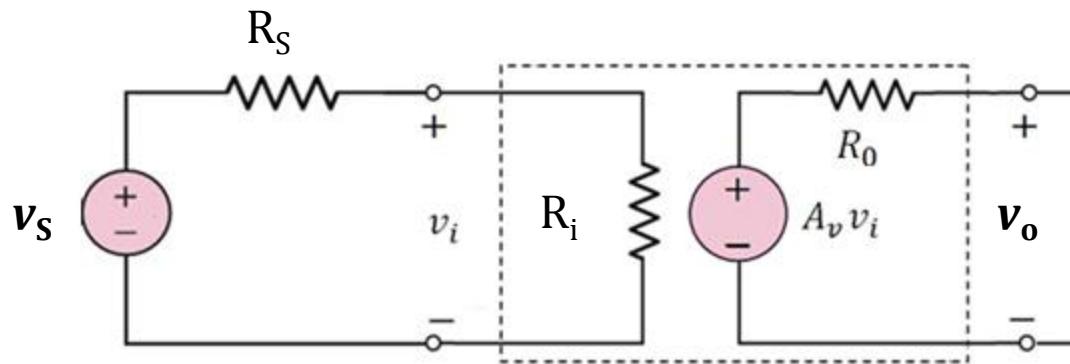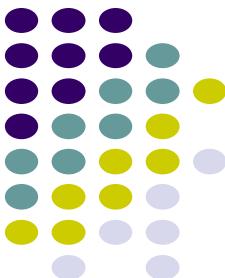5. $A_v v_i = v_o = - (r_o \parallel R_C) g_m v_{be} \leftarrow \text{open circuit voltage}$

$A_v v_i = - (r_o \parallel R_C) g_m v_{be}$ because $v_i = v_{be}$

$A_v = - (r_o \parallel R_C) g_m \leftarrow \text{open circuit voltage gain}$



Equivalent circuit of a voltage amplifier

To find new voltage gain, v_o/v_s with input signal voltage source, v_s



6. v_i in terms of v_s → use voltage divider:

$$v_i = [R_i / (R_i + R_s)] * v_s = \left(\frac{R_{TH} \parallel r_\pi}{(R_{TH} \parallel r_\pi) + R_s} \right) v_s$$

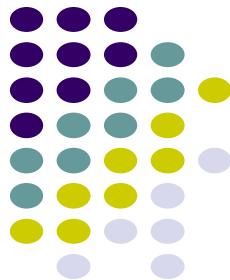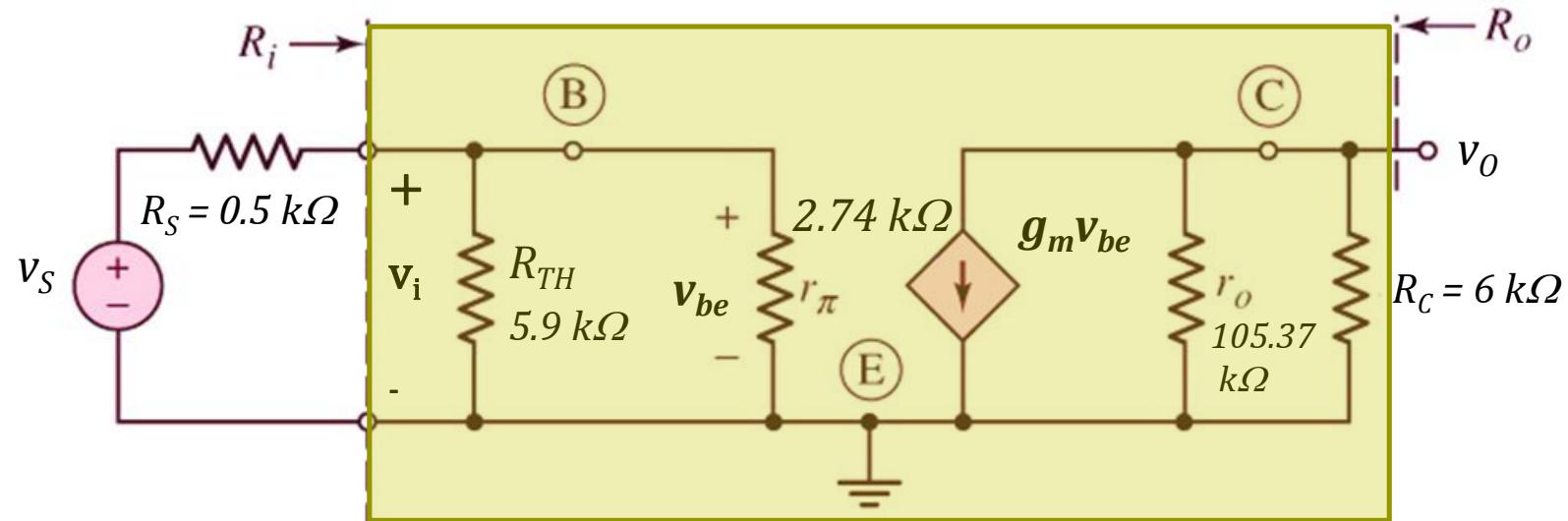7. $v_o = A_v v_i$ ← because there is no load resistor



$$v_o = - (r_o \parallel R_C) g_m \left(\frac{R_{TH} \parallel r_\pi}{(R_{TH} \parallel r_\pi) + R_s} \right) v_s$$

$$v_o/v_s = - (r_o \parallel R_C) g_m \left(\frac{R_{TH} \parallel r_\pi}{(R_{TH} \parallel r_\pi) + R_s} \right)$$



Follow the steps

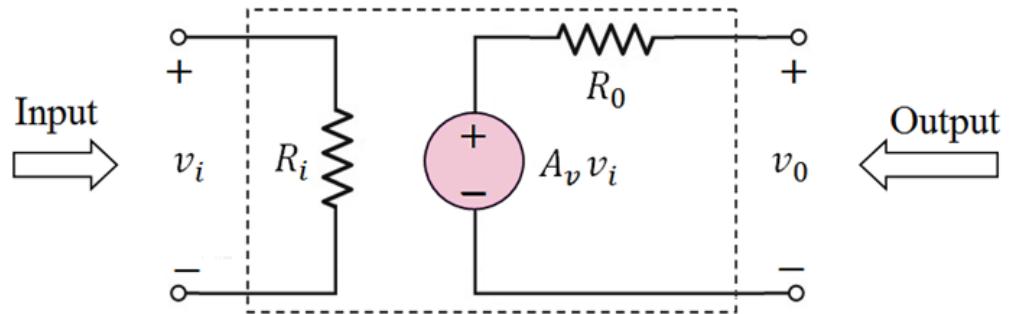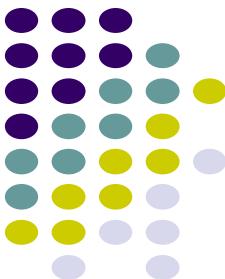1. $R_o = r_o \parallel R_C = 5.677 \text{ k}\Omega$
 2. Equation of v_o : $v_o = - (r_o \parallel R_C) g_m v_{be} = - 36.5 (5.677) v_{be} = -207.21 v_{be}$
-
3. Calculate $R_i \rightarrow R_{TH} \parallel r_\pi = 1.87 \text{ k}\Omega$
 4. $v_{be} = v_i$



Equivalent circuit of a voltage amplifier



Equation of v_o : $v_o = - (r_o \parallel R_C) g_m v_{be} = - 36.5 (5.677) v_{be} = -207.21 v_{be}$

$$v_{be} = v_i$$

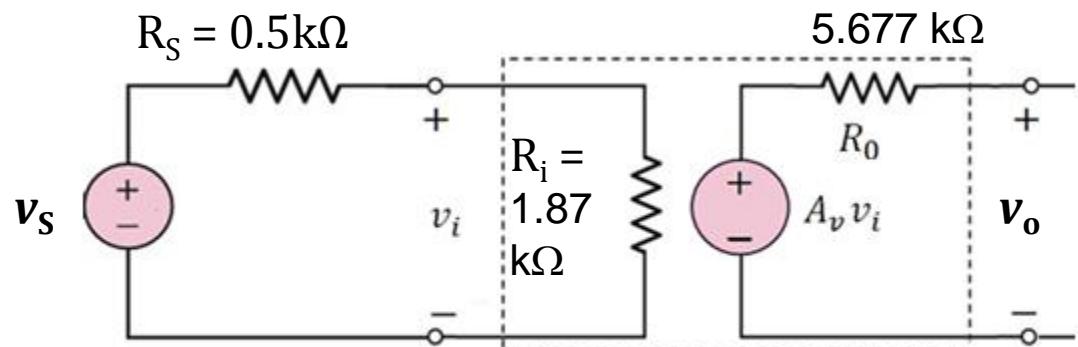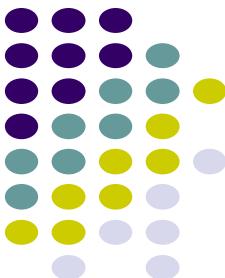5. $A_v v_i = v_o \leftarrow$ open circuit voltage

$$A_v \cancel{v_i} = -207.21 v_{be} = -207.21 \cancel{v_i}$$

$$A_v = -207.21 \leftarrow$$
 open circuit voltage gain



Equivalent circuit of a voltage amplifier

To find new voltage gain, v_o/v_s with input signal voltage source, v_s

6. v_i in terms of v_s → use voltage divider:



$$v_i = [R_i / (R_i + R_s)] * v_s = 0.789 v_s$$


7. $v_o = A_v v_i \leftarrow$ because there is no load resistor

$$v_o = -207.21 (0.789 v_s)$$

$$v_o/v_s = -163.49$$

Example

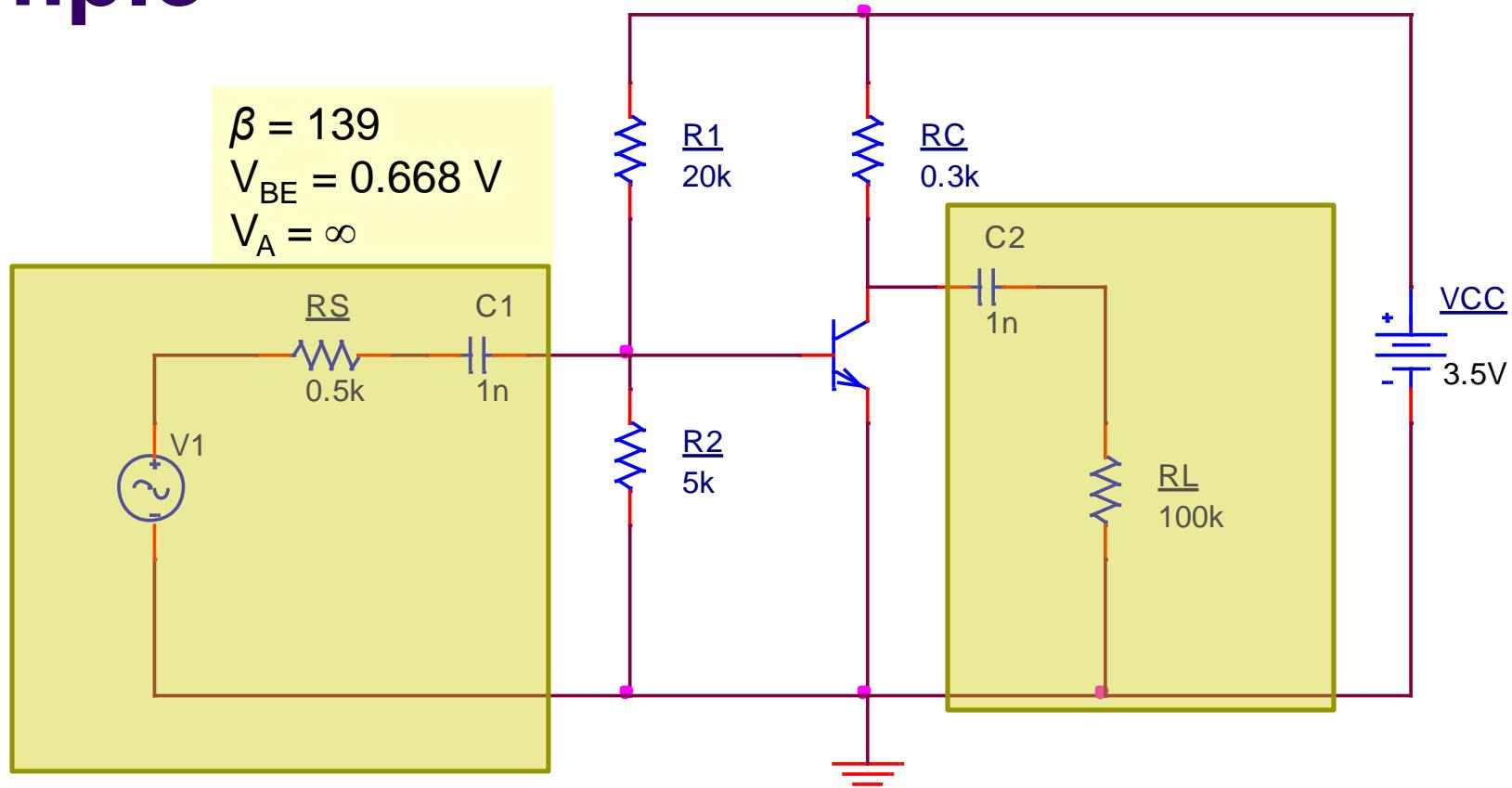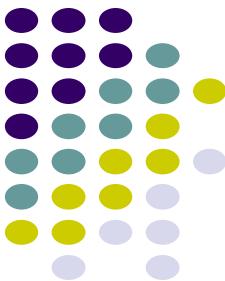

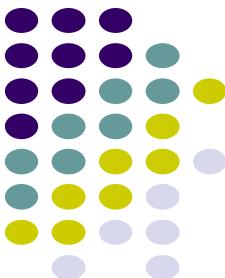

Voltage Divider biasing:

Change to Thevenin Equivalent

$$R_{TH} = 4 \text{ k}\Omega$$

$$V_{TH} = 0.7 \text{ V}$$

$$\beta = 139$$

$$V_{BE} = 0.668 \text{ V}$$

$$V_A = \infty$$

- Perform DC analysis to obtain the value of I_C



$$\text{BE loop: } 4 I_B + 0.668 - 0.7 = 0$$

$$I_B = 0.008$$

$$I_C = \beta I_B = 1.112 \text{ mA}$$

- Calculate the small-signal parameters
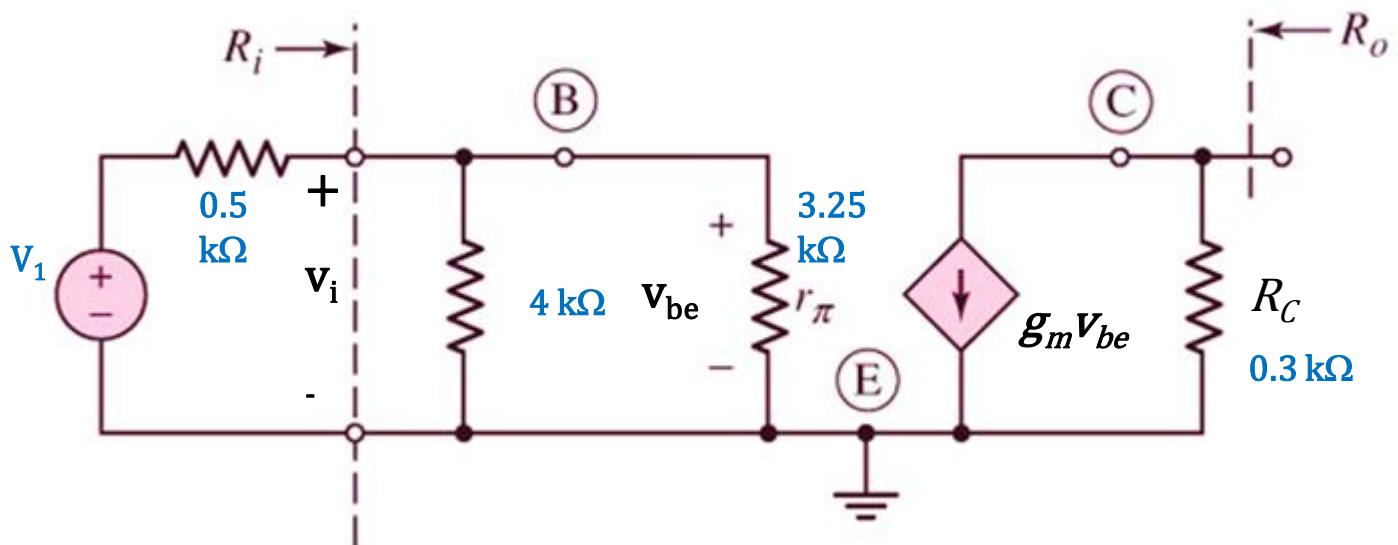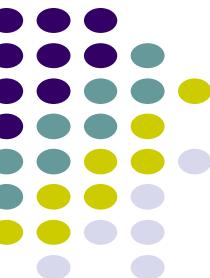
$$r_\pi = 3.25 \text{ k}\Omega, r_o = \infty \text{ and } g_m = 42.77 \text{ mA/V}$$





Follow the steps

1. $R_o = R_C = 0.3 \text{ k}\Omega$

2. Equation of v_o : $v_o = - (R_C) g_m v_{be} = - 0.3 (42.77) v_{be} = -12.831 v_{be}$

3. Calculate $R_i \rightarrow R_{TH} || r_\pi = 4 \parallel 3.25 = 1.793 \text{ k}\Omega$

4. $v_{be} = v_i$

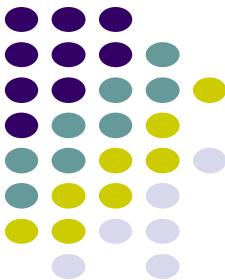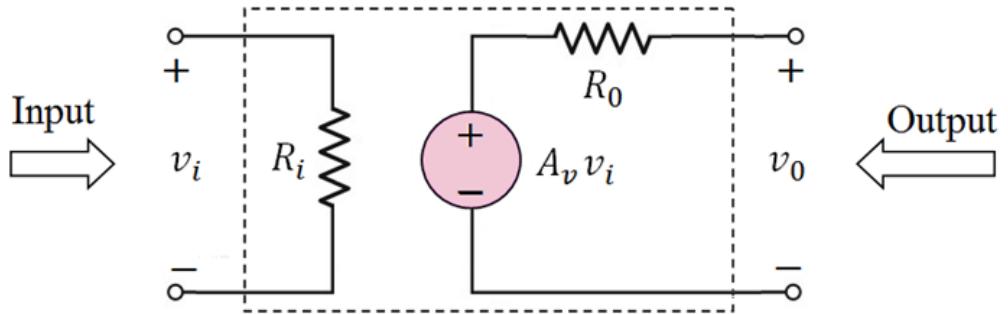

Equivalent circuit of a voltage amplifier



Equation of v_o : $v_o = - (R_C) g_m v_{be} = - 0.3 (42.77) v_{be} = -12.831 v_{be}$

$$v_{be} = v_i$$

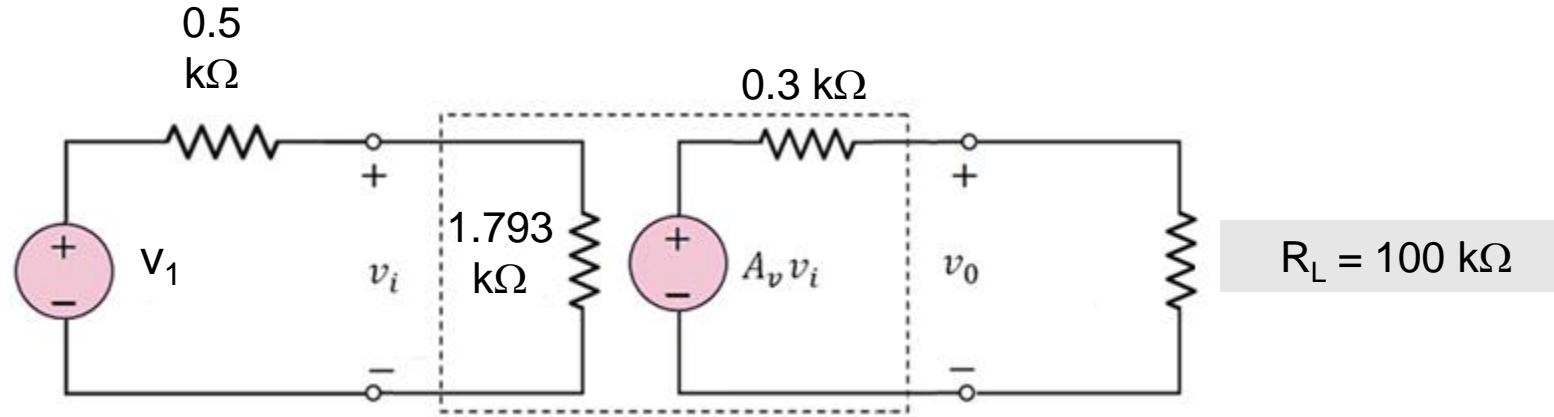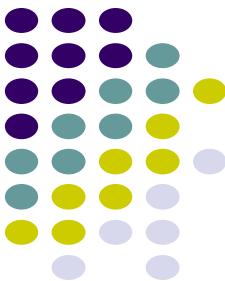5. $A_v v_i = v_o \leftarrow$ open circuit voltage

$$A_v v_i = -12.831 v_{be} = -12.831 v_i$$

$A_v = -12.831 \leftarrow$ open circuit voltage gain



To find new voltage gain, v_o/v_1 now with signal voltage, v_1 and R_L

6. v_i in terms of $v_s \rightarrow$ use voltage divider:

$$v_i = [R_i / (R_i + R_s)] * v_1 = 0.782 v_1$$

7. $v_o = [R_L / (R_L + R_o)] * A_v v_i \leftarrow$ this is because we have load resistor R_L
 $v_o = 0.997 (-12.831) (0.782 v_1)$

$$v_o/v_1 = -10$$