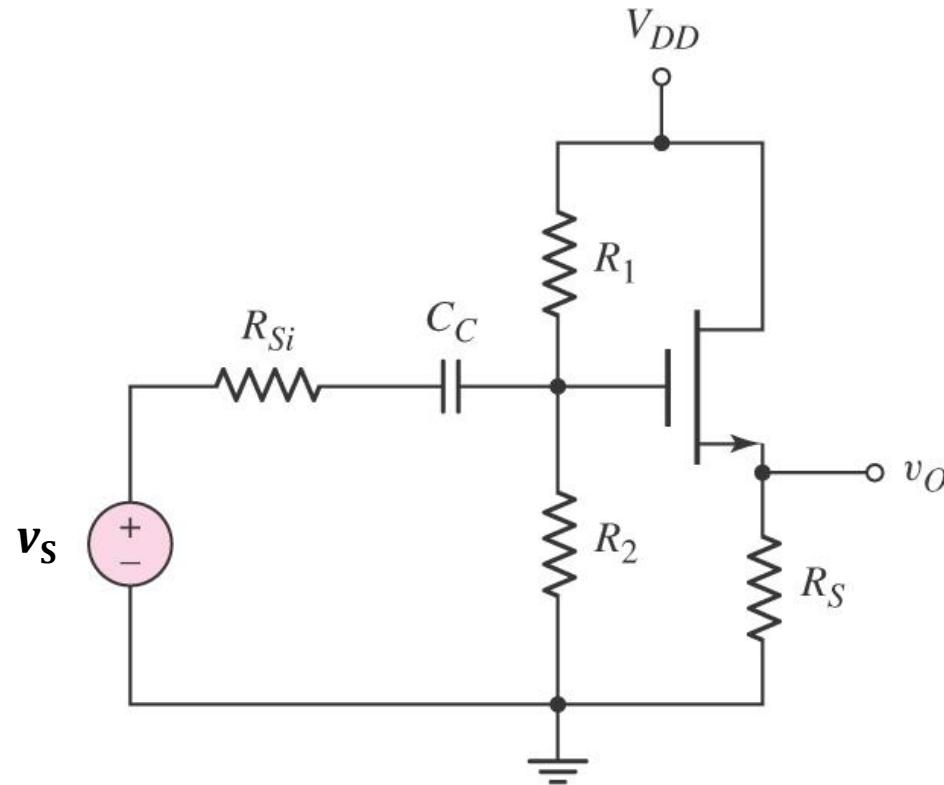


The MOSFET Amplifier - COMMON DRAIN

- The **output** is measured at the **source terminal**
- The gain is **positive value**



COMMON COLLECTOR

OUTPUT SIDE

- Get the equivalent resistance at the output side,

$$R_{eq}$$

- At node x , use KCL and get $i_o = g_m v_{be} + \frac{v_{be}}{r\pi}$


- Get the v_o equation where $v_o = i_o R_{eq}$

INPUT SIDE

- Calculate $R_{ib} = r\pi + (1+\beta) R_{eq}$

- Calculate $R_i = R_{ib} // R_{TH}$

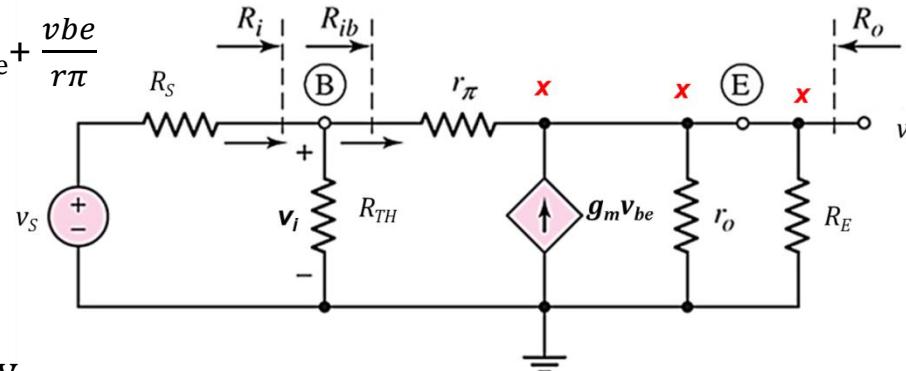- v_{be} in terms of v_i using supermesh, $v_i = v_{be} + v_o$



COMMON DRAIN

OUTPUT SIDE


- Equivalent resistance at the output side, R_{eq}

- Calculate $v_o = g_m v_{gs} R_{eq}$

INPUT SIDE

- Find v_i in terms of v_{gs} using supermesh

$$v_i = v_{gs} + v_o$$

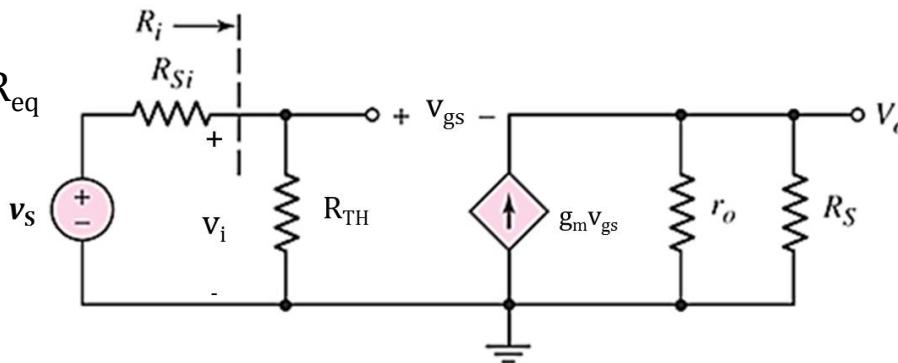

OUTPUT SIDE

1. Equivalent resistance at the output side, $R_{eq} = r_o || R_S$
2. Calculate $v_o = g_m v_{gs} R_{eq} = g_m v_{gs} (r_o || R_S)$

INPUT SIDE


3. Find v_i in terms of v_{gs} using supermesh

$$v_i = v_{gs} + v_o = v_{gs} + g_m v_{gs} (r_o || R_S) = v_{gs} (1 + g_m (r_o || R_S))$$

4. $A_v v_i = v_o = g_m v_{gs} (r_o || R_S) \leftarrow$ open circuit voltage

$$A_v v_i = v_i \left(\frac{g_m (r_o || R_S)}{1 + g_m (r_o || R_S)} \right)$$

$$A_v = \frac{g_m (r_o || R_S)}{1 + g_m (r_o || R_S)} \leftarrow \text{open circuit voltage gain}$$

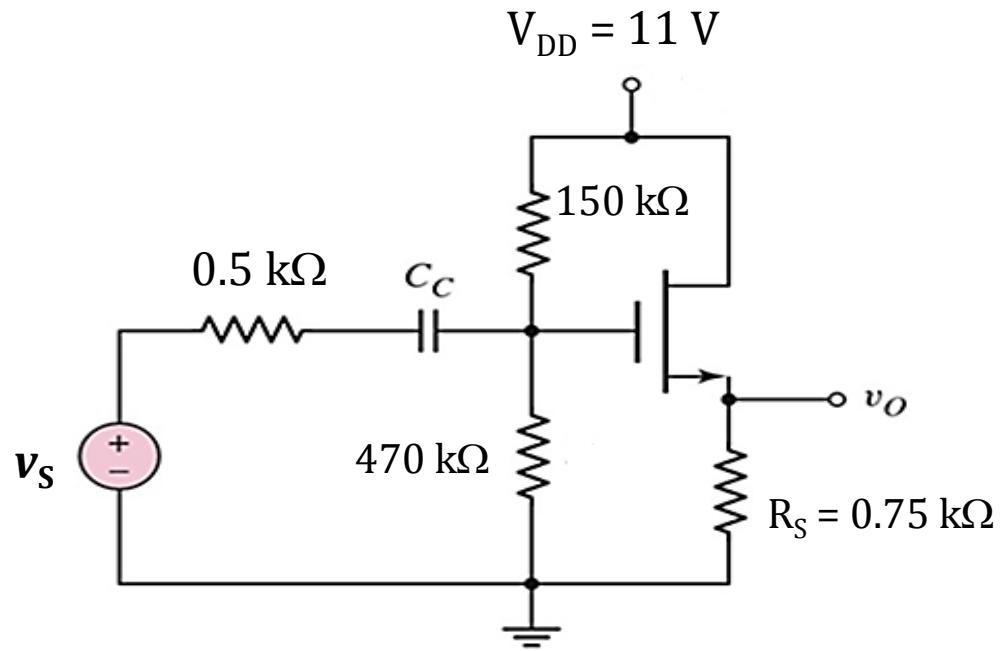

$$V_{TN} = 0.92 \text{ V}, K_n = 4 \text{ mA/V}^2, \lambda = 0.01 \text{ V}^{-1}$$

$$R_{TH} = 113.7 \text{ k}\Omega$$

$$V_{TH} = (470 / 620) \times 11 = 8.34 \text{ V}$$

DC ANALYSIS

- Calculate the value of V_{GS}

KVL at GS loop:

$$0 + V_{GS} + 0.75(I_D) - 8.34 = 0$$

$$V_{GS} = 8.34 - 0.75I_D$$


- Assume the transistor is biased in the saturation region, the drain current:

$$I_D = K_n(V_{GS} - V_{TN})^2$$

$$I_D = 4(8.34 - 0.75I_D - 0.92)^2 = 4(7.42 - 0.75I_D)^2$$

$$I_D = 4(55.06 - 11.13I_D + 0.5625I_D^2)$$

$$2.25I_D^2 - 45.52I_D + 220.24 = 0$$

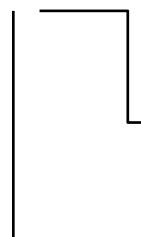

$$\rightarrow I_D = 12.22 \text{ mA}$$

$$\rightarrow I_D = 8 \text{ mA}$$

Replace in V_{GS}
equation in step 1
 $V_{GS} = 2 - 3I_D$

$$\rightarrow V_{GS} = -0.825 \text{ V}$$

$$\rightarrow V_{GS} = 2.34 \text{ V}$$

Why choose $V_{GS} = 2.34 \text{ V}$?
Because it is bigger than V_{TN}



3. Use KVL at DS loop


$$\begin{aligned}V_{DS} + I_D R_S - 11 &= 0 \\V_{DS} &= 5 \text{ V}\end{aligned}$$

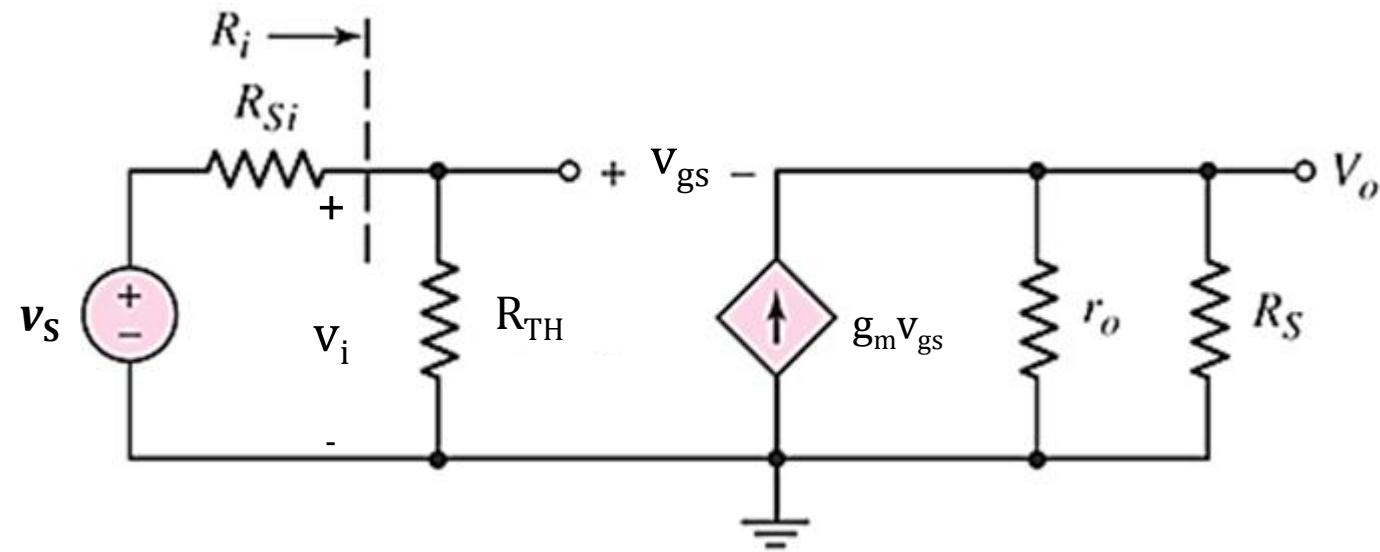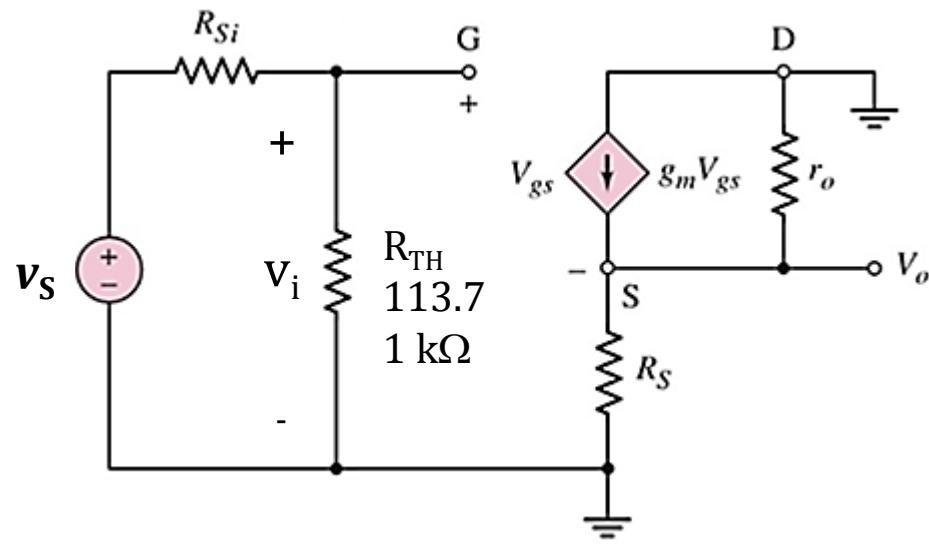4. Calculate $V_{DSsat} = V_{GS} - V_{TN} = 2.34 - 0.92 = 1.42 \text{ V}$
5. Confirm your assumption: $V_{DS} > V_{DSsat}$, our assumption is correct

$$g_m = 2\sqrt{K_n I_{DQ}} \rightarrow g_m = 11.3 \text{ mA/V}$$

$$\lambda = 0.01 \text{ V}^{-1} \rightarrow V_A = 100 \text{ V} \rightarrow r_o = 12.5 \text{ k}\Omega$$




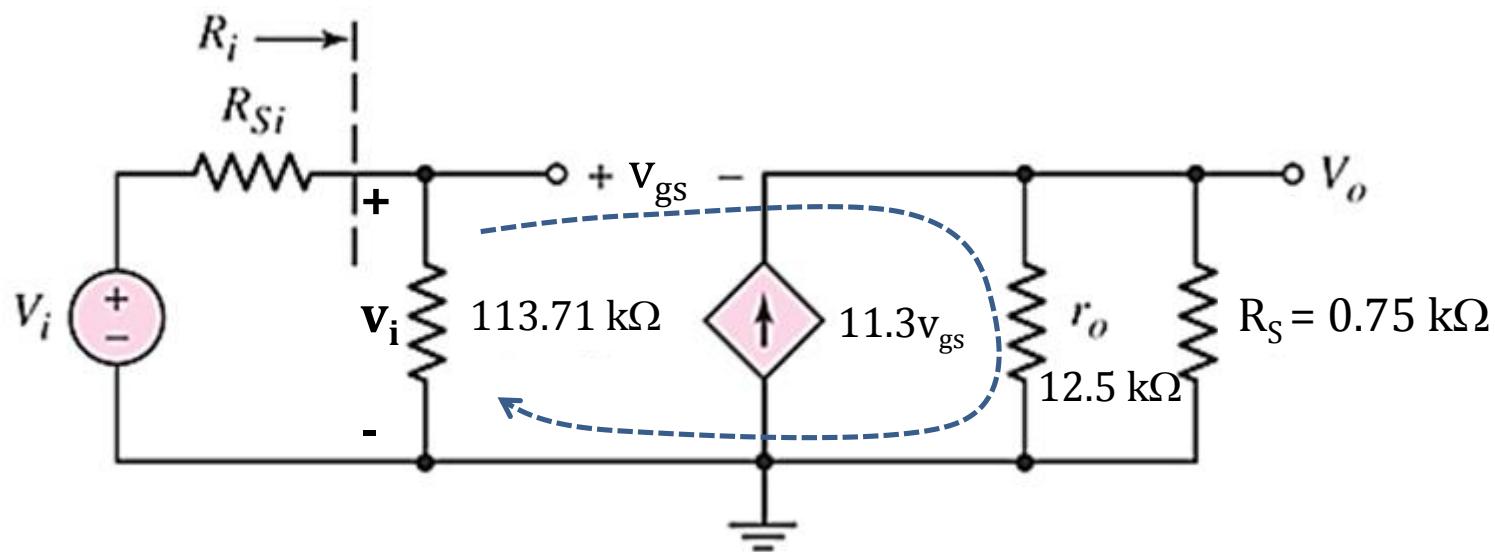

1. The output resistance: $R_{eq} = r_o \parallel R_s = 0.70755 \text{ k}\Omega$
2. The output voltage $v_o = g_m v_{gs} (R_{eq}) = 11.3 v_{gs} (0.70755) = 8 v_{gs}$
3. Find v_i in terms of v_{gs} using supermesh

$$v_i = v_{gs} + v_o$$

$$v_i = v_{gs} + 8 v_{gs} = 9 v_{gs}$$

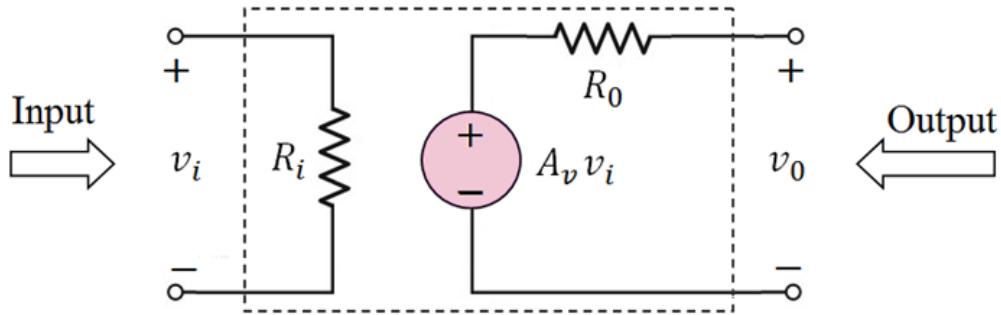

Equivalent circuit of a voltage amplifier


$$\text{Equation of } v_o : v_o = v_o = g_m v_{gs} (R_{eq}) = 11.3 v_{gs} (0.70755) = 8 v_{gs}$$

$$v_i = 9 v_{gs}$$

$$A_v v_i = v_o \leftarrow \text{open circuit voltage}$$

$$A_v v_i = 8 v_{gs} = \frac{8 v_i}{9}$$
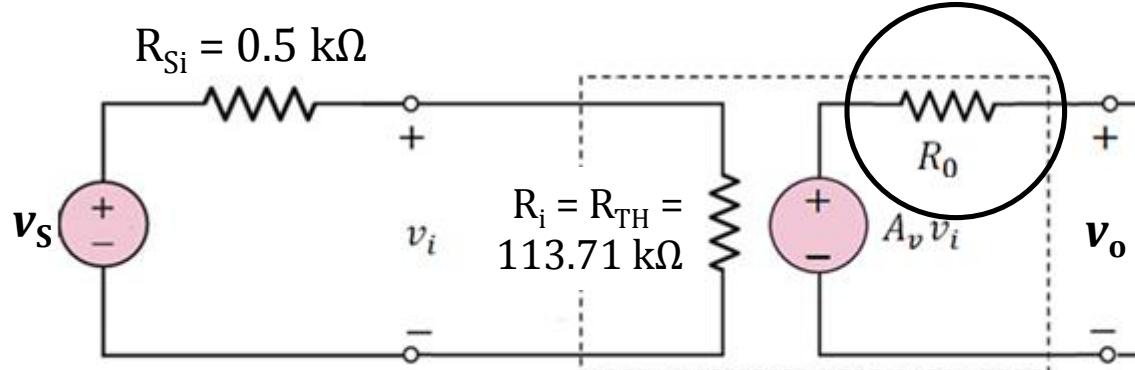
$$A_v = 0.889 \leftarrow \text{open circuit voltage gain}$$



Equivalent circuit of a voltage amplifier

To find new voltage gain, v_o/v_s with input signal voltage source, v_s

v_i in terms of $v_s \rightarrow$ use voltage divider:


$$v_i = [R_i / (R_i + R_s)] * v_s = 0.9956 v_s$$

$$v_o = A_v v_i \leftarrow \text{because there is no load resistor}$$


$$v_o = 0.889 (0.9956 v_s)$$

$$v_o/v_s = 0.885$$

Output Resistance for Common Drain

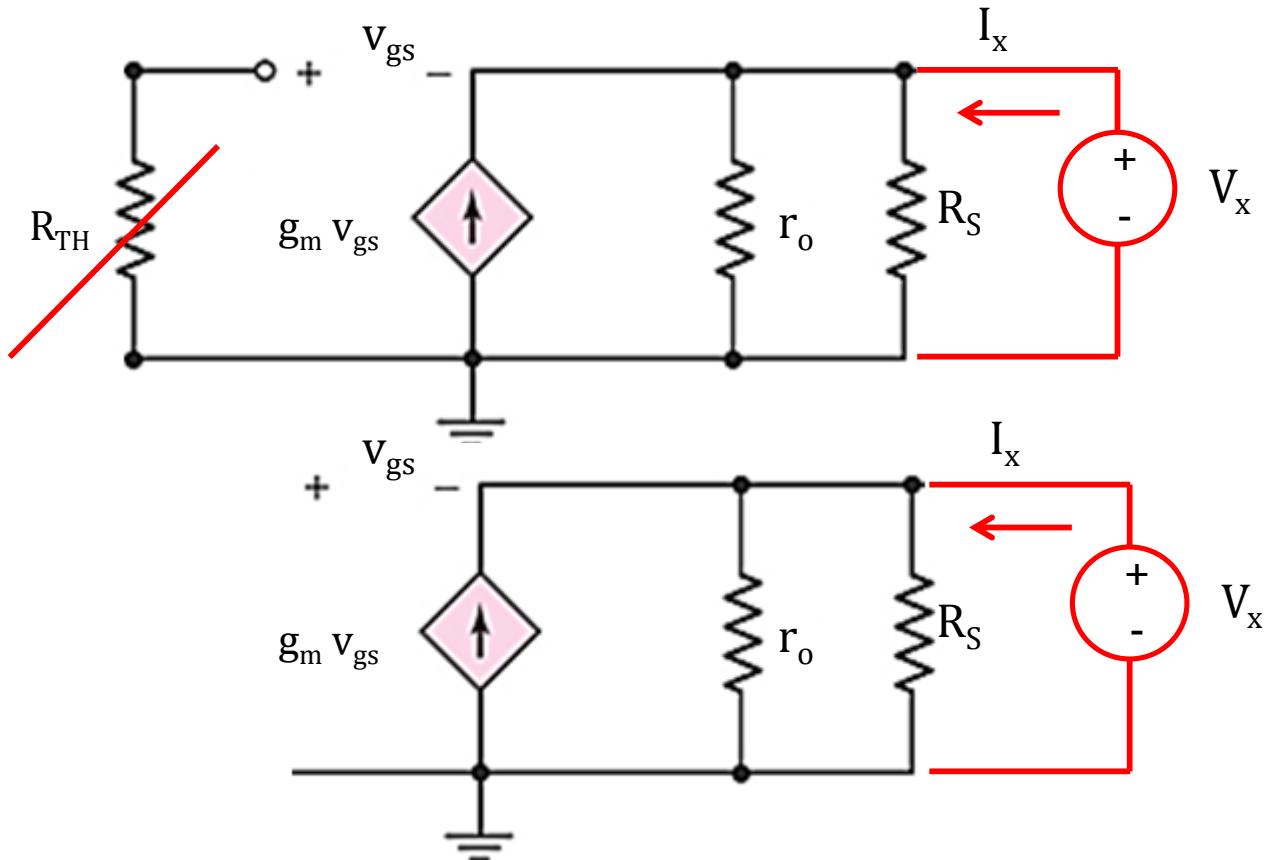

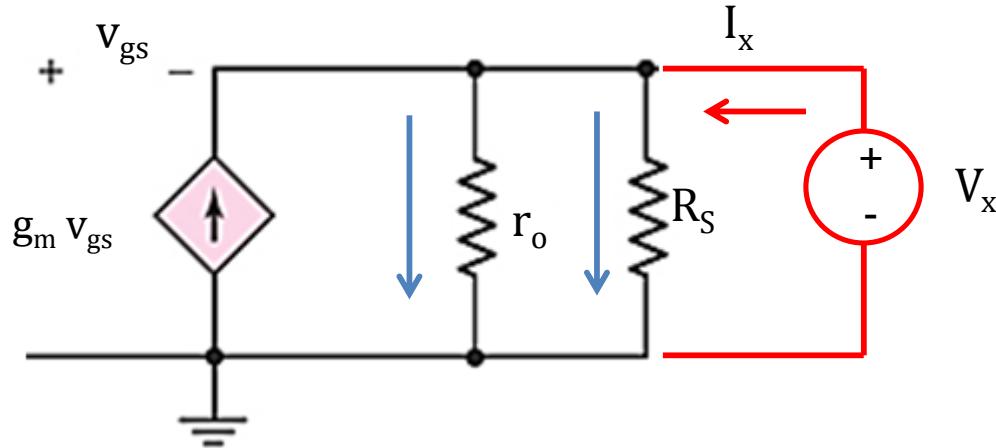v_{gs} in terms of V_x where $v_{gs} = -V_x$



Use nodal analysis

$$\frac{V_x}{r_o} + \frac{V_x}{R_s} = g_m v_{gs} + I_x$$

$$\frac{V_x}{r_o} + \frac{V_x}{R_s} = -g_m V_x + I_x$$


$$\frac{V_x}{r_o} + \frac{V_x}{R_s} + g_m V_x = I_x$$




$$R_0 = \left(\frac{1}{g_m} \parallel R_s \parallel r_o \right)$$

Using DC analysis, calculate the values of g_m and r_0 . Assuming that, $R_G = 100 \text{ k}\Omega$, $K_n = 1.25 \text{ mA/V}^2$, $V_A = 100 \text{ V}$, $I = 0.8 \text{ mA}$ and $R_L = 4 \text{ k}\Omega$

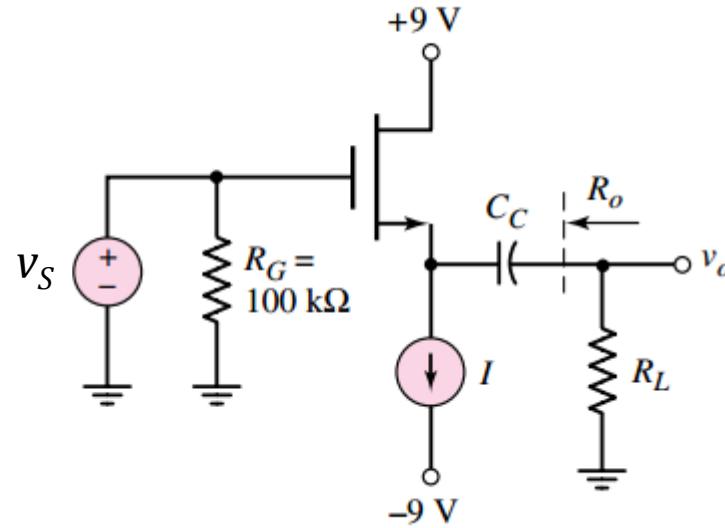Calculate the gain $A_v = \frac{v_o}{v_s}$ and R_o




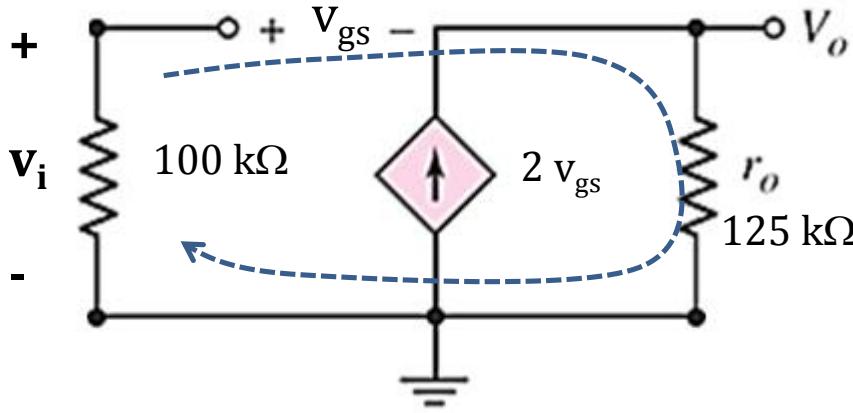

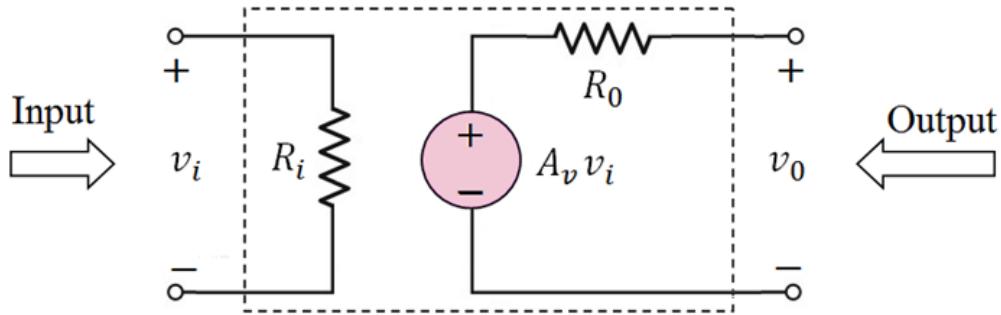1. The output resistance: $R_{eq} = r_o = 125 \text{ k}\Omega$
2. The output voltage $v_o = g_m v_{gs} (R_{eq}) = 2 v_{gs} (125) = 250 v_{gs}$
3. Find v_i in terms of v_{gs} using supermesh

$$v_i = v_{gs} + v_o$$

$$v_i = v_{gs} + 250 v_{gs} = 251 v_{gs}$$



Equivalent circuit of a voltage amplifier


$$\text{Equation of } v_o : v_o = v_o = g_m v_{gs} (R_{eq}) = 250 v_{gs}$$

$$v_i = 251 v_{gs}$$

$$A_v v_i = v_o \leftarrow \text{open circuit voltage}$$

$$A_v v_i = 250 v_{gs} = \frac{250 v_i}{251}$$
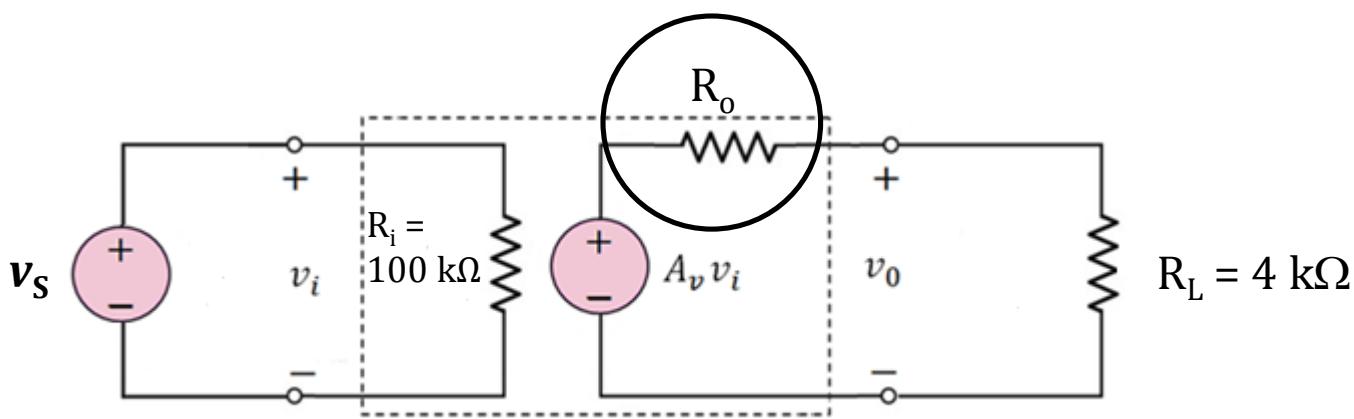
$$A_v = 0.996 \leftarrow \text{open circuit voltage gain}$$



Since we have R_L we have to calculate R_o

$$r_o = 125 \text{ k}\Omega, g_m = 2 \text{ mA/V} \text{ and there is no } R_S$$

$$\text{So, } R_o = 0.498 \text{ k}\Omega$$

$$R_o = \left(\frac{1}{g_m} \parallel R_S \parallel r_o \right)$$

v_i in terms of v_s


$v_i = v_s \leftarrow \text{in parallel}$

$$v_o = [R_L / (R_L + R_o)] * A_v v_i \leftarrow \text{this is because we have load resistor } R_L$$

$$v_o = [4 / (4.498)] (0.996 v_s)$$

$$v_o / v_s = 0.886$$

CURRENT GAIN

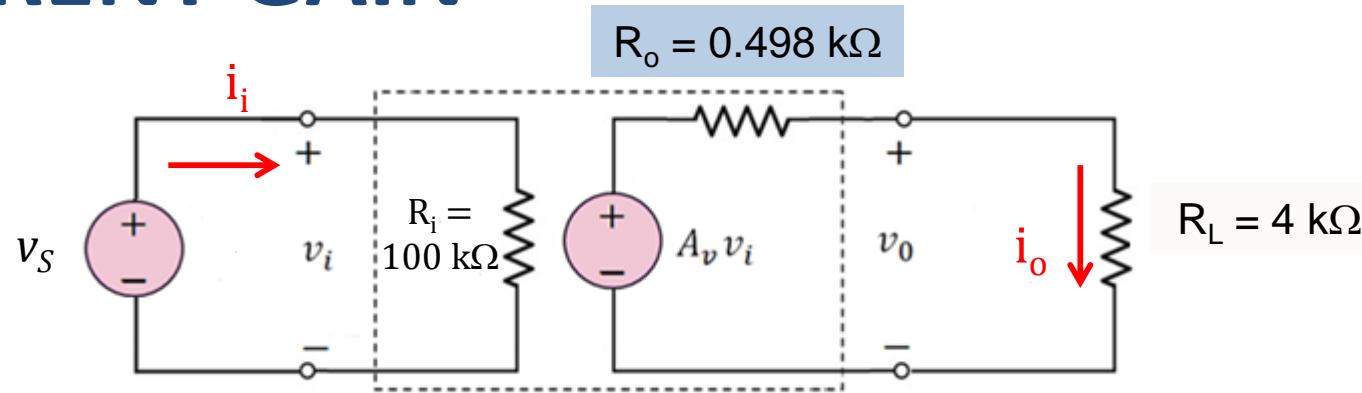

- Output side: $i_o = v_o / 4 = v_o / 4$
- Input side: $i_i = v_s / R_i = v_s / 100$

Current gain

$$= i_o / i_i$$

$$= \frac{v_o (100)}{v_s (4)} = 0.886 * 25$$

$$= 22.15$$

TYPE OF BJT AMPLIFIER	OPEN CIRCUIT VOLTAGE GAIN	INPUT RESISTANCE, R_i	OUTPUT RESISTANCE, R_o
COMMON SOURCE WITH SOURCE GROUNDED	$A_{voc} = - (r_o \parallel R_D) g_m$	R_{TH} or R_G	$r_o \parallel R_D$
COMMON SOURCE WITH R_S (assume $r_o = \infty$)	$A_{voc} = \left(\frac{-R_D g_m}{1 + g_m R_S} \right)$	R_{TH} or R_G	R_D
COMMON SOURCE WITH BYPASS CAPACITOR, C_S	$A_{voc} = - (r_o \parallel R_D) g_m$	R_{TH} or R_G	$r_o \parallel R_D$
COMMON DRAIN	$A_{voc} = \frac{g_m(r_o \parallel R_S)}{1 + g_m(r_o \parallel R_S)}$	R_{TH} or R_G	$\frac{1}{g_m} \parallel r_o \parallel R_S$