

# Type 3: With Source Bypass Capacitor, $C_S$

## ➤ Circuit with Source Bypass Capacitor

- An **source bypass capacitor** can be used to effectively create a short circuit path during ac analysis hence avoiding the effect  $R_S$
- $C_S$  becomes a short circuit path – bypass  $R_S$ ; hence similar to Type 1


## COMMON EMITTER with $C_E$

### OUTPUT SIDE

1. Get the equivalent resistance at the output side,  $R_O$
2. Get the  $v_o$  equation where  $v_o = -g_m v_{be} R_O$

### INPUT SIDE

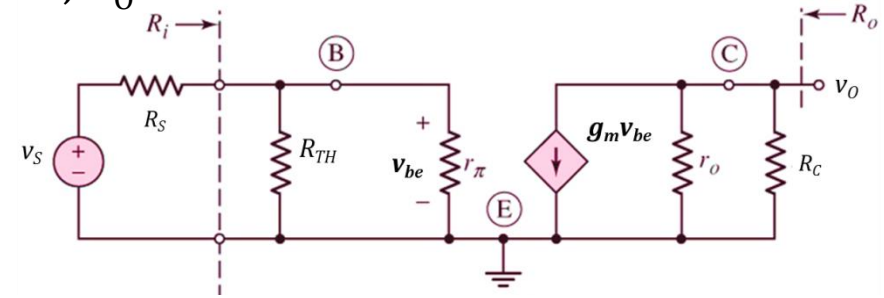3. Calculate  $R_i$
4. Get  $v_{be}$  in terms of  $v_i$




## COMMON SOURCE with $C_S$

### OUTPUT SIDE

1. Equivalent resistance at the output side,  $R_O$
2. Get the  $v_o$  equation where  $v_o = -g_m v_{gs} R_O$

### INPUT SIDE

3. Get  $v_{gs}$  in terms of  $v_i$

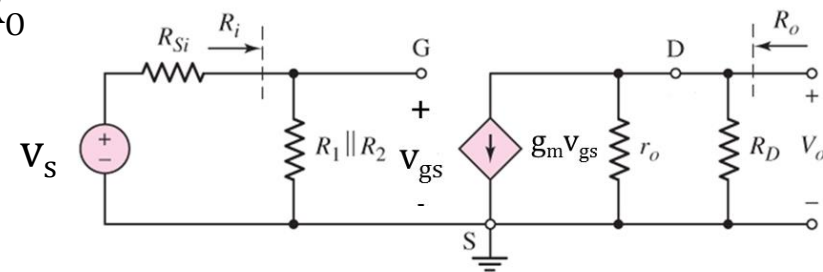

## OUTPUT SIDE

1. Equivalent resistance at the output side,  $R_O = r_o || R_D$
  2. Get the  $v_o$  equation where  $v_o = -g_m v_{gs} R_O = -g_m v_{gs} (r_o || R_D)$
- 


## INPUT SIDE

3. Get  $v_{gs}$  in terms of  $v_i \rightarrow v_{gs} = v_i$

4.  $A_v v_i = v_o = -g_m v_{gs} (r_o || R_D) \leftarrow$  open circuit voltage

$$A_v v_i = -g_m v_i (r_o || R_D)$$


$$A_v = -g_m (r_o || R_D) \leftarrow \text{open circuit voltage gain}$$

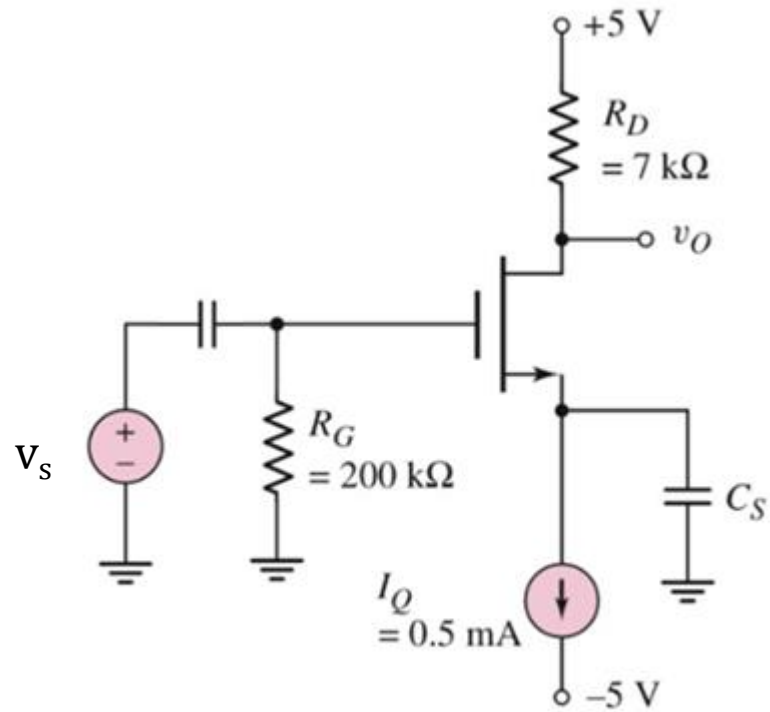


$$I_Q = 0.5 \text{ mA} \text{ hence, } I_D = 0.5 \text{ mA}$$

$$r_o = \infty$$
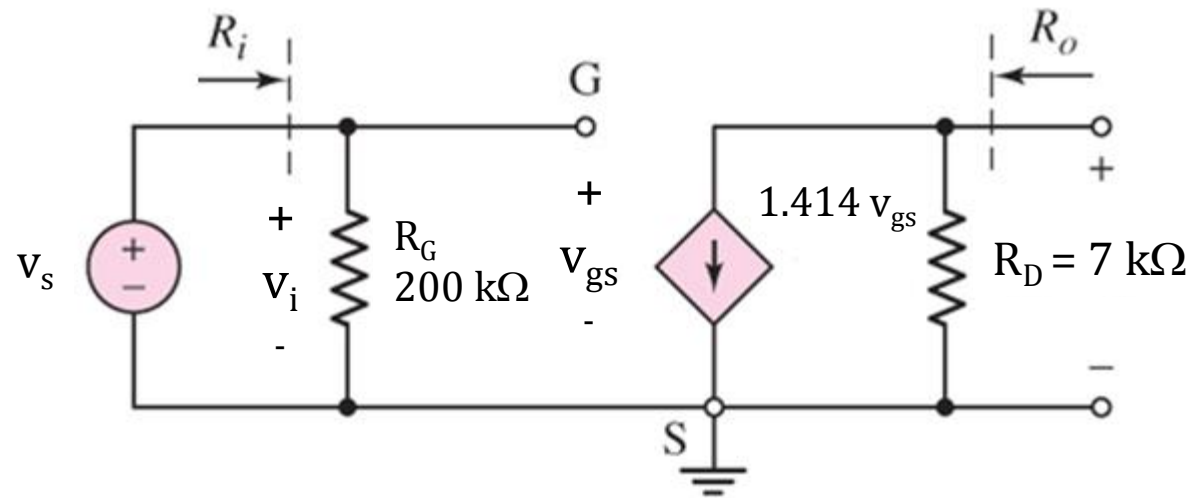
$$g_m = 2\sqrt{K_n I_{DQ}} \rightarrow g_m = 1.414 \text{ mA/V}$$



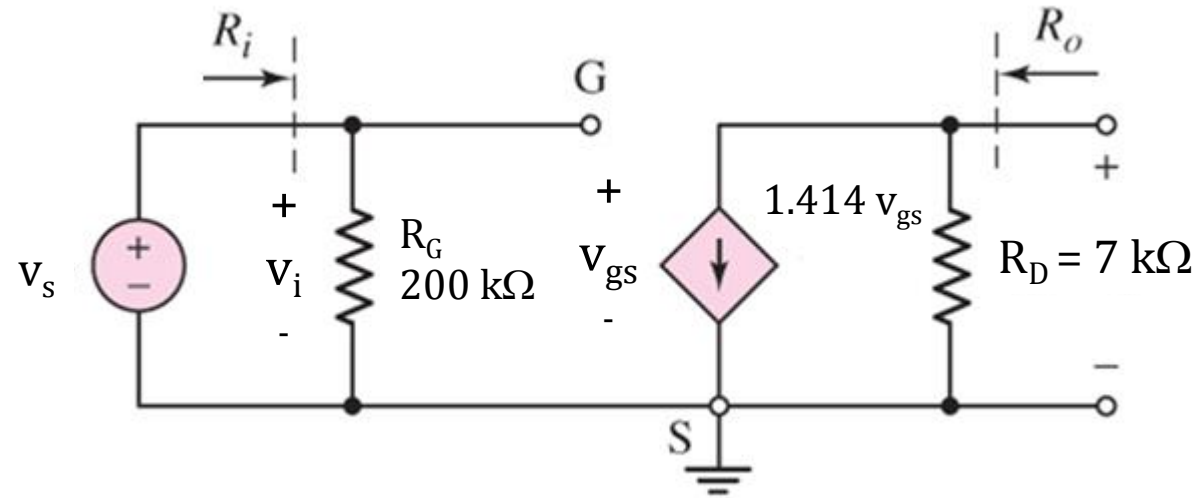


1. The output resistance,  $R_o = R_D = 7 \text{ k}\Omega$
2. The output voltage:

$$v_o = -g_m v_{gs} (R_D) = -1.414 (7) v_{gs} = -9.898 v_{gs}$$


---

3. The gate-to-source voltage:

$$v_{gs} = v_i$$

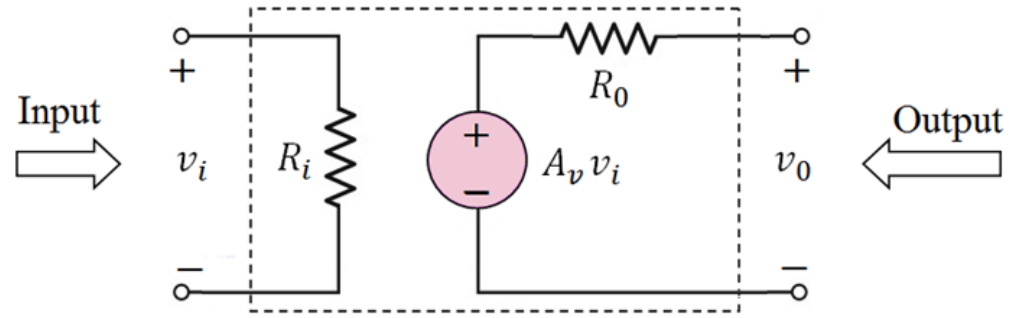

Equivalent circuit of a voltage amplifier


Equation of  $v_o$ :  $v_o = -g_m v_{gs} (R_D) = -1.414 (7) v_{gs} = -9.898 v_{gs}$

$V_i = V_{gs}$

$A_v v_i = v_o \leftarrow$  open circuit voltage

$A_v v_i = -9.898 v_{gs} = -9.898 v_i$

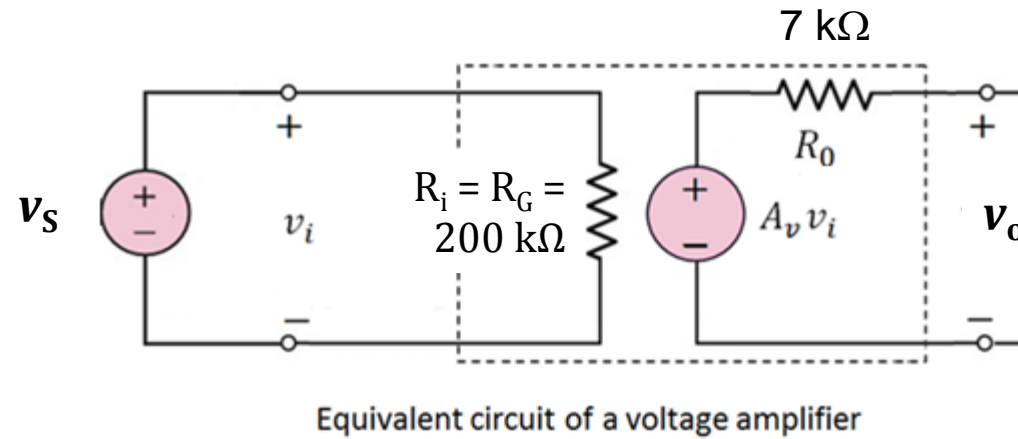$A_v = -9.898 \leftarrow$  open circuit voltage gain



To find new voltage gain,  $v_o/v_s$  with input signal voltage source,  $v_s$

$v_i$  in terms of  $v_s$

$v_i = v_s$  ← in parallel

$v_o = A_v v_i$  ← because there is no load resistor

$v_o = -9.898 (v_s)$


$v_o/v_s = -9.898$

| TYPE OF BJT AMPLIFIER                             | OPEN CIRCUIT VOLTAGE GAIN                               | INPUT RESISTANCE, $R_i$ | OUTPUT RESISTANCE, $R_o$ |
|---|---|-------------------------|--------------------------|
| COMMON SOURCE WITH SOURCE GROUNDED                | $A_{voc} = - (r_o    R_D) g_m$                          | $R_{TH}$ or $R_G$       | $r_o    R_D$             |
| COMMON SOURCE WITH $R_S$ (assume $r_o = \infty$ ) | $A_{voc} = \left( \frac{-R_D g_m}{1 + g_m R_S} \right)$ | $R_{TH}$ or $R_G$       | $R_D$                    |
| COMMON SOURCE WITH BYPASS CAPACITOR, $C_S$        | $A_{voc} = - (r_o    R_D) g_m$                          | $R_{TH}$ or $R_G$       | $r_o    R_D$             |


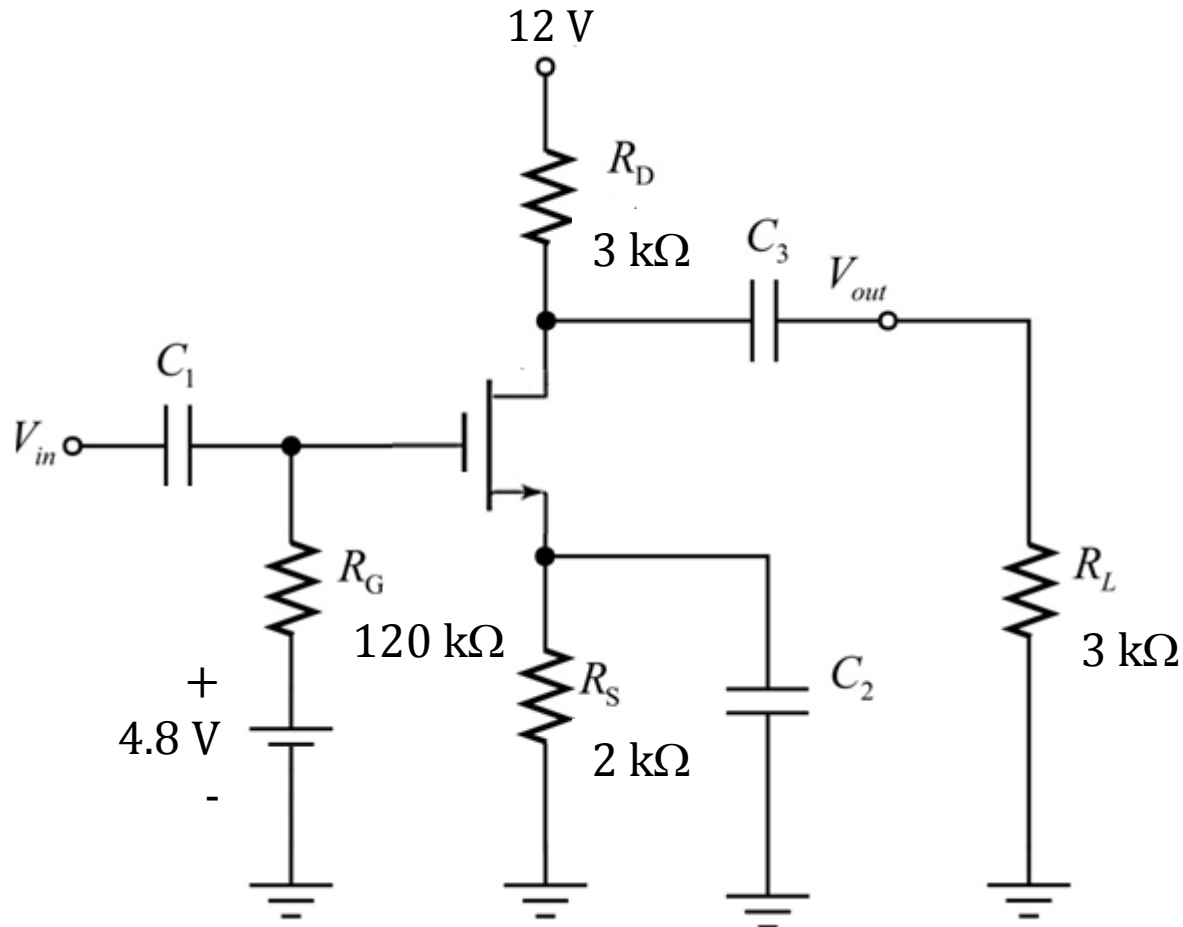
# Example

$$V_{TN} = 2 \text{ V}, K_n = 1 \text{ mA} / \text{V}^2, \lambda = 0$$



1. Without bypass capacitor – TYPE 2
2. With bypass capacitor – TYPE 3

## DC ANALYSIS

1. Calculate the value of  $V_{GS}$

**KVL at GS loop:**

$$0 + V_{GS} + 2(I_D) - 4.8 = 0$$

$$V_{GS} = 4.8 - 2I_D$$

2. Assume the transistor is biased in the saturation region, the drain current:

$$I_D = K_n (V_{GS} - V_{TN})^2$$

$$I_D = 1(4.8 - 2I_D - 2)^2 = 1(2.8 - 2I_D)^2$$

$$I_D = 1(7.84 - 11.2I_D + 4I_D^2)$$

$$4I_D^2 - 12.2I_D + 7.84 = 0$$

$$V_{TN} = 2 \text{ V}, K_n = 1 \text{ mA} / \text{V}^2$$

$$I_D = 2.13 \text{ mA}$$

$$\text{Replace in } V_{GS} \text{ equation in step 1} \rightarrow V_{GS} = 0.54 \text{ V}$$

$$I_D = 0.92 \text{ mA}$$

$$V_{GS} = 4.8 - 2I_D \rightarrow V_{GS} = 2.96 \text{ V}$$

Why choose  $V_{GS} = 2.96 \text{ V}$ ?  
Because it is bigger than  $V_{TN}$

3. Use KVL at DS loop

$$3I_D + V_{DS} + 2I_D - 12 = 0$$
$$V_{DS} = \mathbf{7.4\text{ V}}$$

4. Calculate  $V_{DSsat} = V_{GS} - V_{TN} = 4.8 - 2 = \mathbf{2.8\text{ V}}$

5. Confirm your assumption:  $V_{DS} > V_{DSsat}$ , our assumption is correct

$$g_m = 2\sqrt{K_n I_{DQ}} \longrightarrow g_m = 1.92\text{ mA/V}$$

$$\lambda = 0 \longrightarrow V_A = \infty \longrightarrow r_o = \infty$$