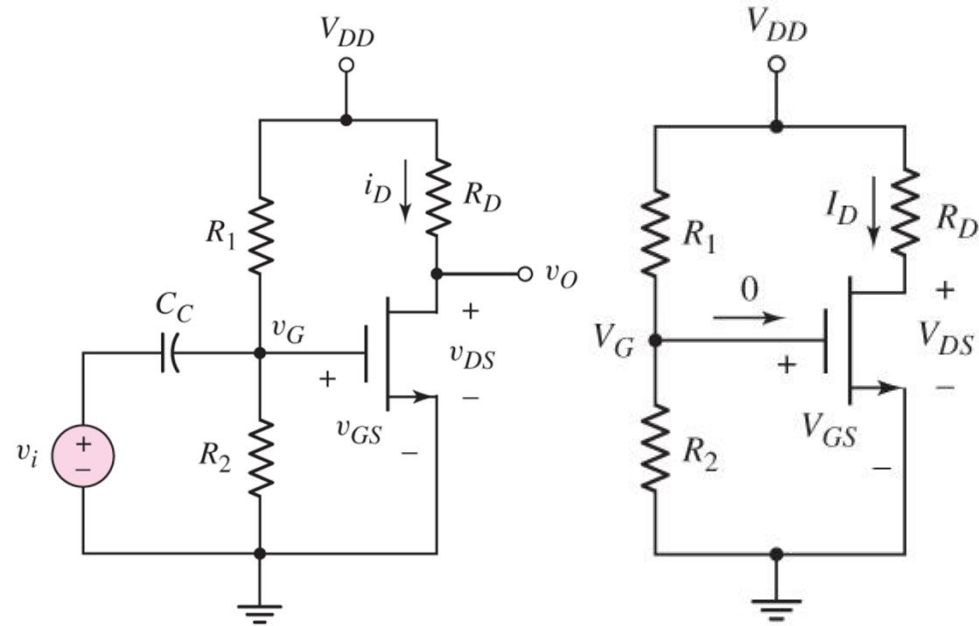


DC Analysis of FET

MOSFET DC Circuit Analysis - NMOS

- The source terminal is at ground and common to both input and output portions of the circuit.
- The C_C acts as an open circuit to dc but it allows the signal voltage to the gate of the MOSFET.



- In the DC equivalent circuit, the **gate current into the transistor is zero**, the voltage at the gate is given by a voltage divider principle:

$$V_G = V_{TH} = \left(\frac{R_2}{R_1 + R_2} \right) V_{DD}$$

MOSFET DC Circuit Analysis - NMOS

1. Calculate the value of V_{GS}
2. Assume the transistor is biased in the saturation region, the drain current:

$$I_D = K_n (V_{GS} - V_{TN})^2$$


3. Use KVL at DS loop

$$I_D R_D + V_{DS} - V_{DD} = 0$$

$$V_{DS} = V_{DD} - I_D R_D$$

 4. Calculate $V_{DSsat} = V_{GS} - V_{TN}$
5. Confirm your assumption:

If $V_{DS} > V_{DS(sat)} = V_{GS} - V_{TN}$, then the transistor is biased in the saturation region. If $V_{DS} < V_{DS(sat)}$, then the transistor is biased in the non-saturation region.



EXAMPLE:

Calculate the drain current and drain to source voltage of a common source circuit with an n-channel enhancement mode MOSFET. Assume that $R_1 = 30 \text{ k}\Omega$, $R_2 = 20 \text{ k}\Omega$, $R_D = 20 \text{ k}\Omega$, $V_{DD} = 5\text{V}$, $V_{TN} = 1\text{V}$ and $K_n = 0.1 \text{ mA/V}^2$

1. Calculate the value of V_{GS}

$$V_{TH} = \left(\frac{20}{30 + 20} \right) 5 = 2\text{V} \text{ hence } V_{GS} = V_{TH} = 2\text{V}$$

2. Assume the transistor is biased in the saturation region, the drain current:


$$I_D = K_n (V_{GS} - V_{TN})^2$$
$$I_D = 0.1(2 - 1)^2 = 0.1\text{mA}$$

3. Use KVL at DS loop

$$I_D R_D + V_{DS} - V_{DD} = 0$$


$$V_{DS} = V_{DD} - I_D R_D = 3\text{V}$$

 4. Calculate $V_{DSsat} = V_{GS} - V_{TN} = 2 - 1 = 1\text{V}$
5. Confirm your assumption: $V_{DS} > V_{DSsat}$, our assumption that the transistor is in saturation region is correct



 EXAMPLE

- The transistor has parameters $V_{TN} = 2V$ and $K_n = 0.25\text{mA/V}^2$.
- Find I_D and V_{DS}



Solution

1. Calculate the value of V_{GS}

$$V_{TH} = \left(\frac{160}{160 + 280} \right) 10 = 3.636 \text{ V}$$

KVL at GS loop: $V_{GS} - V_{TH} + 0 = 0 \rightarrow V_{GS} = V_{TH}$

2. Assume the transistor is biased in the saturation region, the drain current:

$$I_D = K_n (V_{GS} - V_{TN})^2$$
$$I_D = 0.25(3.636 - 2)^2 = 0.669 \text{ mA}$$


3. Use KVL at DS loop

$$I_D R_D + V_{DS} - V_{DD} = 0$$

$$V_{DS} = V_{DD} - I_D R_D = 3.31 \text{ V}$$

 5. Confirm your assumption: $V_{DS} > V_{DSsat}$, our assumption that the transistor is in saturation region is correct

Answer: $I_D = 0.669 \text{ mA}$ and $V_{DS} = 3.31 \text{ V}$



The MOSFET in the circuit shown has parameters, $V_{TN} = 0.8\text{ V}$ and $K_n = 0.03\text{ mA/V}^2$. Assume that, $R_1 = 160\text{ k}\Omega$, $R_2 = 520\text{ k}\Omega$ and $R_D = 6\text{ k}\Omega$. Calculate I_{DQ} and V_{DSQ} .

Solution

1. Calculate the value of V_{GS}

$$\text{KVL at GS loop: } V_{GS} - V_{TH} + 0 = 0 \rightarrow V_{GS} = 6.12 \text{ V}$$

2. Assume the transistor is biased in the saturation region, the drain current:

$$I_D = K_n (V_{GS} - V_{TN})^2$$

$$I_D = 0.03(6.12 - 0.8)^2 = 0.85 \text{ mA}$$

3. Use KVL at DS loop

$$I_D R_D + V_{DS} - 8 = 0$$

$$V_{DS} = 8 - 6(0.85) = 2.9 \text{ V}$$

4. Calculate $V_{DSsat} = V_{GS} - V_{TN} = 6.12 - 0.8 = 5.32 \text{ V}$

5. Confirm your assumption: $V_{DS} < V_{DSsat}$, our assumption that the transistor **is in saturation region is NOT CORRECT**

That means our transistor is in non-saturation mode: Go back to step 2

$$I_D = K_n [2(V_{GS} - V_{TN})V_{DS} - V_{DS}^2]$$

$$I_D = 0.03 \left[2(5.32)(8 - 6I_D) - (8 - 6I_D)^2 \right]$$

$$33.33 I_D = \left[10.64(8 - 6I_D) - (64 - 96I_D + 36I_D^2) \right]$$

$$33.33 I_D = \left[85.12 - 63.84 I_D - 64 + 96I_D - 36I_D^2 \right]$$

$$36 I_D^2 + 1.17 I_D - 21.12 = 0$$

$$I_D = 0.75 \text{ mA}$$

$$I_D = -0.78 \text{ mA}$$

3. Go back to DS loop


$$I_D R_D + V_{DS} - 8 = 0$$



$$V_{DS} = 8 - 6(0.75) = 3.5 \text{ V}$$

Answer: $I_D = 0.75 \text{ mA}$ and $V_{DS} = 3.5 \text{ V}$

LOAD LINE, I_D versus V_{DS}

 
- Common source configuration i.e source is grounded.
- It is the linear equation of I_D
- Use KVL
- $V_{DS} = V_{DD} - I_D R_D$
- $I_D = \frac{-V_{DS}}{R_D} + \frac{V_{DD}}{R_D}$



 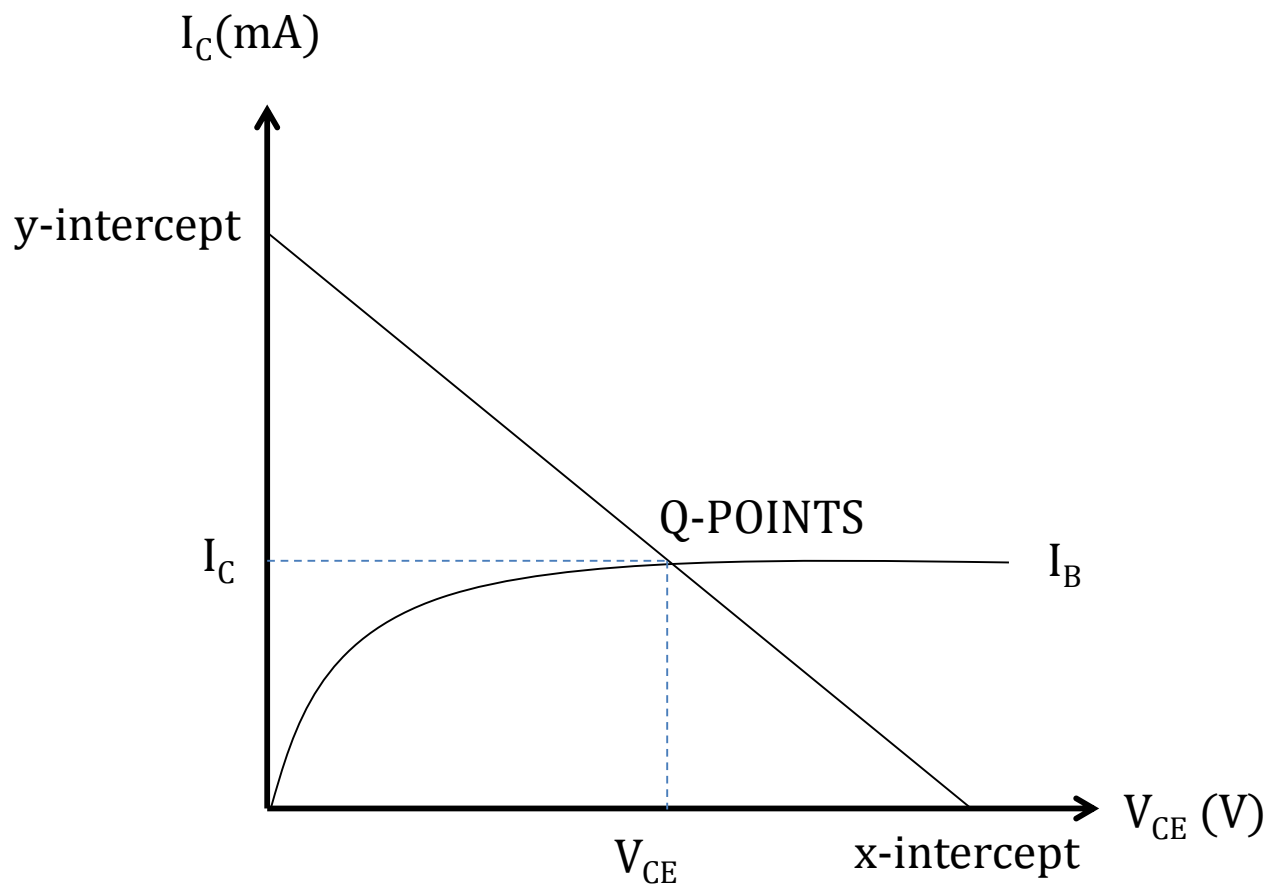

- DC Analysis where source is NOT GROUNDED

 For the NMOS transistor in the circuit below, the parameters are $V_{TN} = 1V$ and $K_n = 0.5 \text{ mA/V}^2$.



1. Calculate the value of V_{GS}

KVL at GS loop:

$$0 + V_{GS} + 1(I_D) - 5 + 1 = 0$$

$$V_{GS} = 4 - I_D$$

2. Assume the transistor is biased in the saturation region, the drain current:

$$I_D = K_n (V_{GS} - V_{TN})^2$$

$$I_D = 0.5(4 - I_D - 1)^2 = 0.5(3 - I_D)^2$$

$$2I_D = 9 - 6I_D + I_D^2$$

$$I_D^2 - 8I_D + 9 = 0$$

$$I_D = 6.646 \text{ mA}$$

$$I_D = 1.354 \text{ mA}$$


Replace in V_{GS}
equation in step 1

$$V_{GS} = 4 - I_D$$

$$V_{GS} = -2.646 \text{ V}$$


$$V_{GS} = 2.646 \text{ V}$$

 Why choose $V_{GS} = 2.646 \text{ V}$?
Because it is bigger than V_{TN}



 3. Use KVL at DS loop

$$\begin{aligned} I_D R_D + V_{DS} + I_D R_S - 5 - 5 &= 0 \\ 1.354 (2) + V_{DS} + 1.354 - 10 &= 0 \\ V_{DS} &= 10 - 1.354 - 2.708 = \mathbf{5.938 \text{ V}} \end{aligned}$$




4. Calculate $V_{DSsat} = V_{GS} - V_{TN} = 2.646 - 1 = \mathbf{1.646 \text{ V}}$

5. Confirm your assumption: $V_{DS} > V_{DSsat}$, our assumption is correct

 EXAMPLE 2

Assume that the transistor parameters are $V_{TN} = 0.8 \text{ V}$ and $K_n = 0.80 \text{ mA/V}^2$. Given $V_{DD} = 5 \text{ V}$ and $R_1 + R_2 = 670 \text{ k}\Omega$, design the circuit such that $I_D = 0.88 \text{ mA}$ and $V_{DS} = 2.5 \text{ V}$. Confirm any assumptions you make during your analysis.



Answers:

$$R_1 = 422 \text{ k}\Omega$$

$$R_2 = 248 \text{ k}\Omega$$

$$R_D = 2.84 \text{ k}\Omega$$