

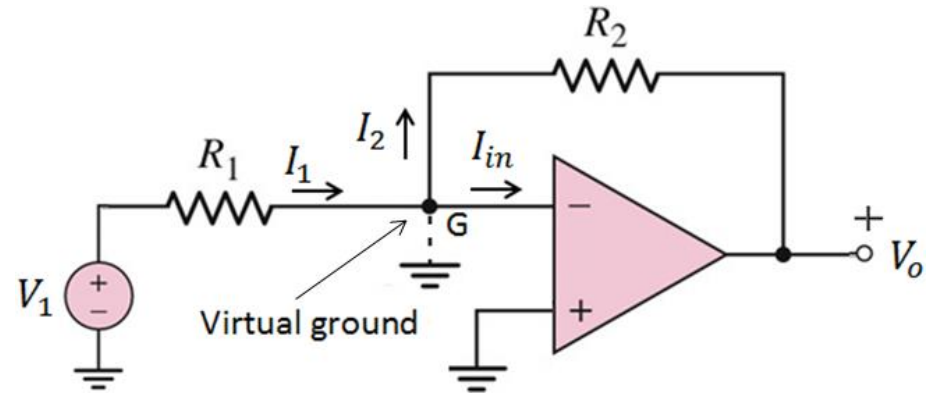
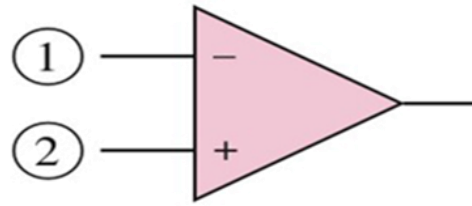



INVERTING AMPLIFIER

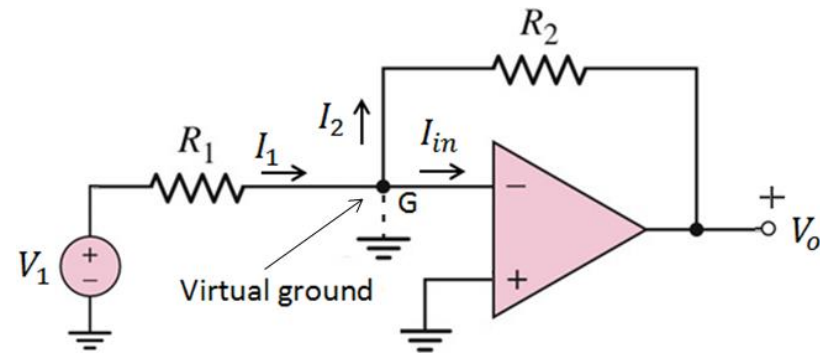

We want the open loop gain to be equal to ∞ which means that $v_2 = v_1$

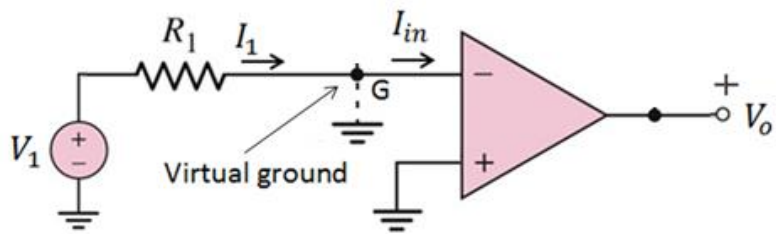the input resistance to be equal to ∞ , hence there is no current going into the op-amp



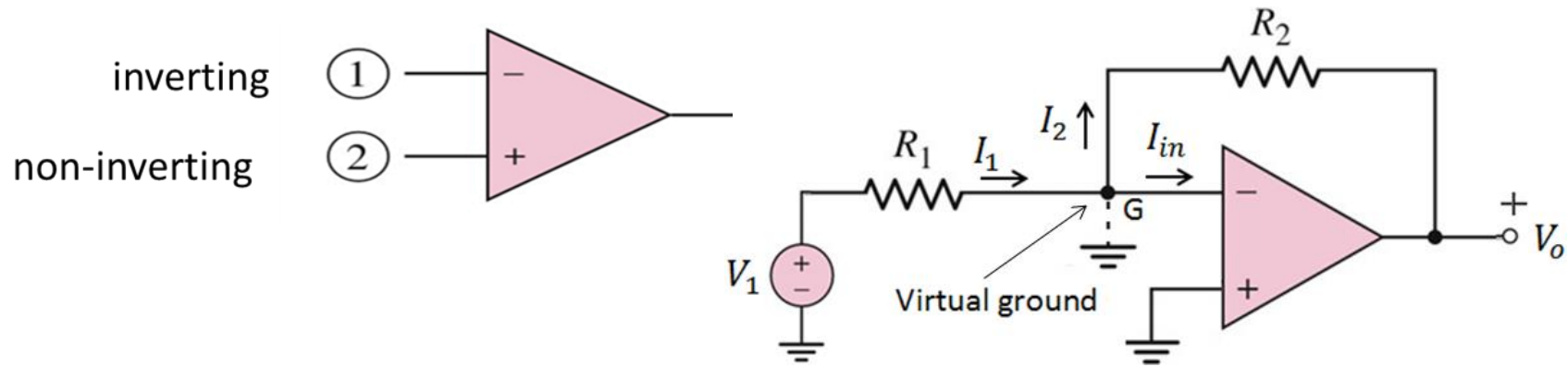

Voltage at node 1 (inverting) = voltage at node 2 (non-inverting)

KCL at node 1:

$$I_1 - I_2 - I_{in} = 0$$

$$(V_1 - 0) / R_1 = (0 - V_o) / R_2$$

$$V_i / R_1 = - V_o / R_2$$

$$\frac{V_o}{V_i} = -\frac{R_2}{R_1}$$




Voltage gain, $A_v = \frac{V_o}{V_i} = -\frac{R_2}{R_1}$

Input Resistance, $R_i = \frac{V_i}{I_1} = R_1$

Output resistance, $R_o = \frac{V_o}{I_2} = R_2$

Example 1

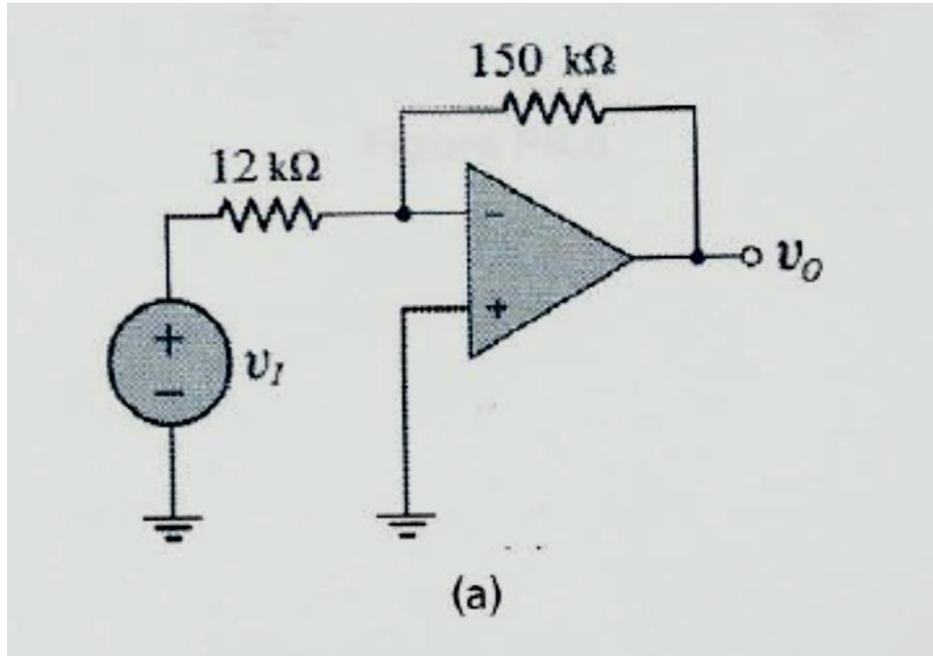

KCL at node 1:

$$I_1 - I_2 - I_{in} = 0$$

$$(V_i - 0) / 12k = (0 - V_o) / 150k$$

$$V_i / 12 = -V_o / 150$$

$$\frac{V_o}{V_i} = \frac{-150}{12}$$


$$\text{Gain} = -(R_2 / R_1) = -(150/12) = \mathbf{-12.5}$$

Example 2

A voltage source V_S with source resistance $R_S = 1.5\text{ k}\Omega$ is connected to the input of an op-amp inverting amplifier circuit

- (a) If the $R_1 = 1.0\text{ k}\Omega$ and $R_2 = 15.0\text{ k}\Omega$ then calculate the voltage gain, V_O/V_S
(b) Determine the output voltage V_O for the source voltage $V_S = 45\text{ mV}$


Series \rightarrow ADD

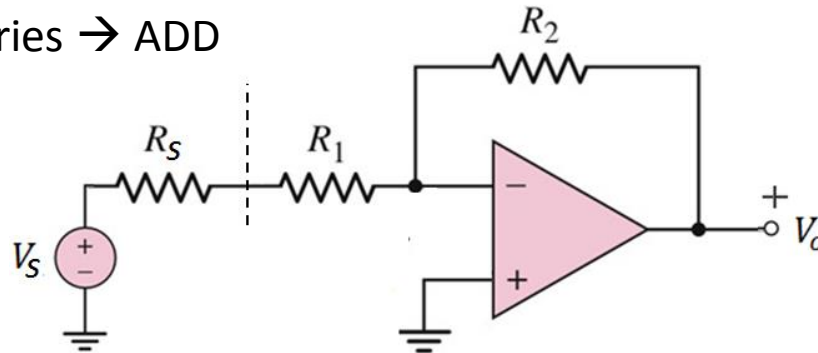

Answers:

(a) - 6

(b) - 0.27 V

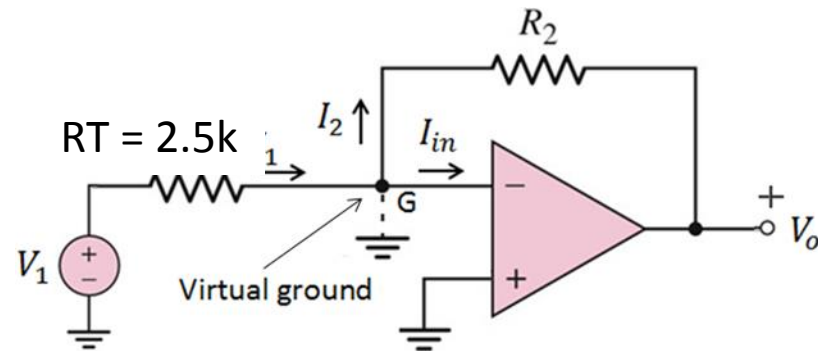

$$V_O/V_S = -6$$

$$V_O/45\text{mV} = -6$$

$$V_O = -270\text{mV} = -0.27\text{V}$$