Chapter 3 Diode Circuits

Rectifier

Rectifier Circuits

- A DC power supply is required to bias all electronic circuits.
- A diode rectifier forms the first stage of a DC power supply.



Diagram of an Electronic Power Supply

- Rectification is the process of converting an alternating (ac) voltage into one that is limited to one polarity.
- Rectification is classified as <u>half-wave</u> or <u>full-wave</u> rectifier.

Rectifier Parameters

Relationship between the number of turns of a step-down transformer and the input/output voltages - transformer ratio

$$\frac{v_P}{v_S} = \frac{N_1}{N_2}$$



The **peak inverse voltage (PIV)** of the diode is the peak value of the voltage that a diode can withstand when it is reversed biased

Duty Cycle: The **fraction of the wave cycle** over which the diode is conducting.

Half Wave Rectifier

- $V_{S} < V\gamma$, diode off, open circuit, no current flow, <u>Vo = 0V</u>
- $\mathcal{V}_{S} \geq \mathbf{V} \boldsymbol{\gamma}$, diode conducts, current flows,

 $\mathcal{V}_{o} = \mathcal{V}_{S} - \mathcal{V}_{D}$

5V

VSA

Vγ

0

 θ_1



Equation of $V_{\rm 0}$ and current when diode is conducting

$$v_O = i_D R = v_S - V_D$$

$$i_D = \frac{v_S - V_D}{R}$$



- $V_{S} < V\gamma$, diode off, **open circuit**, no current flow, $V_{O} = 0V$
- $V_{S} > V\gamma$, diode conducts, current flows and $V_{O} = V_{S} V_{D}$

Consider a sine wave where $V_{g} = V_{m} \sin \omega t$ and V_{m} is the peak value



Example

Consider the rectifier circuit in the figure below. Let $R=1~k\Omega$, and the diode has the properties of $V_{\gamma}=0.6~V$ and $r_f=20~\Omega.$

Assume $V_s = 10 \sin \omega t (V)$

- i. Determine the **peak value** of the diode current
- ii. Sketch v_0 versus time, t. Label the peak value of v_0 .



SOLUTION

 $0.6 + I_D r_f + I_D R - 10 = 0$ $I_D = (10 - 0.6) / 1020 = 9.22 \text{ mA}$



- Peak Inverse Voltage Half Wave
- Duty cycle Half Wave

Peak Inverse Voltage is also known as Maximum Reverse Biased Voltage

• The objective is to know whether the diode can withstand a certain voltage when it is reversed and to avoid damaging the diode – each diode has PIV rating. $V_{RMS} = \frac{1}{\sqrt{2}} \times V_{pk}$

Maximum Ratings and Electrical Characteristics @TA = 25°C unless otherwise specified

Single phase, half wave, 60Hz, resistive or inductive load. For capacitive load, derate current by 20%.

Characteristic	Symbol	1N4001	1N4002	1N4003	1N4004	1N4005	1N4006	1N4007	Unit
Peak Repetitive Reverse Voltage Working Peak Reverse Voltage DC Blocking Voltage	VRRM VRWM VR	50	100	200	400	600	800	1000	v
RMS Reverse Voltage	V _{R(RMS)}	35	70	140	280	420	560	700	V
Average Rectified Output Current (Note 1) @ TA = 75°C	lo	0.000	1.0					A	
Non-Repetitive Peak Forward Surge Current 8.3ms single half sine-wave superimposed on rated load	IFSM		30					A	
Forward Voltage @ I _F = 1.0A	VFM		1.0					V	
Peak Reverse Current @T _A = 25°C at Rated DC Blocking Voltage @ T _A = 100°C	IRM		5.0 50					μΑ	
Typical Junction Capacitance (Note 2)	Ci		15 8			pF			
Typical Thermal Resistance Junction to Ambient	Reja		100					K/W	
Maximum DC Blocking Voltage Temperature	TA		+150					°C	
Operating and Storage Temperature Range	TJ. TSTG	-65 to +150				°C			

Notes: 1. Leads maintained at ambient temperature at a distance of 9.5mm from the case.

2. Measured at 1.0 MHz and applied reverse voltage of 4.0V DC.

3. EU Directive 2002/95/EC (RoHS). All applicable RoHS exemptions applied, see EU Directive 2002/95/EC Annex Notes.



Hence, for the example just now, the PIV for the diode is 10 V

• **Duty cycle** is the fraction of the wave cycle over which the diode is conducting with respect to the full wave of the cycle



Hence for this example:

$$0.6 = 10 \sin (\theta_1)$$

 $\theta_1 = \sin^{-1} (0.6/10) = 3.44^{\circ}$

At second quadrant for sine wave: 176.56° $\theta_2 = 180^{\circ} - \theta_1$

Duty cycle =
$$\left(\frac{\theta_2 - \theta_1}{2\pi}\right) X 100\% = 48\%$$



A half-wave rectifier circuit is connected to a 2 k Ω load as shown in the figure. Assume that the input of the transformer is connected to a 120 V(rms), 60 Hz power supply, the turns ratio of the step-down transformer is 10:1, the diode cut-in voltage V γ = 0.7 V

- i. Calculate the peak output voltage, v_o
- ii. Determine the peak diode current, i_D

iii. Determine the fraction of conduction angle of a cycle when diode is conducting.

v_o = 16.27 V i_D = 16.27 / 2 = 8.135 mA Duty cycle = 48.69%

Full Wave Rectifier

- Center-Tapped
 - Bridge





Full-Wave Rectification – circuit with center-tapped transformer

- > Positive cycle, D2 off, D1 conducts; $V_o - V_s + V_D = 0$ $V_o = V_s - V_D$
- > Negative cycle, D1 off, D2 conducts; $V_o - V_s + V_D = 0$ $V_o = V_s - V_D$
- Since a rectified output voltage occurs during both positive and negative cycles of the input signal, this circuit is called a full-wave rectifier.
- Also notice that the polarity of the output voltage for both cycles is the same





 $V_{\rm s} = V_{\rm m} \sin \omega t$



• $V_s < V\gamma$, diode off, open circuit, no current flow, $V_o = 0V$

PIV FOR CENTER-TAPPED RECTIFIER



- A full-wave center-tapped rectifier circuit is shown in the figure below. Assume that for each diode, the cut-in voltage, $V_{\gamma} = 0.6$ V and the diode forward resistance, r_f is 15 Ω . The load resistor, $R = 95 \Omega$. Determine:
 - i. peak output voltage, v_o across the load, R
 - ii. Sketch the output voltage, v_0 and label its peak value.



• SOLUTION

i. peak output voltage, V_o









Full-Wave Rectification –Bridge Rectifier

- Positive cycle, D_1 and D_2 conducts, D_3 and D_4 off; $V_D + V_o + V_D V_s = 0$ $v_o = v_s 2V_D$
- Negative cycle, D3 and D4 conducts, D1 and D2 off $V_D + V_o + V_D V_s = 0$ $v_o = v_s 2V_D$





>Also notice that the **polarity of the output voltage for both cycles is the same**

PIV FOR BRIDGE RECTIFIER



 $v_R = v_s peak - V_D$

Summary of PIV

Type of Rectifier	PIV
Half Wave	Peak value of the input secondary voltage, $v_{s (peak)}$
Full Wave : Center-Tapped	2v _{s (peak)} - V _D
Full Wave: Bridge	v _{s (peak)} - V _D

• DUTY CYCLE FOR FULL WAVE



Multiply by 2