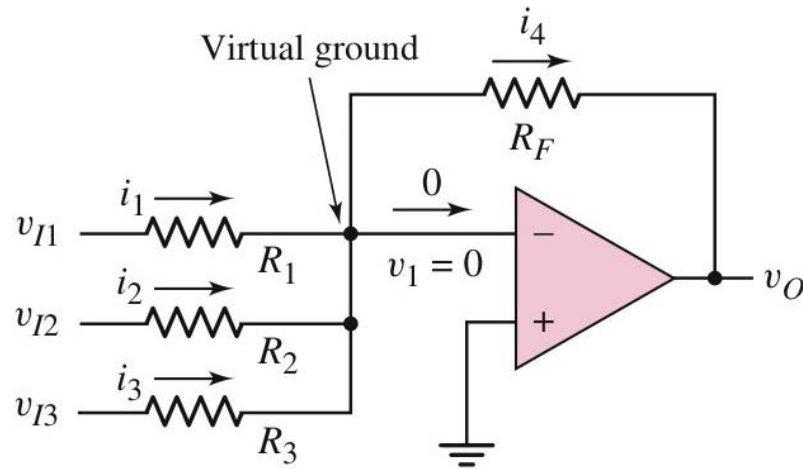


SUMMING AMPLIFIER



Similarly,

Using KCL at the input node

$$i_1 + i_2 + i_3 - i_4 - 0 = 0$$

Output voltage

$$V_0 = -R_F \left(\frac{V_{i1}}{R_1} + \frac{V_{i2}}{R_2} + \frac{V_{i3}}{R_3} \right)$$

$$V_0 = -R_F \left(\frac{V_{i1}}{R_1} + \frac{V_{i2}}{R_2} \right)$$

Example 8.2

Design a summing amplifier as shown in figure to produce a specific output signal, such that $v_o = 1.25 - 2.5 \cos \omega t$ volt. Assume the input signals are $v_{i1} = -1.0 \text{ V}$, $v_{i2} = 0.5 \cos \omega t$ volt. Assume the feedback resistance $R_F = 10 \text{ k}\Omega$

Solution: output voltage

$$V_0 = -R_F \left(\frac{V_{i1}}{R_1} + \frac{V_{i2}}{R_2} \right) = -R_F \left[\frac{(-1)}{R_1} + \frac{0.5 \cos \omega t}{R_2} \right]$$

$$\text{Or, } 1.25 - 2.5 \cos \omega t = R_F \left[\frac{1}{R_1} - \frac{0.5 \cos \omega t}{R_2} \right]$$

$$\text{Or, } \boxed{1.25} - \boxed{2.5} \cos \omega t = \boxed{\frac{R_F}{R_1}} - \boxed{\left(\frac{R_F}{R_2} \right) (0.5 \cos \omega t)}$$

$$\frac{R_F}{R_1} = 1.25 \quad \text{Or, } R_1 = \frac{R_F}{2.5} = \frac{10}{1.25} = 8 \text{ k}\Omega$$

$$\left(\frac{R_F}{R_2} \right) (0.5 \cos \omega t) = 2.5 \cos \omega t \quad \text{Or, } R_2 = R_F \times \frac{0.5 \cos \omega t}{2.5 \cos \omega t} = 10 \times \frac{0.5}{2.5} = 2 \text{ k}\Omega$$

Calculating Gain and Design Questions

INVERTING

$$\text{Voltage gain, } A_v = \frac{V_o}{V_i} = -\frac{R_2}{R_1}$$

NON - INVERTING


$$\text{Voltage gain, } A_v = \frac{V_o}{V_i} = 1 + \frac{R_2}{R_1}$$

Calculating Output and Design Questions

SUMMING AMPLIFIER

Output voltage
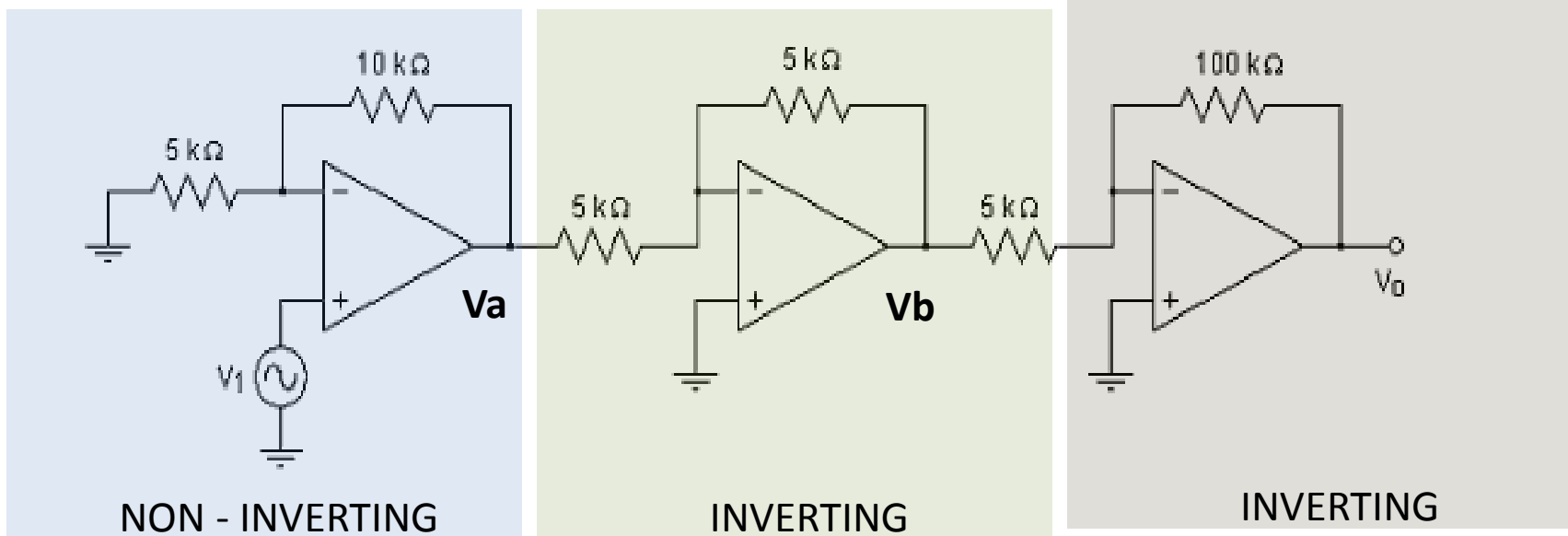
$$V_o = -R_F \left(\frac{V_{i1}}{R_1} + \frac{V_{i2}}{R_2} + \frac{V_{i3}}{R_3} \right)$$



Calculate the input voltage if the final output, V_o is 10.08 V.

Finally:

$$V_a = (1 + 10/5) V_1$$

$$0.504 = 3V_1$$

$$\underline{V_1 = 0.168 \text{ V}}$$



Then:

$$V_b = -(5/5) V_a$$

$$-0.504 = -V_a$$

$$V_a = 0.504 \text{ V}$$




Have to work backwards:

$$V_o = -(100/5) V_b$$

$$10.08 = -20 V_b$$

$$V_b = -0.504 \text{ V}$$

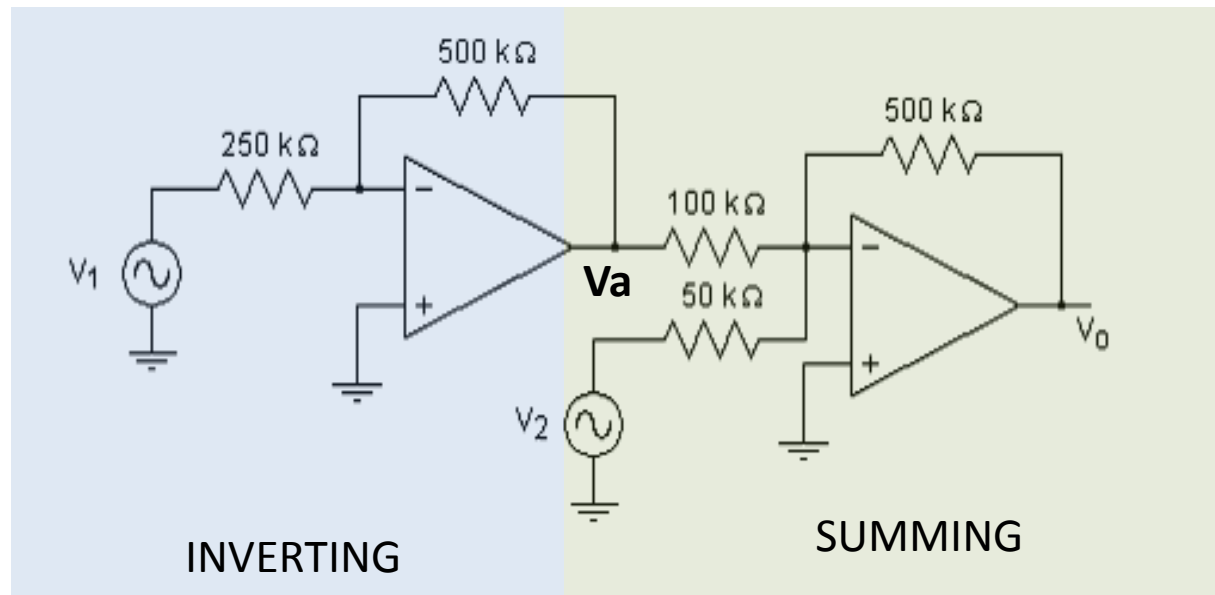

Calculate the output voltage, V_o if V₁ = V₂ = 700 mV

$$V_a = -(500/250) 0.7$$

$$V_a = -1.4 \text{ V}$$




Then:

$$V_o = - 500 [V_a / 100 + V_2 / 50]$$

$$V_o = - 500 [-1.4 / 100 + 0.7 / 50]$$

$$V_o = 0 \text{ V}$$

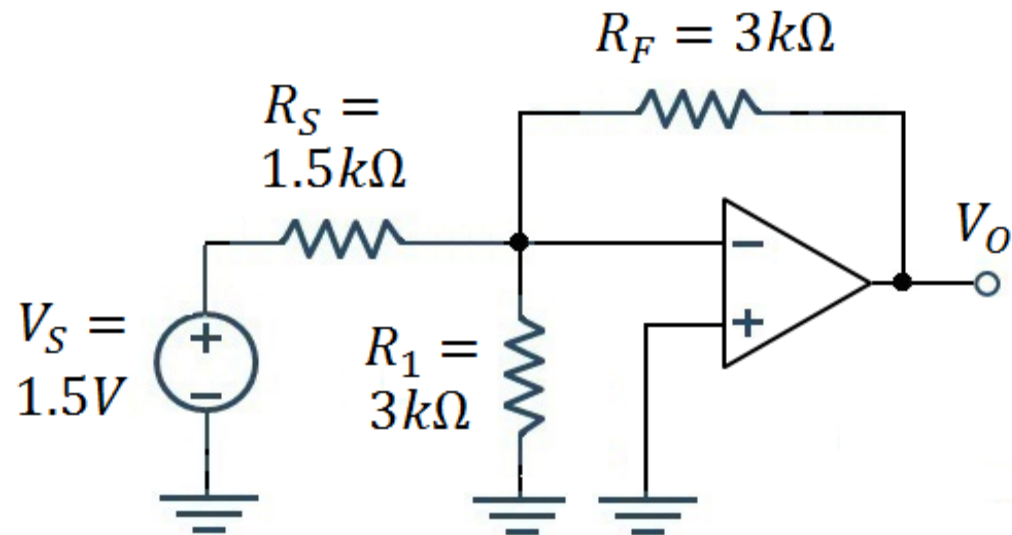

Calculate the output voltage V_O of the operational amplifier circuit as shown in the figure.

Answer: -3 V

$$i_1 - i_2 - i_3 - 0 = 0$$

$$(V_S - 0) / R_S - [(0 - 0) / R_1] - [(0 - V_O) / R_F] = 0$$

$$1.5 / 1.5 - [(- V_O) / 3] = 0$$

$$1 + [V_O / 3] = 0$$

$$V_O / 3 = -1$$

$$V_O = -3 \text{ V}$$