
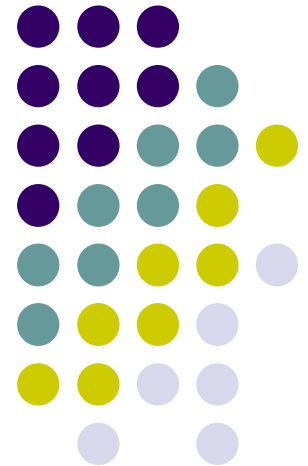



Voltage Transfer Characteristic

V_O versus V_i

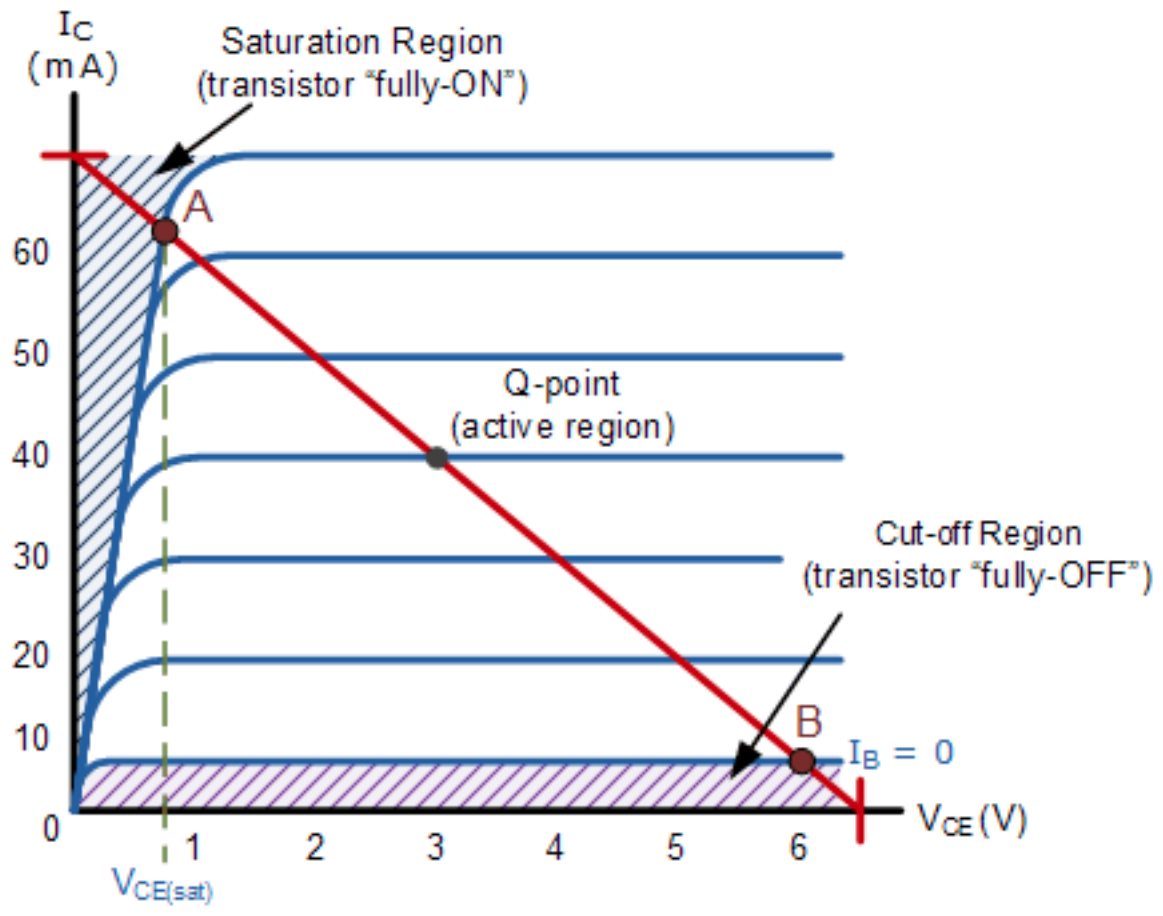





Voltage Transfer Characteristics - npn

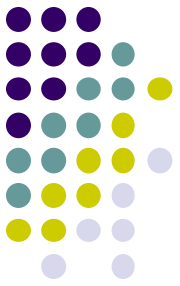



- A plot of the transfer characteristics (**output voltage versus input voltage**) can also be used to visualize the operation of a circuit or the state of a transistor.
- the input is voltage changed slowly enough that the output can keep up.

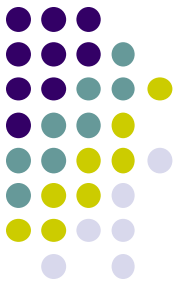

Example 1

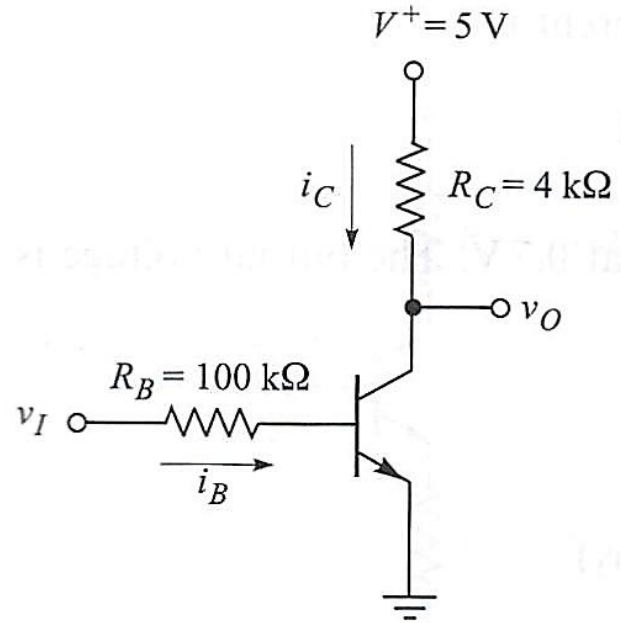

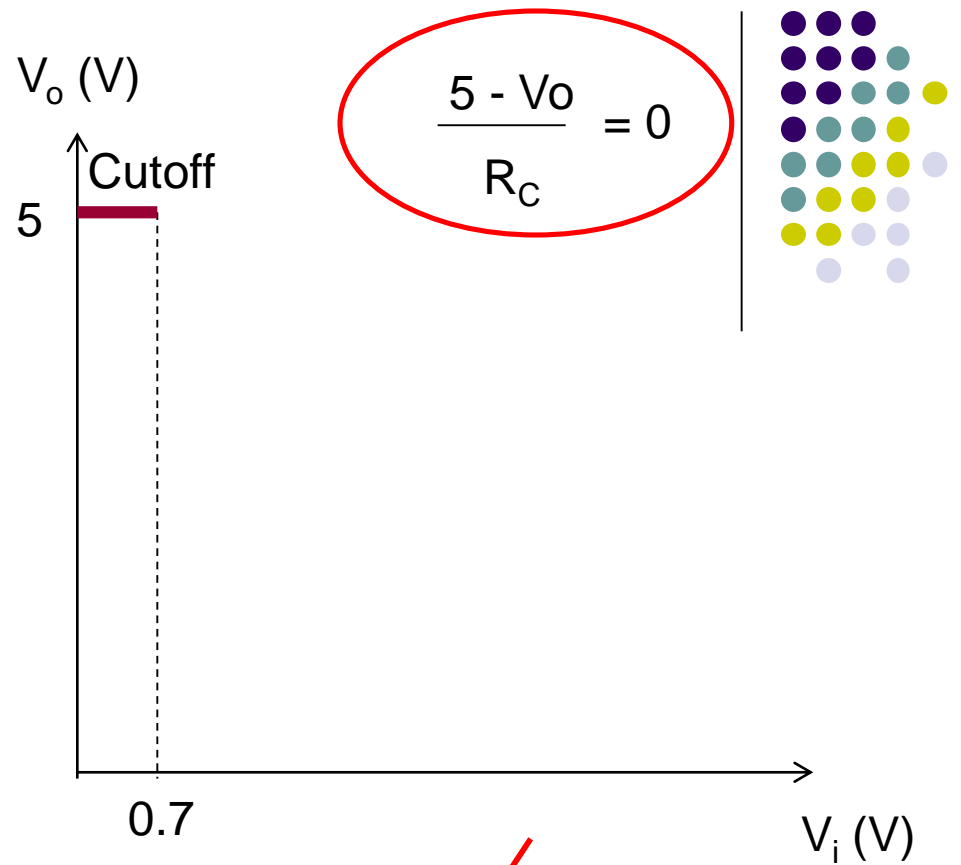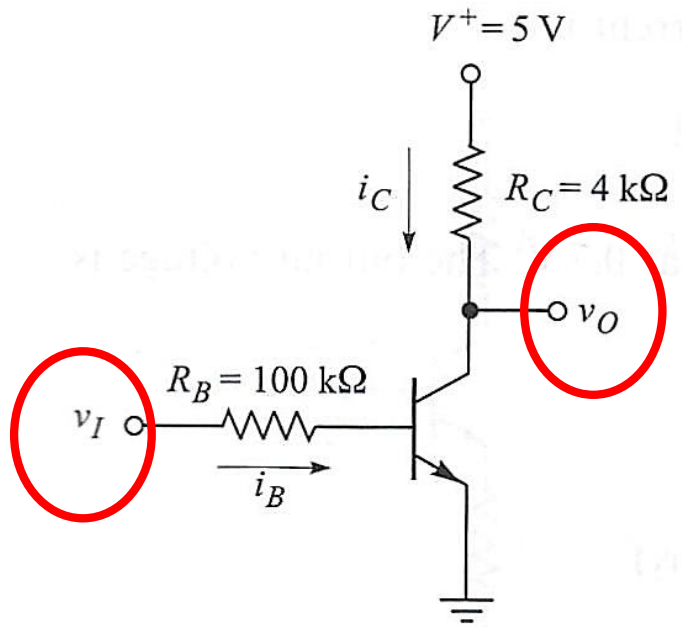Given $V_{BEon} = 0.7\text{V}$, $\beta = 120$, $V_{CEsat} = 0.2\text{V}$, Develop the voltage transfer curve





• In this circuit, $V_o = V_C = V_{CE}$

$V_{CE} = V_C - V_E$ $V_{CE} = V_C$

- Initially, the transistor is in **cutoff mode** because V_i is too small to turn on the diodes. In cut off mode, there is no current flow.
- Then as V_i starts to be bigger than V_{BEon} the transistor operates in **forward-active mode**.

Active Mode

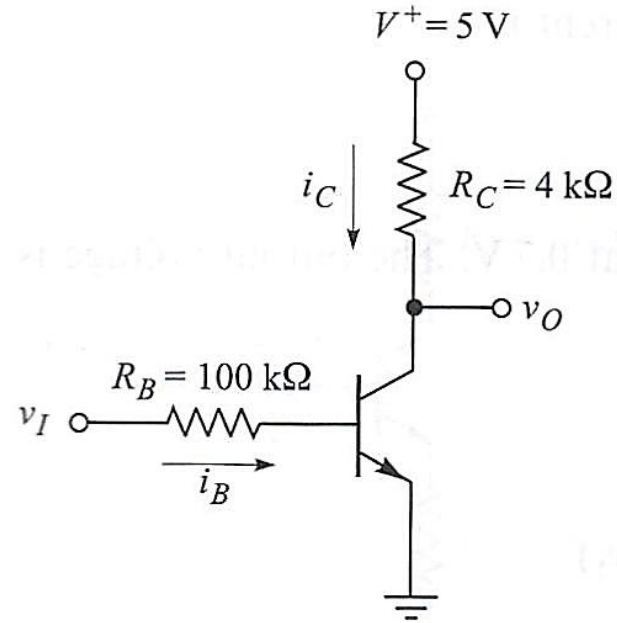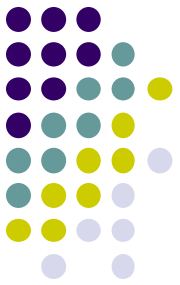

- BE Loop

- $100I_B + V_{BE} - V_i = 0$
- $I_B = (V_i - 0.7) / 100$



- CE Loop

- $I_C R_C + V_O - 5 = 0$
- $I_C = (5 - V_O) / 4$
- $\beta I_B = (5 - V_O) / 4$ $\beta = 120$
- $I_B = (5 - V_O) / 480$

A linear equation with negative slope

- Equate the 2 equations:
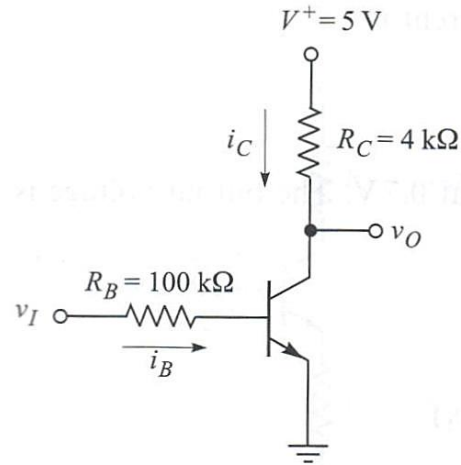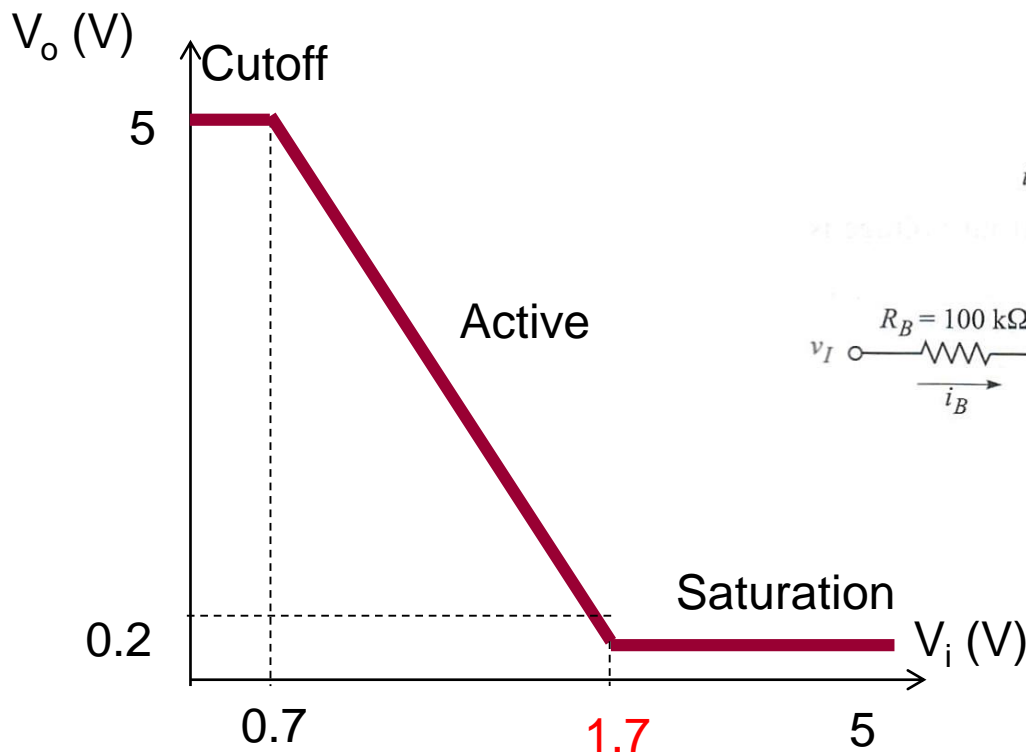
$$(V_i - 0.7) / 100 = (5 - V_O) / 480 \quad \Rightarrow \quad V_O = \frac{-480 V_i + 836}{100}$$



To find point x, the coordinate is (x, 0.2)


- However, as you increase V_i even further, it reaches a point where both diodes start to become forward biased – transistor is now in **saturation mode**.
- In saturation mode, $V_O = V_{CEsat} = 0.2\text{V}$. So, what is the starting point, x, of the input voltage, V_i when this occurs?

Need to substitute in the linear equation \rightarrow
and V_O stays constant at 0.2V until $V_i = 5\text{V}$


$$V_o = \frac{-480 V_i + 836}{100}$$

$$\rightarrow V_i = 1.7\text{ V}$$

Example 2

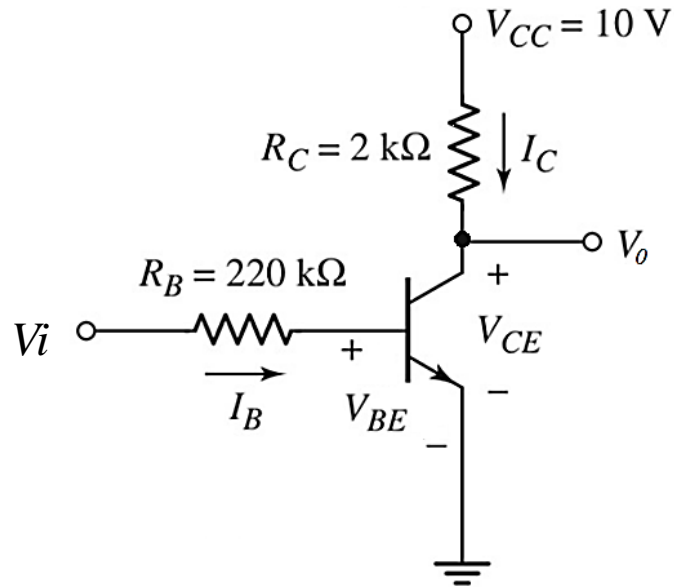

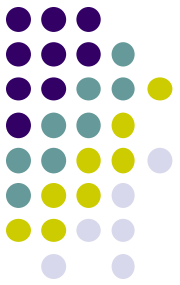Develop the voltage transfer curve given V_{CE} at saturation = 0.25 V.



What happen to V_o when $V_{in} < 0.7V$?

CUTOFF


$$V_o = V_{CC} = 10 \text{ V}$$

What happen to V_o when $V_{in} > 0.7V$?

ACTIVE

BE LOOP & CE LOOP EQUATION

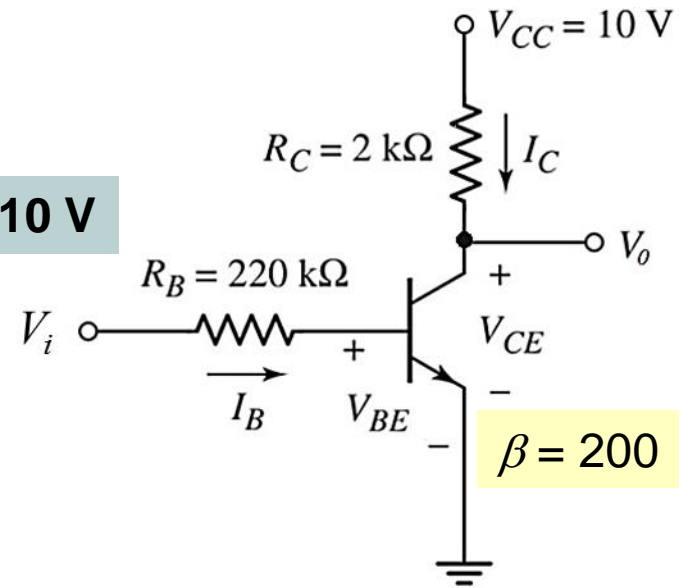What happen to V_i when V_o reach saturation $V_{CEsat} = 0.25V$?



$$V_o = V_C = V_{CE}$$

$$V_o = V_{CEsat} = 0.25 \text{ V}$$

SATURATION

- BE Loop

- $220I_B + V_{BE} - V_i = 0$

- $I_B = (V_i - 0.7) / 220$

- CE Loop

- $I_C R_C + V_O - 10 = 0$

- $I_C = (10 - V_O) / 2$

- $200I_B = (10 - V_O) / 2$

- $I_B = (10 - V_O) / 400$

- Equate the 2 equations:

$$(V_i - 0.7) / 220 = (10 - V_O) / 400$$

$$V_o = - 1.82 V_i + 11.274$$

