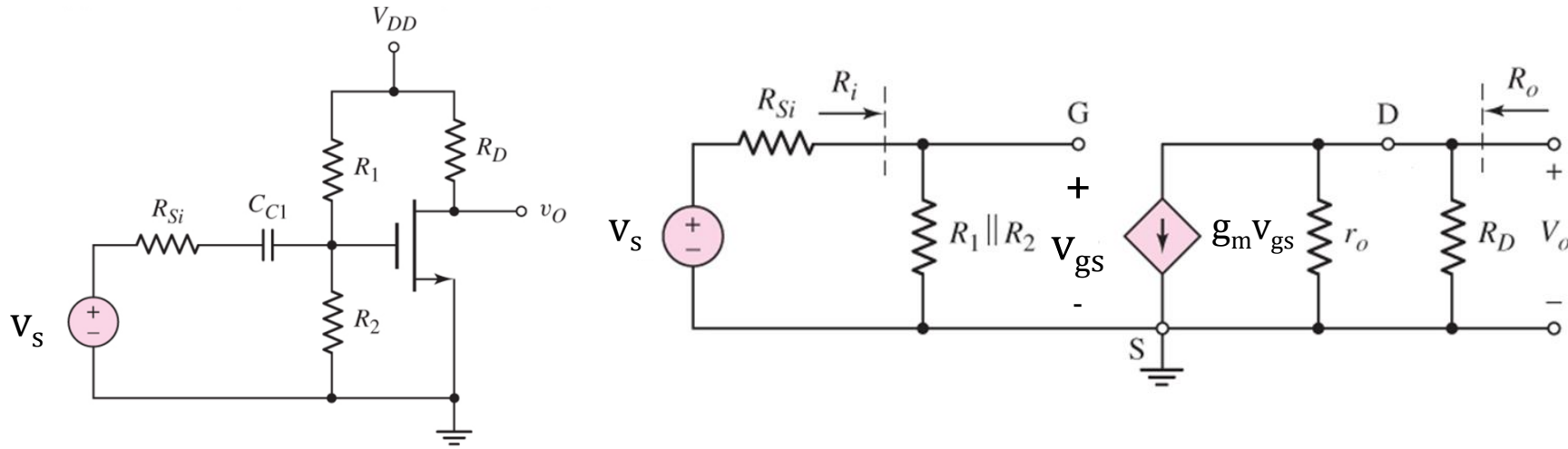


The MOSFET Amplifier - COMMON SOURCE

- The **output** is measured at the **drain** terminal
- The gain is **negative value**
- Three types of common source
 - source grounded
 - with source resistor, R_s
 - with bypass capacitor, C_s

Common Source - Source Grounded

- A Basic Common-Source Configuration:



Assume that the transistor is biased in the saturation region by resistors R_1 and R_2 , and the signal frequency is sufficiently large for the coupling capacitor to act essentially as a short circuit.

EXAMPLE

The transistor parameters are:


$V_{TN} = 0.8V$, $K_n = 0.2mA/V^2$ and $\lambda = 0$.

Voltage Divider biasing:

Change to Thevenin Equivalent

$$R_{TH} = 198 \text{ k}\Omega$$

$$V_{TH} = 1.905 \text{ V}$$

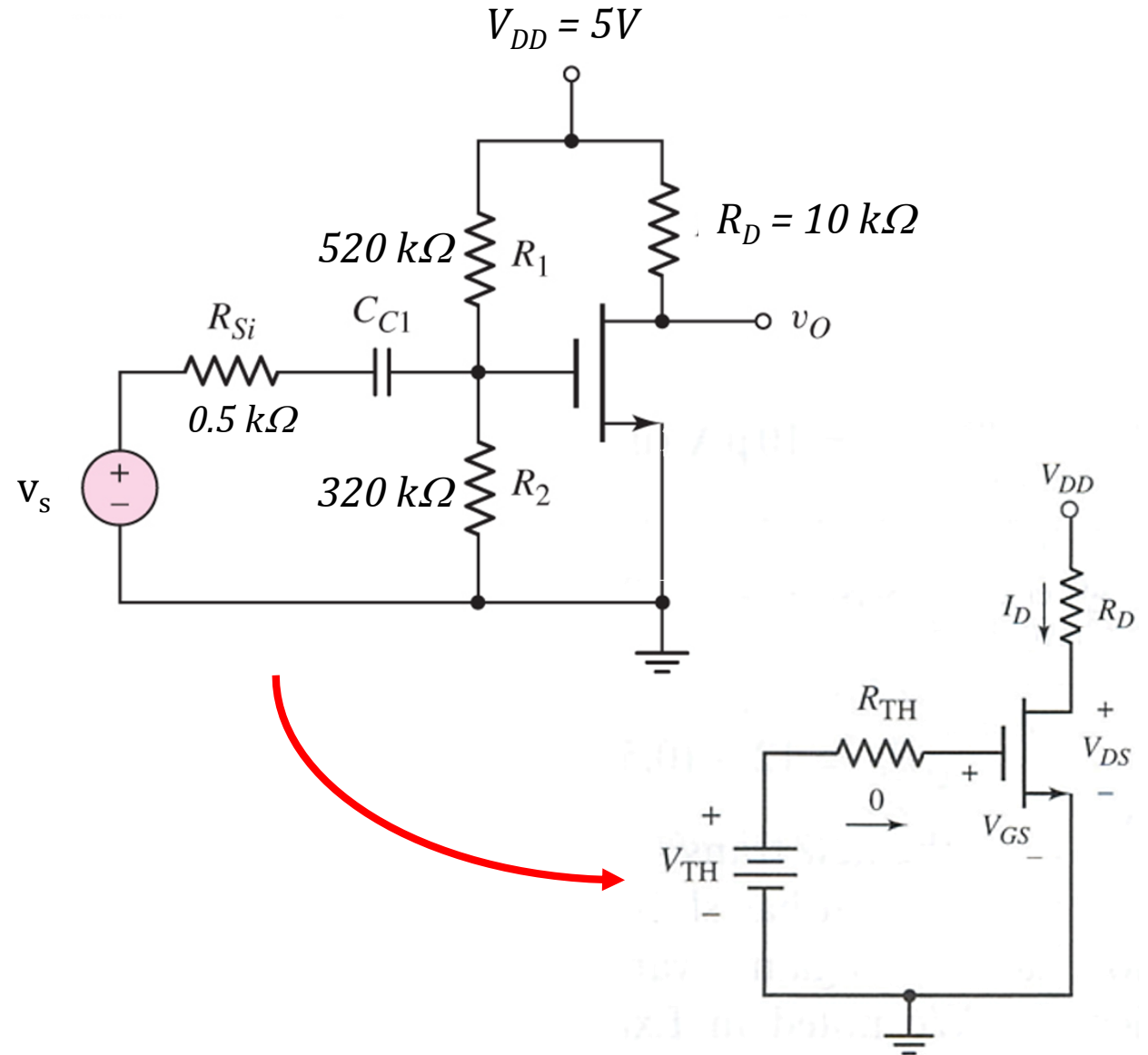

DC ANALYSIS

1. Calculate the value of V_{GS}

$$V_{GS} - V_{TH} = 0$$

$$V_{GS} = 1.905 \text{ V}$$

2. Assume the transistor is biased in the saturation region, the drain current:

$$I_D = K_n (V_{GS} - V_{TN})^2$$

$$I_D = 0.2(1.905 - 0.8)^2 = 0.244 \text{ mA}$$

3. Use KVL at DS loop

$$I_D R_D + V_{DS} - V_{DD} = 0$$

$$V_{DS} = V_{DD} - I_D R_D = 2.56 \text{ V}$$

4. Calculate $V_{DSsat} = V_{GS} - V_{TN} = 1.905 - 0.8 = 1.105 \text{ V}$
5. Confirm your assumption: $V_{DS} > V_{DSsat}$, our assumption that the transistor is in saturation region is correct

$$g_m = 2\sqrt{K_n I_{DQ}} \longrightarrow g_m = 0.442 \text{ mA/V}$$


COMMON EMITTER GROUNDED

OUTPUT SIDE

1. Get the equivalent resistance at the output side, R_o
2. Get the v_o equation where $v_o = -g_m v_{be} R_o$

INPUT SIDE

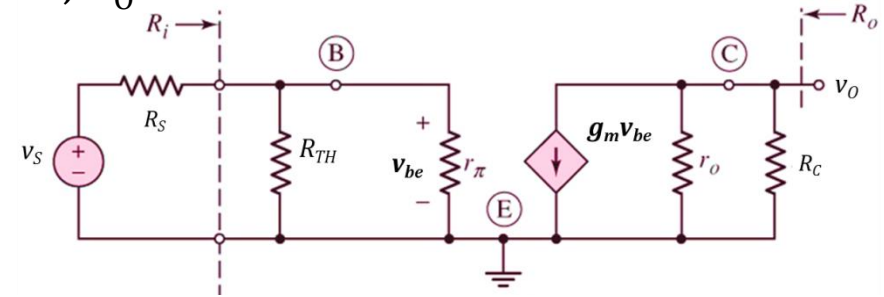
3. Calculate R_i
4. Get v_{be} in terms of v_i



COMMON SOURCE GROUNDED


OUTPUT SIDE

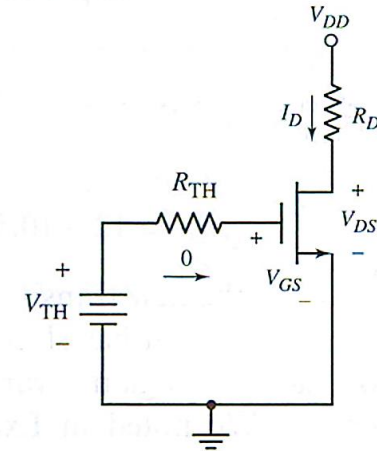1. Equivalent resistance at the output side, R_o
2. Get the v_o equation where $v_o = -g_m v_{gs} R_o$



INPUT SIDE

3. Get v_{gs} in terms of v_i

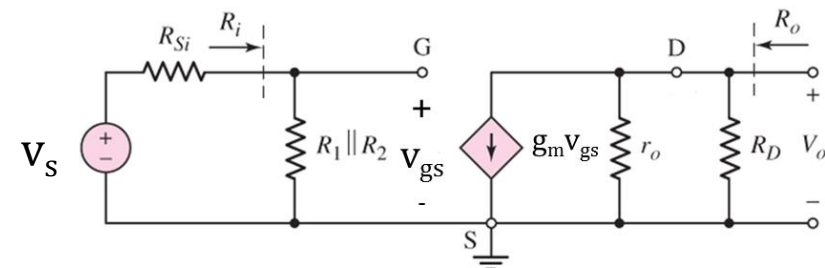


OUTPUT SIDE

1. Equivalent resistance at the output side, $R_o = r_o || R_D$
 2. Get the v_o equation where $v_o = -g_m v_{gs} R_o = -g_m v_{gs} (r_o || R_D)$
-

INPUT SIDE

3. Get v_{gs} in terms of $v_i \rightarrow v_{gs} = v_i$
4. $A_v v_i = v_o = -g_m v_{gs} (r_o || R_D) \leftarrow$ open circuit voltage
 $A_v v_i = -g_m v_i (r_o || R_D)$
 $A_v = -g_m (r_o || R_D) \leftarrow$ open circuit voltage gain

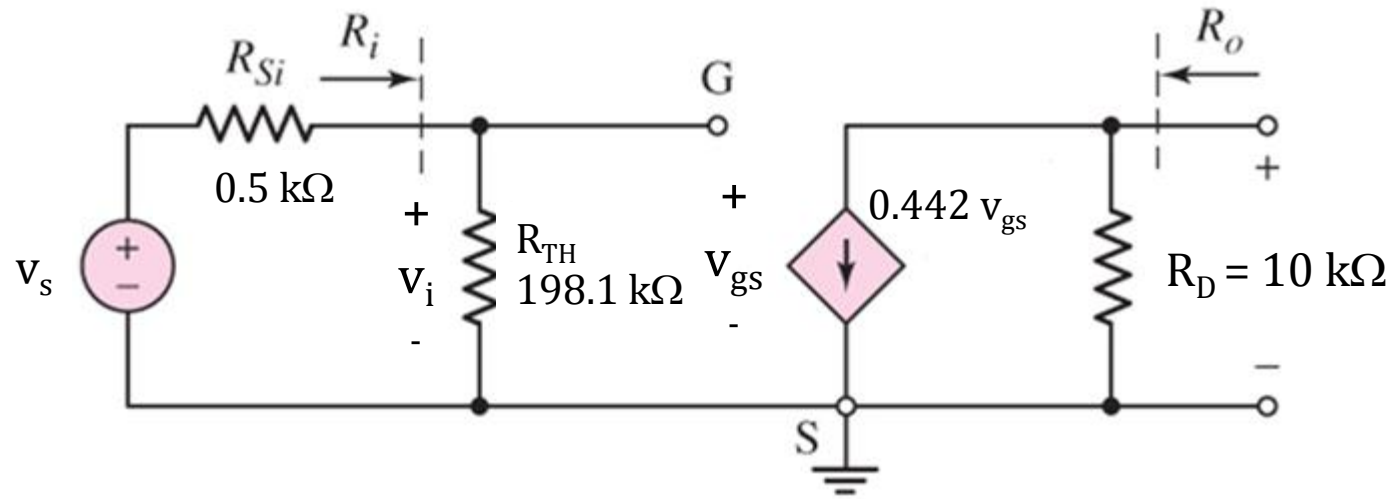


1. The output resistance, $R_o = R_D$
2. The output voltage:

$$v_o = -g_m v_{gs} (R_o) = -g_m v_{gs} (10) = -4.42 v_{gs}$$

3. Get v_i in terms of v_{gs}

$$v_{gs} = v_i$$

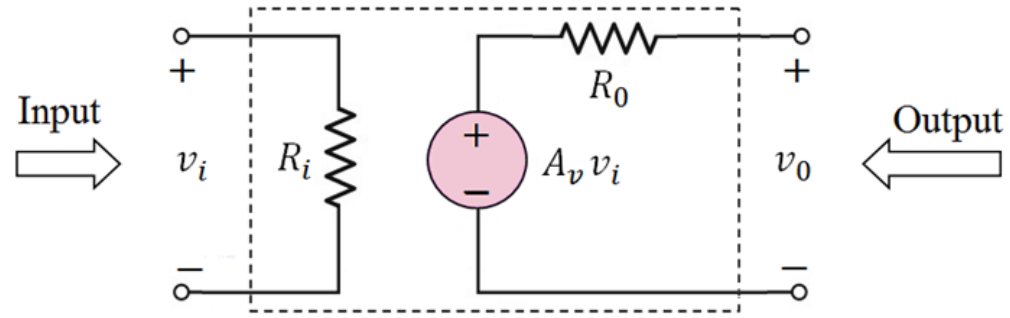

Equivalent circuit of a voltage amplifier


Equation of v_o : $v_o = -g_m v_{gs} (R_o) = -g_m v_{gs} (10) = -4.42 v_{gs}$

$V_i = V_{gs}$

$A_v v_i = v_o \leftarrow$ open circuit voltage

$A_v \cancel{v_i} = -4.42 v_{gs} = -4.42 \cancel{v_i}$

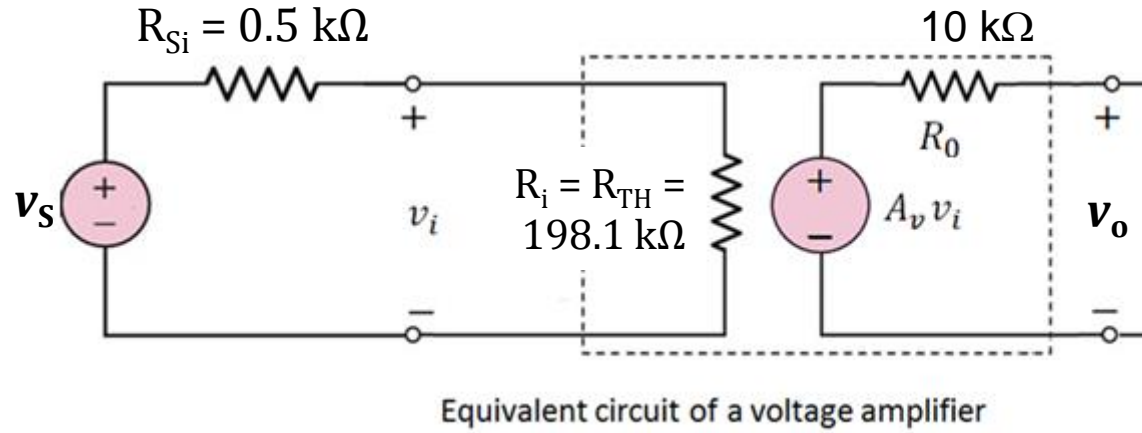$A_v = -4.42 \leftarrow$ open circuit voltage gain



To find new voltage gain, v_o/v_s with input signal voltage source, v_s

v_i in terms of $v_s \rightarrow$ use voltage divider:

$$v_i = [R_i / (R_i + R_s)] * v_s = 0.9975 v_s$$

$v_o = A_v v_i \leftarrow$ because there is no load resistor

$$v_o = -4.42 (0.9975 v_s)$$

$$v_o/v_s = -4.41$$