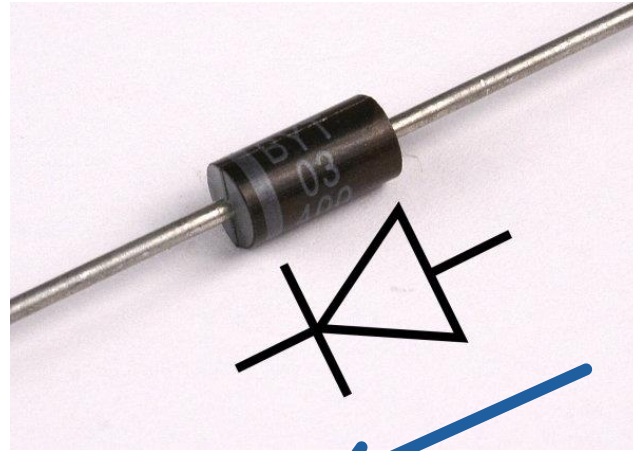



# CHAPTER 1

## Introduction to Electronics and Basic Amplifiers


# PN Junction - Diode



Current Flow

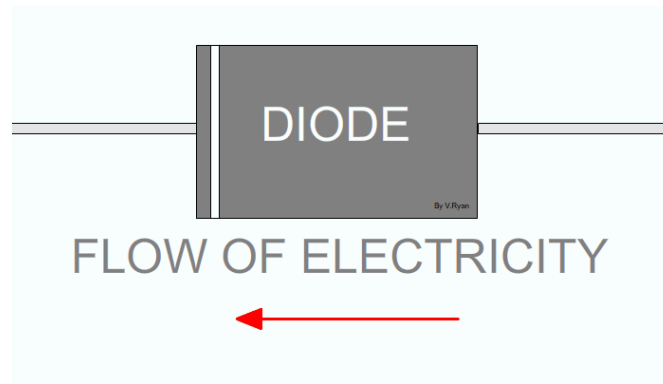


# Bipolar Junction Transistor: BJT

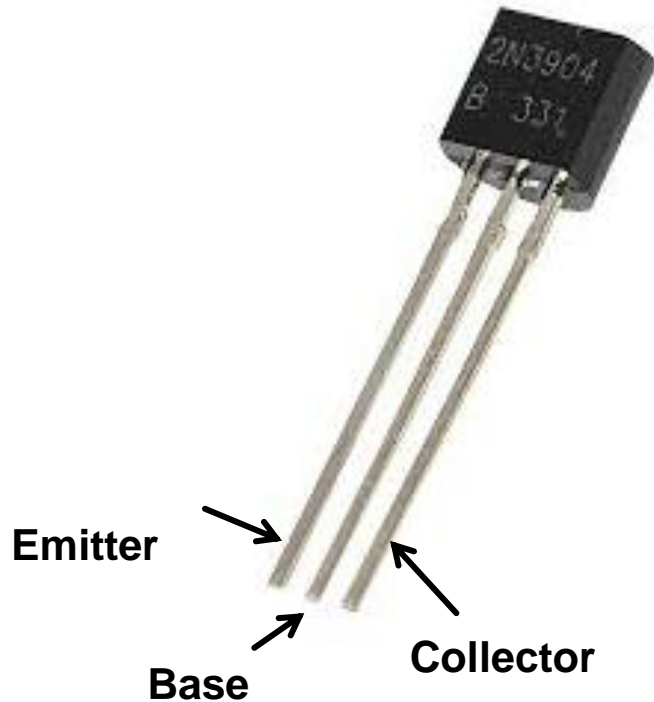

Voltage at Base must be large enough to turn on the transistor to allow current to flow

# Field Effect Transistor: FET

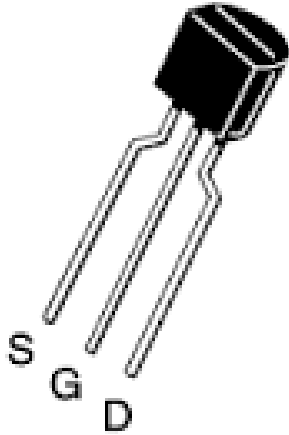

**S = Source**  
**G = Gate**  
**D = Drain**

# Passive and Active Components

## Passive Components:

**Do not require/depend on power supply for its operation** or the device which electrical characteristics does not depend on the power supply

Examples: Resistor, capacitor, inductor


## Active components:

**Do require/depend on power supply for its operation** or the device which electrical characteristics depend on the power supply

Examples: Transistors such as BJT and FET
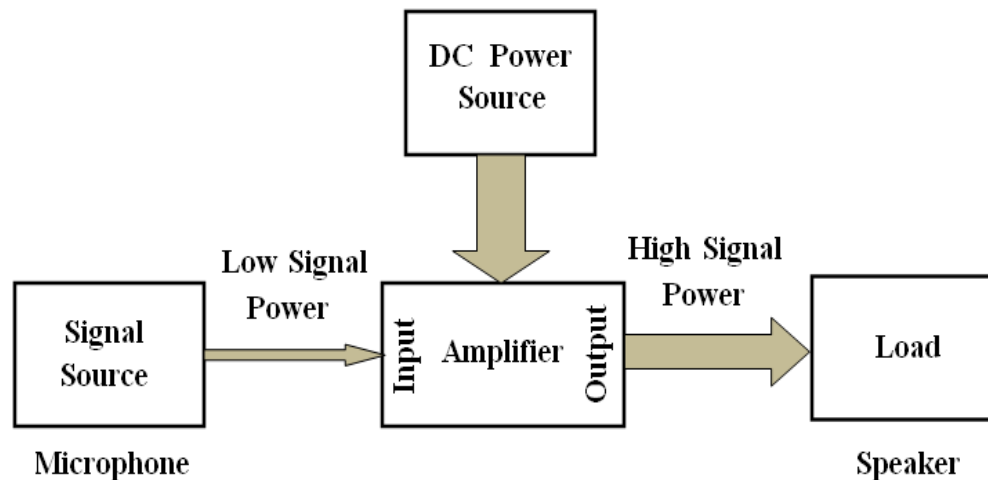
# Electronic Circuits


- An electronic circuit **generally contains both the passive and active components**. Therefore, a DC power supply is essential for the operation of its active components. An electronic processing or amplifier devices also need different power source than its DC operating power source called input signal.
- This input signal characteristics and power can be modified by the electronic circuit with the presence of its DC operating power supply. The processed input signal which is obtained from the electronic circuit is called output signal.



Block diagram of an electronic circuit (Amplifier)

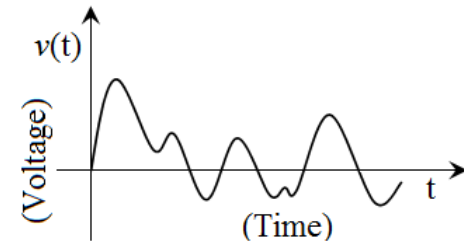
# Analog and Digital Signals

An electrical signal is a **time varying voltage or current** which bears the information by altering the characteristics of the voltage or current. In an analog signal the characteristics of the voltage or current which represents the information can be any value.



Analog signal

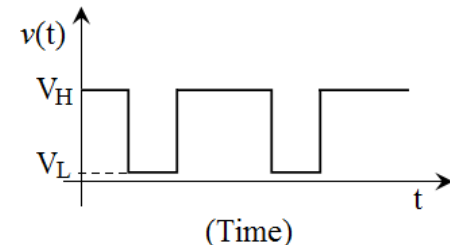Digital signal must **have discrete value**, it is said quantization. In a digital signal the characteristics of the voltage or current which represents the information has **only two values and sometimes it is called binary signal**.





Digital signal
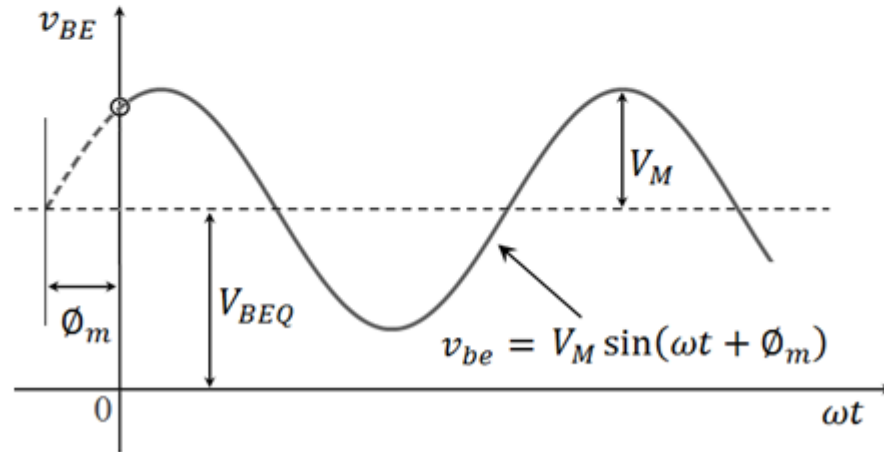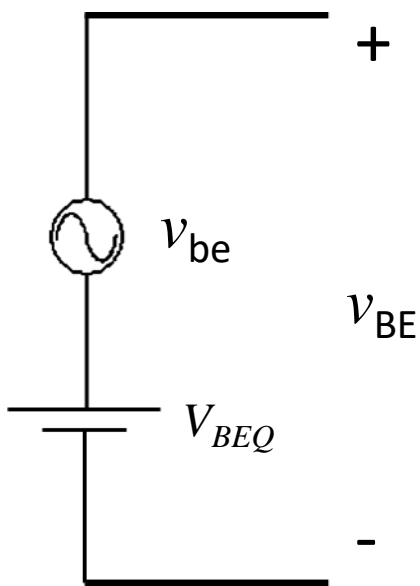
# Representation of Signal




A sinusoidal voltage when it is superimposed on a DC voltage can be represented as

$$v_{BE} = V_{BEQ} + v_{be} = V_{BEQ} + V_M \sin(\omega t + \phi_m)$$



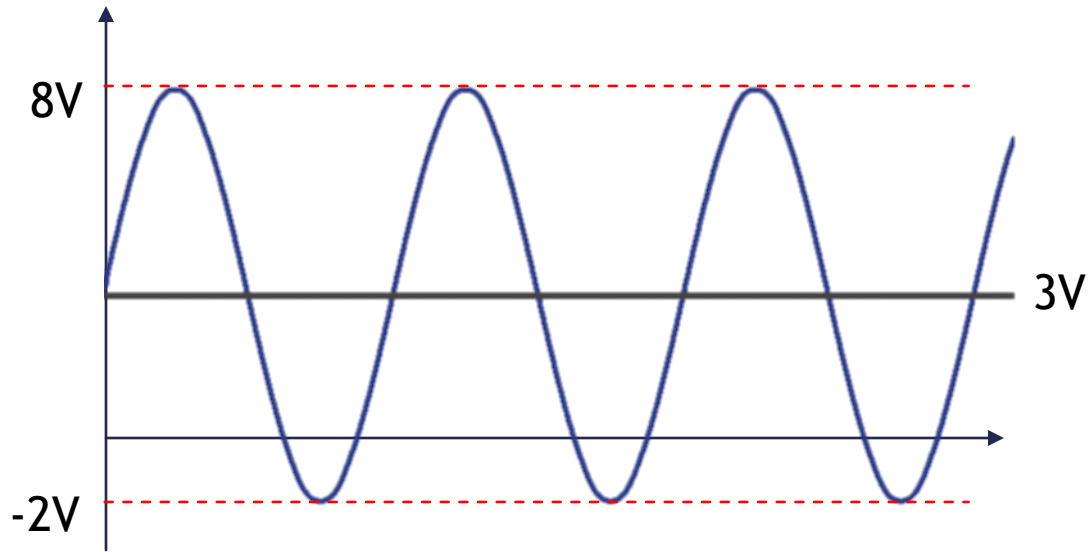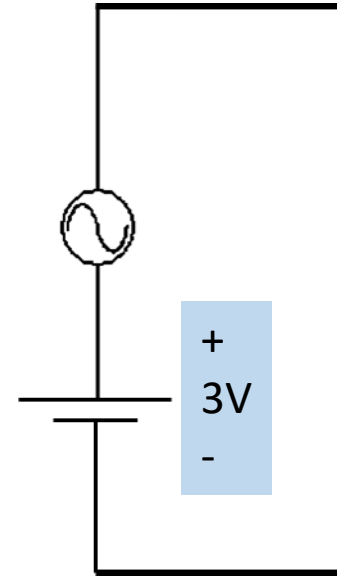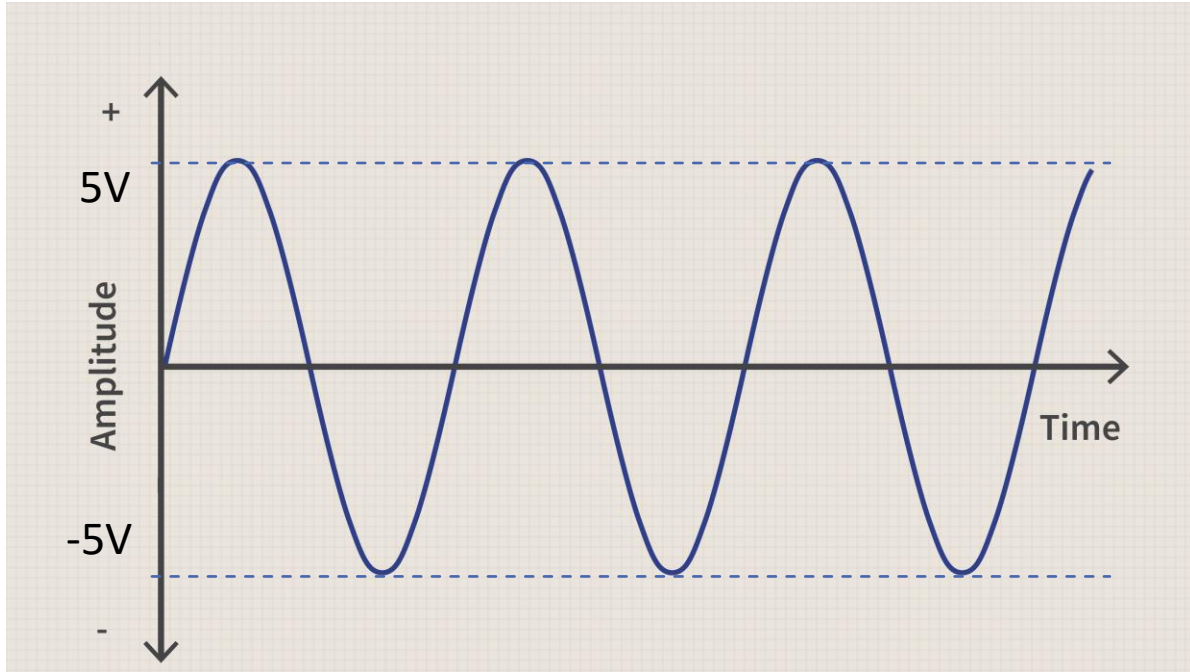Sinusoidal voltage superimposed on DC voltage  $V_{BEQ}$





$$v_{BE} = V_{BEQ} + v_{be} = V_{BEQ} + V_M \sin(\omega t)$$

<b>Variable Notation</b>	<b>Meaning</b>
$v_{BE}$	Total instantaneous value
$v_{be}$	Instantaneous AC value
$V_{BEQ}$	DC value

# Voltage Amplifier

# Amplifier Characteristics


The voltage gain of the amplifier is defined as the ratio between output voltage and input voltage, mathematically

The gain of a voltage amplifier is unit less (there is no unit)

$$A_v = v_o / v_i.$$

$$\text{Gain} = \frac{\text{output}}{\text{input}}$$

$A_v$  = open circuit  
voltage gain

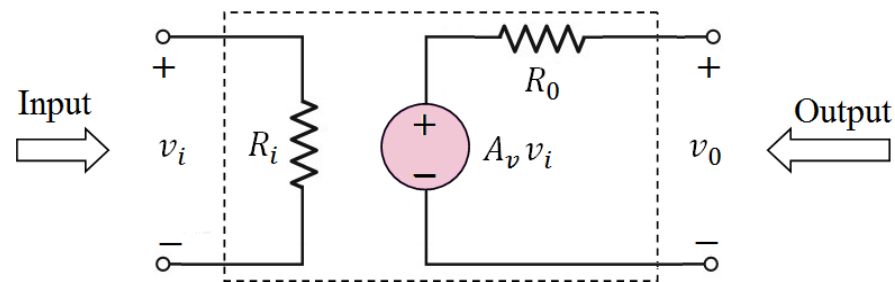


Equivalent circuit of a voltage amplifier

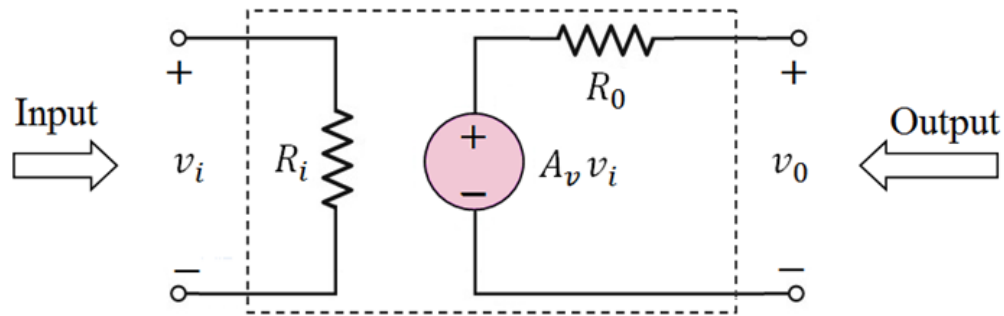**Example 1:** The output voltage of an amplifier is 10.5V when its input is 150mV. Determine the voltage gain of the amplifier.

Solution: Here,  $v_0 = 10.5\text{V}$  and  $v_i = 150\text{mV} = 0.15\text{V}$


So the voltage gain,  $A_v = \frac{10.5\text{V}}{0.15\text{V}} = 70$



Equivalent circuit of a voltage amplifier

**Example 2:** A load resistance of  $475\Omega$  is connected with the output of a voltage amplifier as shown in the Figure. The output voltage across the load resistance is  $10.5V$  when the amplifier input is  $150mV$ . Determine the open circuit voltage gain,  $A_v$  of the amplifier. Assume that the output resistance of the amplifier is  $25\Omega$ .

$A_v v_i \neq v_o$

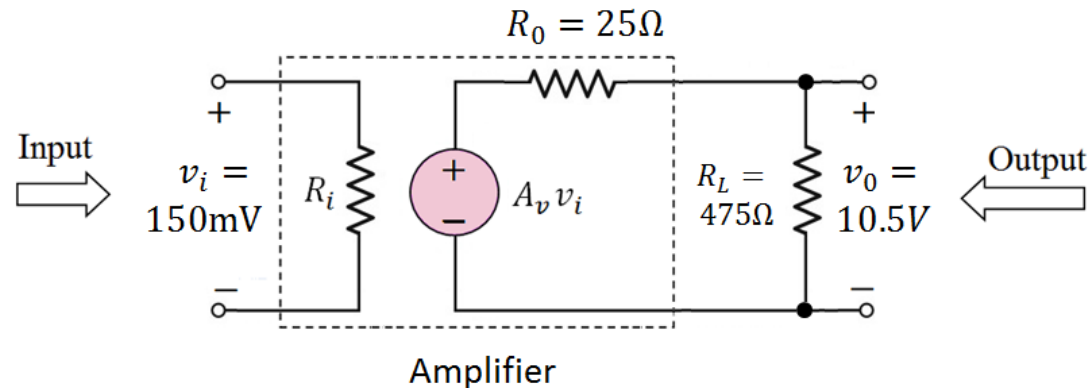

**Solution:** Here,  $v_o = 10.5V$  and  $v_i = 150mV = 0.15V$

Output current in the circuit,  $i_o = \frac{10.5V}{475\Omega} = 22.1mA$

So the open circuit voltage of the amplifier can be calculated by using KVL at the output loop


$$A_v v_i = R_o i_o + R_L i_o = 25\Omega \times 22.1mA + 475\Omega \times 22.1mA = 11.05V$$

The open circuit voltage gain of the amplifier,  $A_v = \frac{11.05V}{0.15V} \cong 73.67$

Avvi = open circuit voltage

**Ex. 3:** The open circuit voltage of a voltage amplifier is 12.5V when its input is connected to a signal source. Assume that the signal source voltage is 2.5 V and its resistance is 2.0k $\Omega$  respectively. If the input and output resistance of the amplifier is 5k $\Omega$  and 50 $\Omega$  respectively.

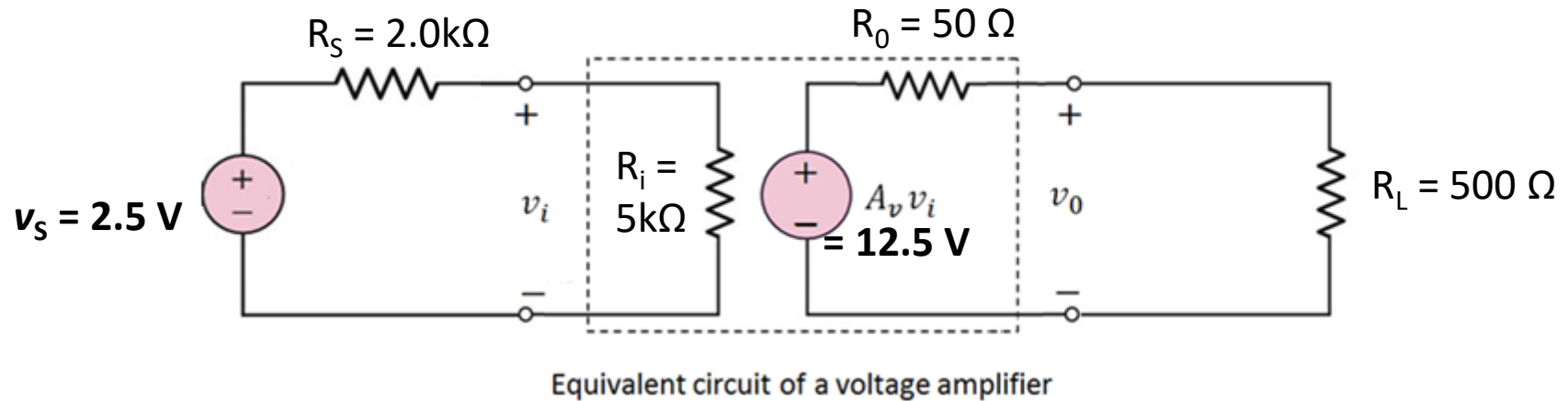- i. Calculate the value of  $A_v$
- ii. The amplifier output is connected to drive a load resistance 500 $\Omega$ , determine the output voltage across the load resistance.



1. Calculate the value of  $v_i$
2. We know that the open circuit voltage,  $A_v v_i = 12.5 \text{ V}$
3. For part (ii) Use KVL or voltage divider to calculate output across the load.

1. Calculate the value of  $v_i$

$$v_i = \left( \frac{R_i}{R_i + R_s} \right) v_s \quad v_i = (5/7) * 2.5$$
$$v_i = 1.786 \text{ V}$$

2. We know that the open circuit voltage,  $A_v v_i = 12.5 \text{ V}$

$$A_v v_i = 12.5 \text{ V}$$

$$A_v = 12.5 / 1.786 = 7$$

3. For part (ii) Use KVL or voltage divider to calculate output across the load.

$$v_o = \left( \frac{R_L}{R_L + R_o} \right) A_v v_i \quad v_o = (500/550) * 12.5$$
$$v_o = 11.36 \text{ V}$$

**Answers:**


$$A_v = 7.0$$

**Voltage across load = 11.36 V**


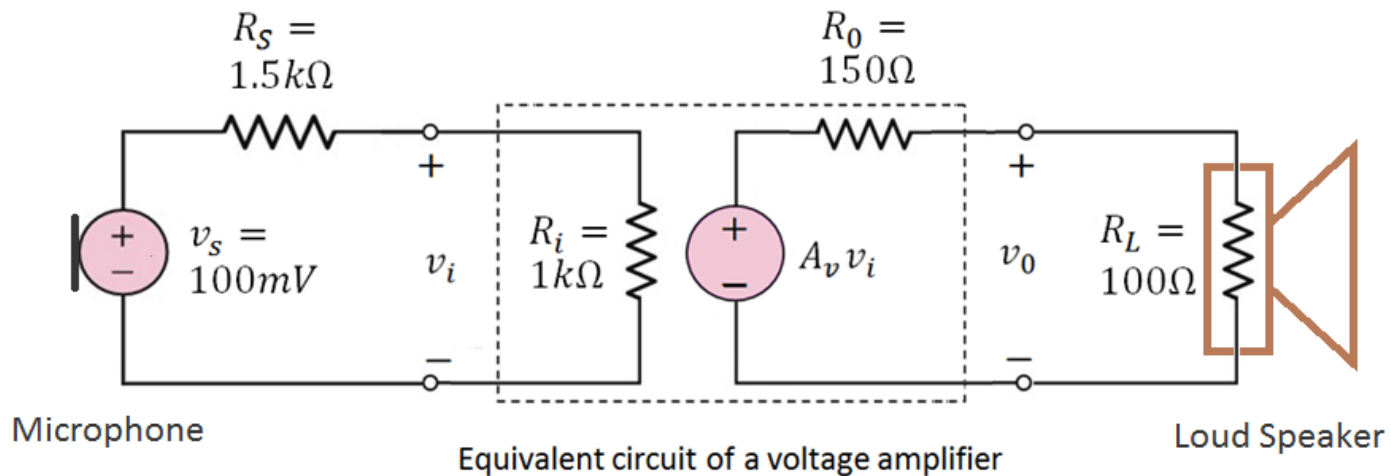
### Ex. 4:


The figure shows a public address system i.e. a voltage amplifier input is connected with a microphone (input signal source) and output of the amplifier is connected with a loud speaker (load). If the voltage of the microphone is 100 mV determine the output voltage across in the speaker. Assume that the gain of the amplifier  $A_v = 100$  the input and output resistances are,  $R_i = 1k\Omega$ ,  $R_o = 150\Omega$  respectively. It is also assume that the microphone and speaker resistances are  $R_s = 1.5k\Omega$  and  $R_L = 100\Omega$  respectively.



1. Must calculate  $v_i$
2. Calculate the open circuit voltage,  $A_v v_i$
3. Then use voltage divider to find out the voltage across  $R_L$

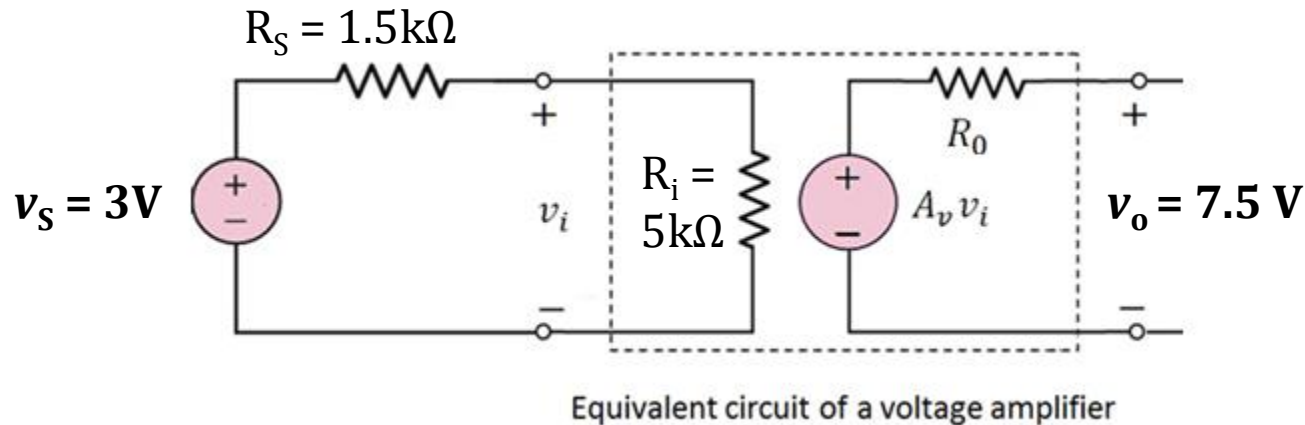**Answer: 1.6V**

**Ex. 5:** The **open circuit voltage of a voltage amplifier is 7.5V** when its input is connected to a signal source. Assume that the signal source voltage is 3.0V and its resistance is 1.5k $\Omega$  respectively. If the input resistance of the amplifier is 5k $\Omega$ , what would be the voltage gain of the amplifier.



1. Must calculate  $v_i$
2. We know that the open circuit voltage,  $A_v v_i = 7.5 \text{ V}$
3. Calculate  $A_v$

**Answer: 3.25**